

04.04.2011
①

$$* I_E = I_C + I_B$$

$$* I_C = \beta \cdot I_B$$

$$* I_E = \beta \cdot I_B + I_B$$

$$** I_E = (\beta + 1) I_B$$

$$* \beta \gg 1$$

$$* I_E \approx \beta I_B \approx I_C$$

$$\alpha = \frac{I_C}{I_E}$$

$$\alpha = \frac{\beta \cancel{I_B}}{(\beta + 1) \cancel{I_B}}$$

$$* \alpha = \frac{\beta}{\beta + 1} < 1$$

$$\alpha \beta + \alpha = \beta$$


$$\alpha \beta - \beta = -\alpha$$

$$\beta - \alpha \beta = \alpha$$

$$\beta(1 - \alpha) = \alpha$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

DC BIASING the BJT's

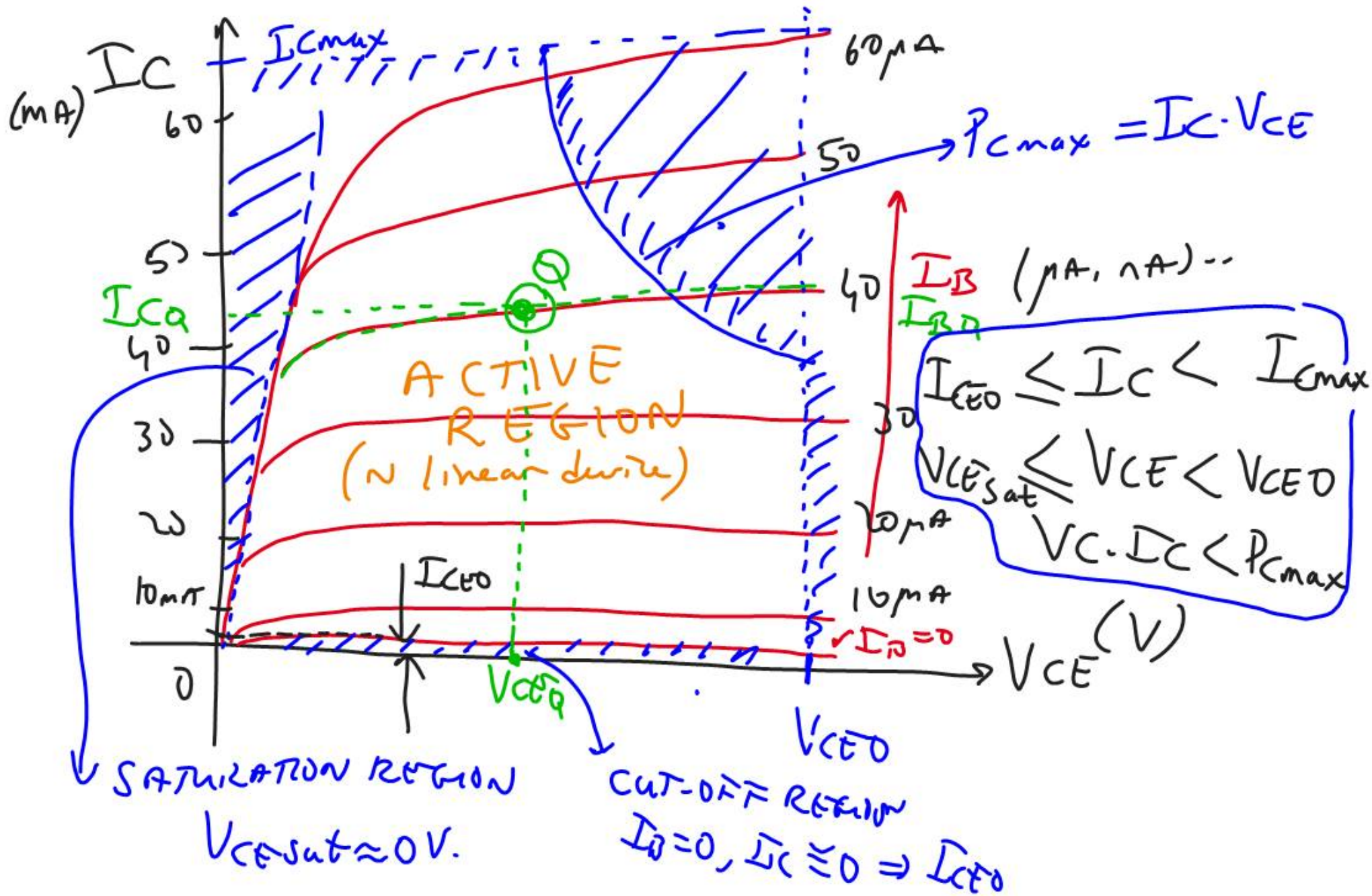


Biassing \Rightarrow is made to make the BJT operate in the desired operating point

\Downarrow
the quiescent point (Q)


In active area we use transistors as Linear Devices

to amplify the small signals. (to some extent)

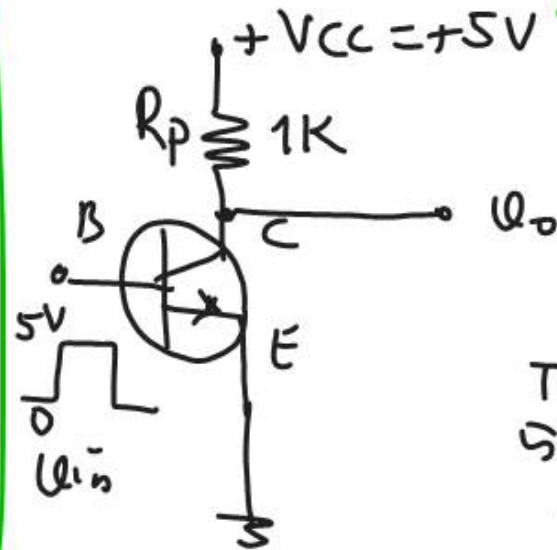
Nonlinear Operation of a Transistor \Rightarrow Transistor as a SWITCH for example.



When $V_{in} = 5V$

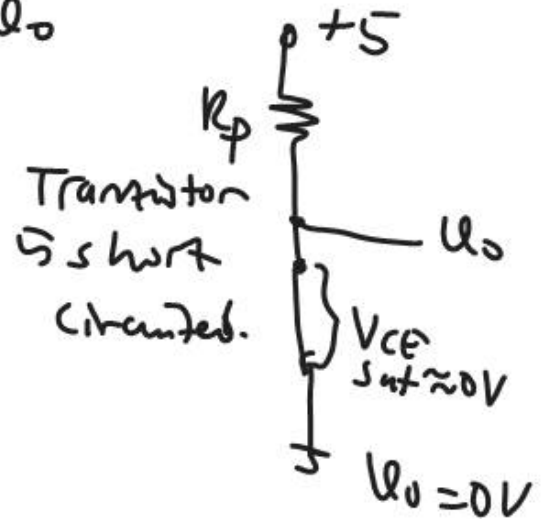

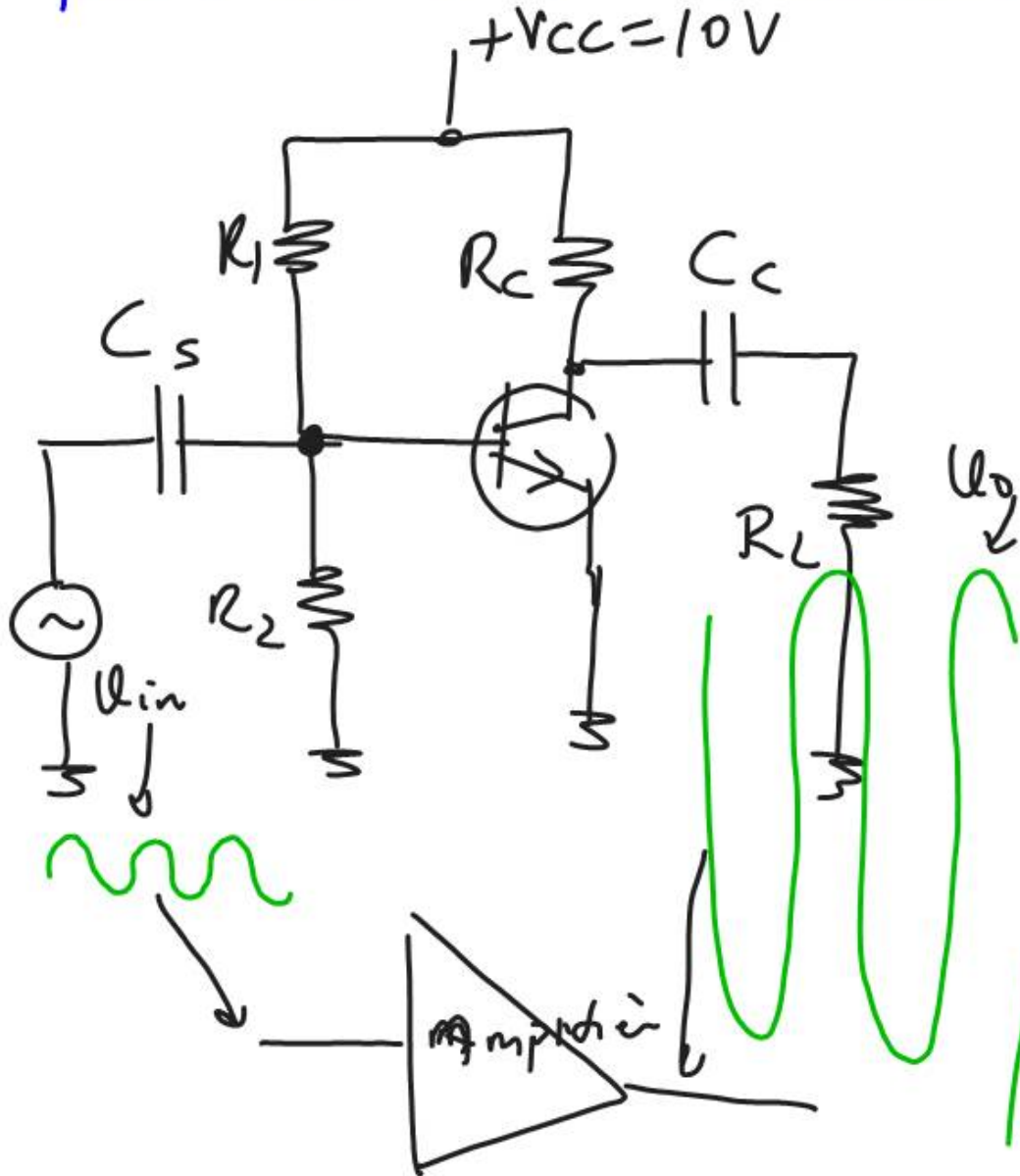For linear operation
The transistor as an amplifier



When $U_{in} = 0V$
The transistor goes into CUTOFF region $\rightarrow I_C = 0$

