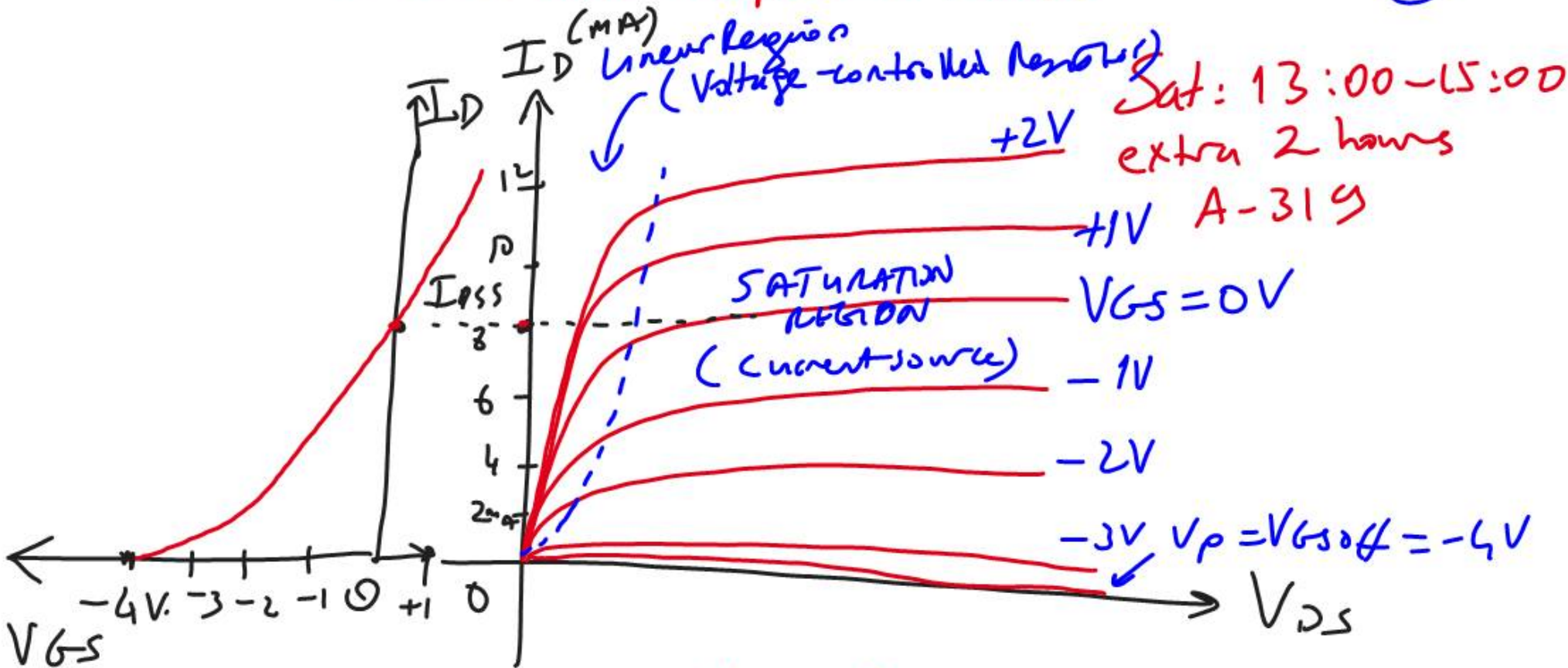


n-channel Depletion Mode

25.04.2011
©





$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

Shockley's Eqn.


n-channel Depletion-mode MOSFET (D-MOSFET)
(Normally-on)

p-channel Depletion mode MOSFET

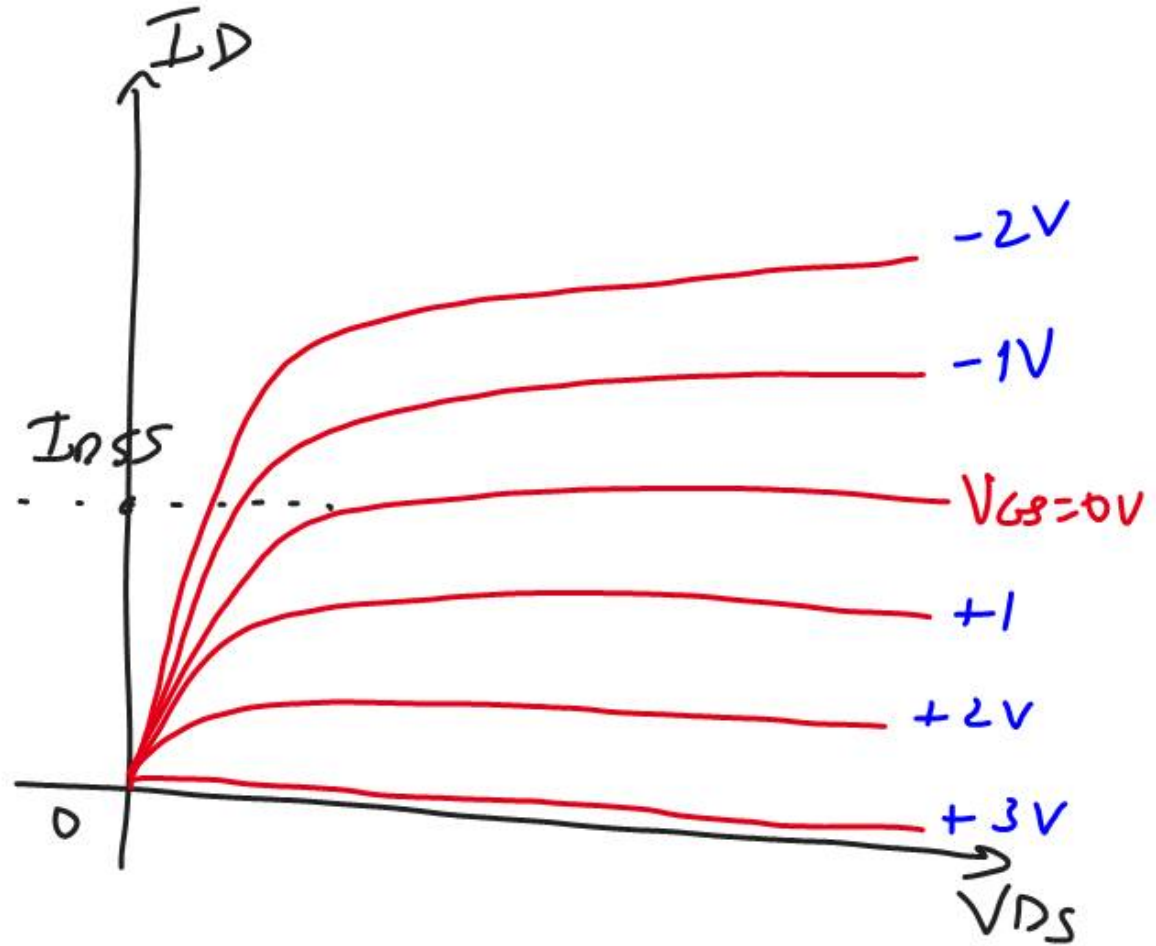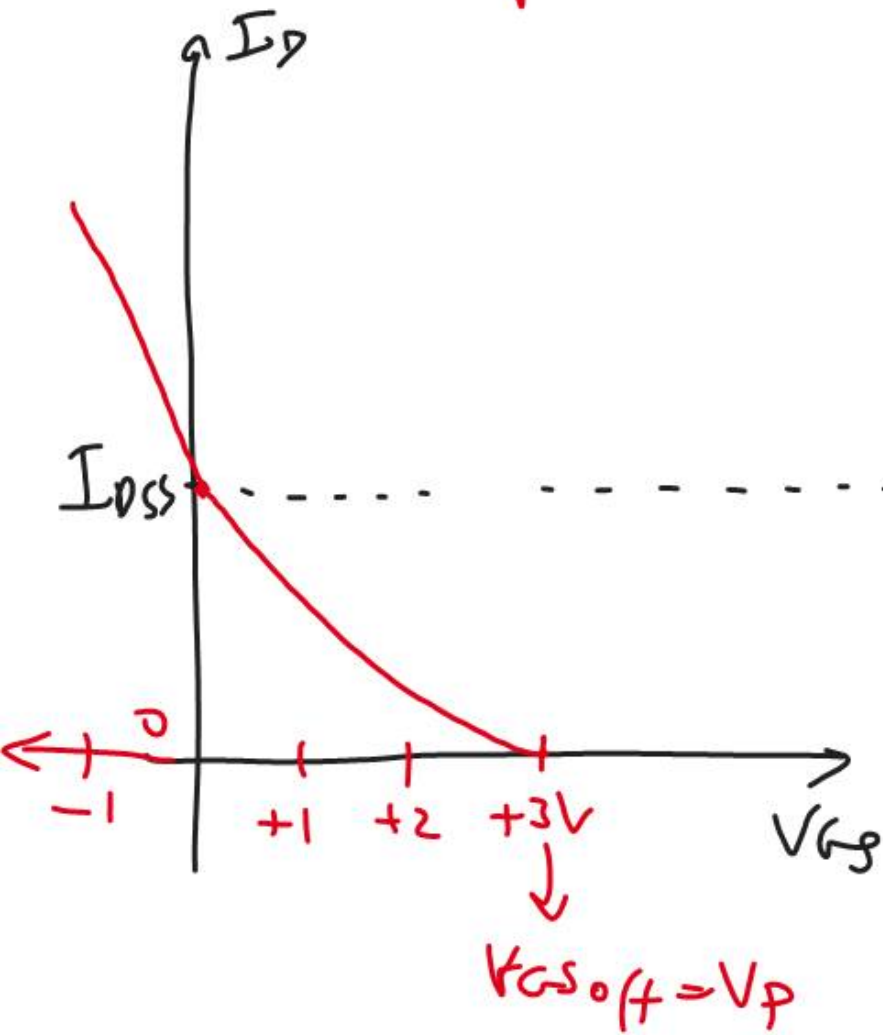

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Enhancement type (normally-off) MOSFETS

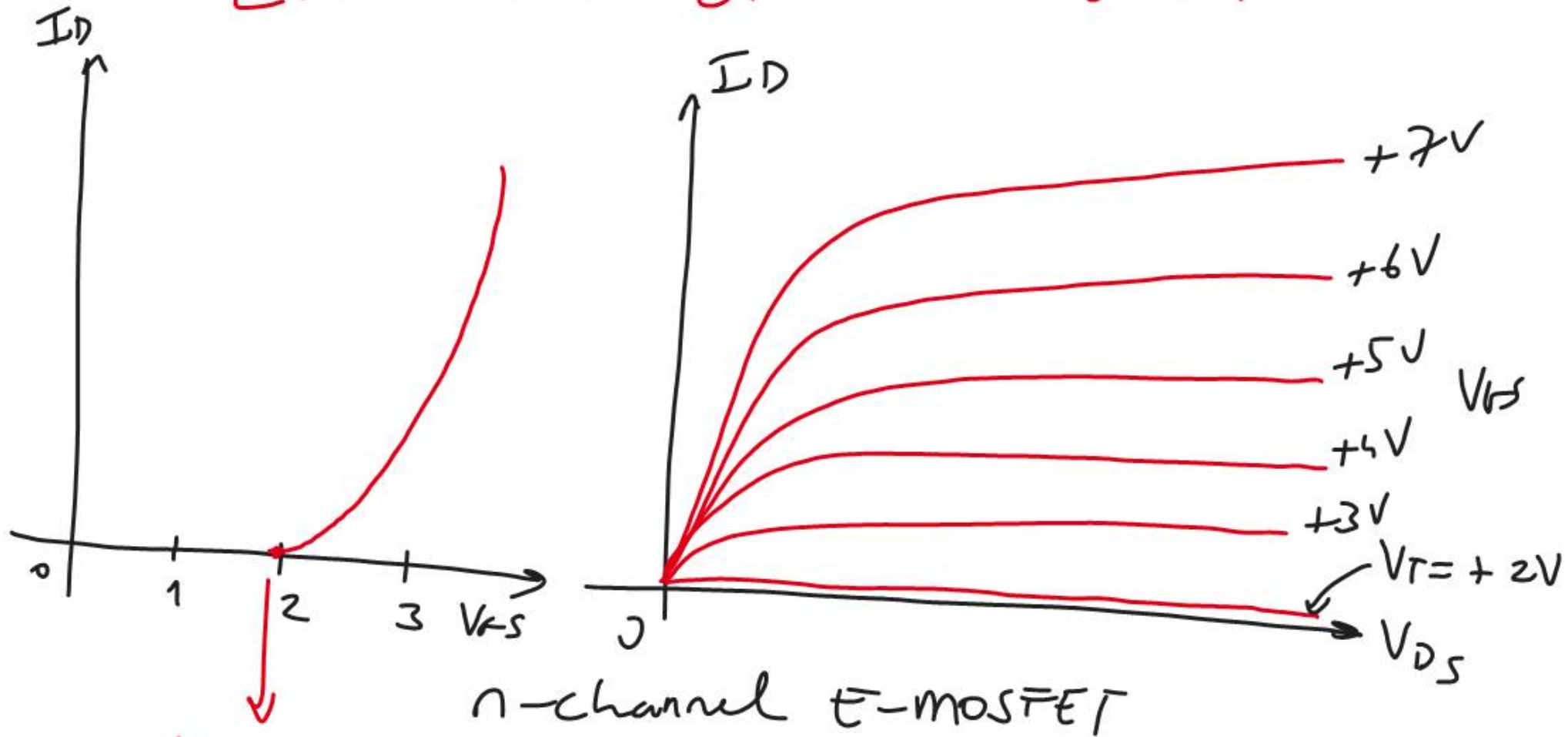

n-channel E-MOSFET

$V_{GS(off)} = V_T \rightarrow$ Threshold voltage

$$I_D = k \cdot (V_{GS} - V_T)^2$$

ex $k = 0.5 \times 10^{-3} \text{ A/V}^2$

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2}$$

FET BIASING

Remember that:


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = k (V_{GS} - V_{T0})^2$$

for E-MOSFET

for JFETs, D-MOSFETs

① JFET BIASING

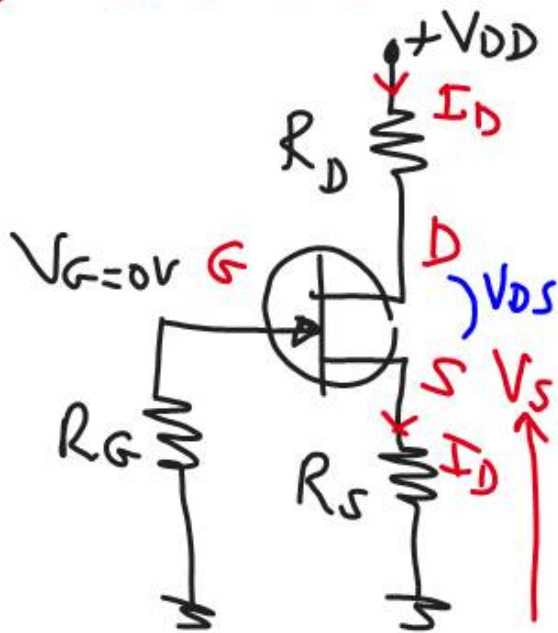


SELF-BIASING

$$V_S = I_D \cdot R_S$$

$$V_{GS} = V_G - V_S$$

$$= 0 - I_D \cdot R_S$$

$$V_{GS} = -I_D \cdot R_S$$

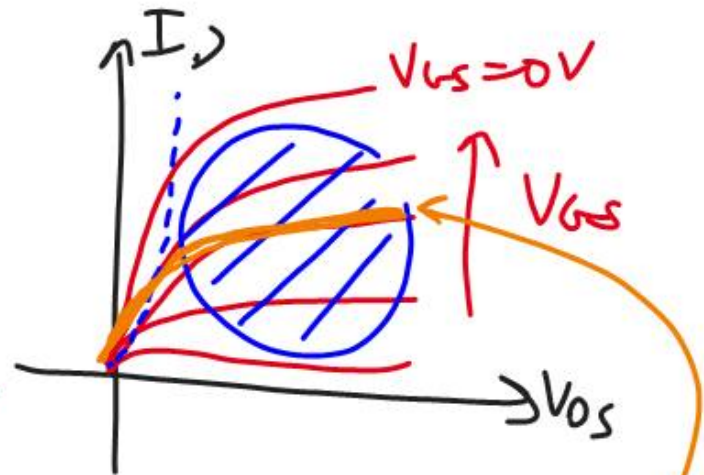

Output KVL

$$V_{DD} - I_D \cdot R_D - V_{DS} - I_D \cdot R_S = 0 \rightarrow V_{DS}$$

$$V_{GS} = -I_D \cdot R_S \Rightarrow 2 \text{ unknowns } I_D, V_{GS}$$

Eqn. 1


Graphical method

Equation Method (Analytic method)

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Eqn. 2

are known

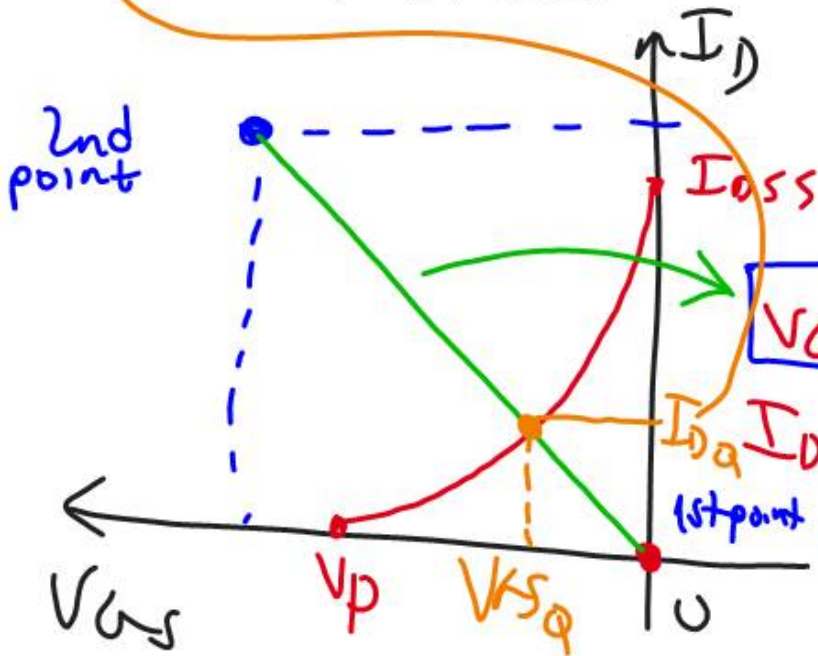

$$V_{GS} = -I_D R_S \text{ a line equation}$$

$$I_{DQ}, I_D = 0 \quad V_{GS} = 0$$

give a value to I_D
and determine V_{GS}
as the second point

For the operation point $Q \Rightarrow V_{GSQ}, I_{DQ}, V_{DSQ}$

