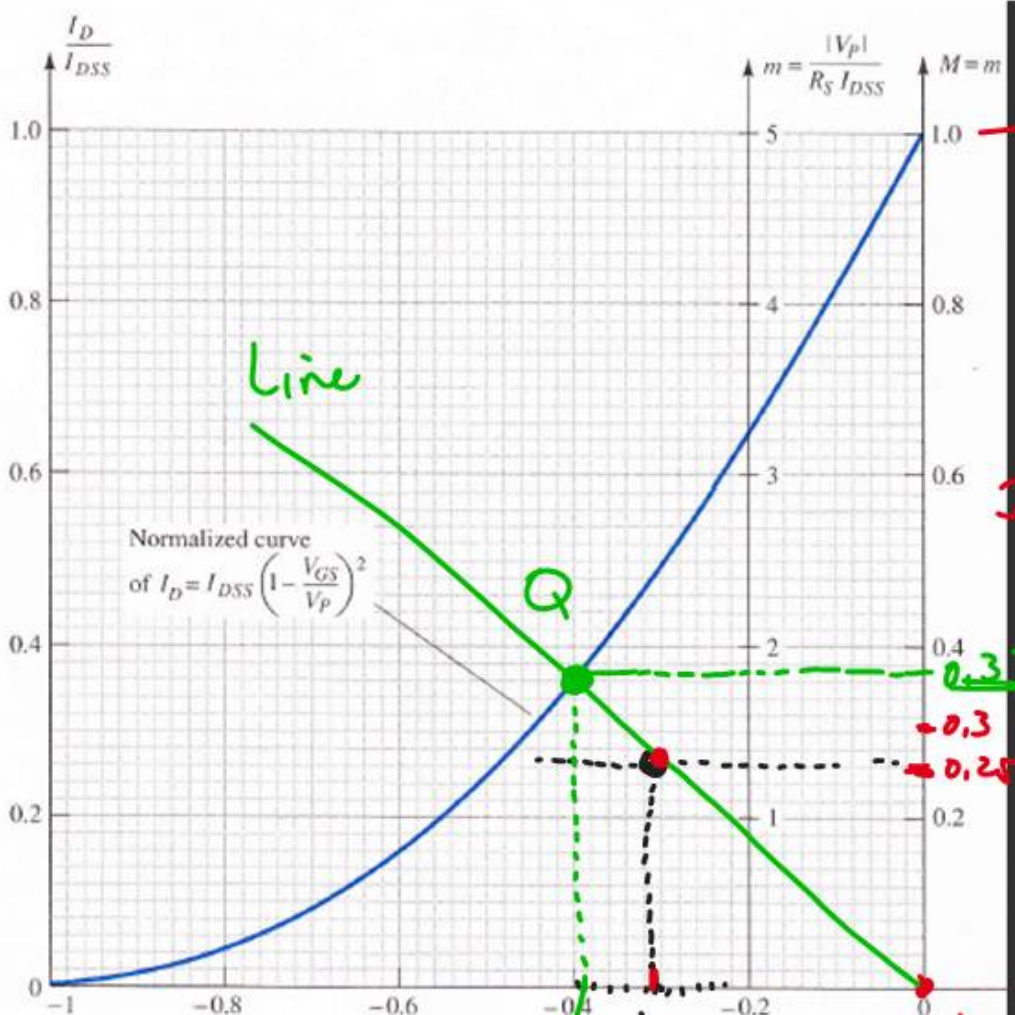


26.04.2011
 <Z>

Ex Determine Q point (V_{GSQ}, I_{DQ}, V_{DSQ})
 $\sim \frac{I_D}{I_{DSS}}$




$\frac{V_{GS}}{|V_P|}$

$V_{GSQ} \sim -0.4$

(0,0)
1st point

Assistant
 Osman Öz

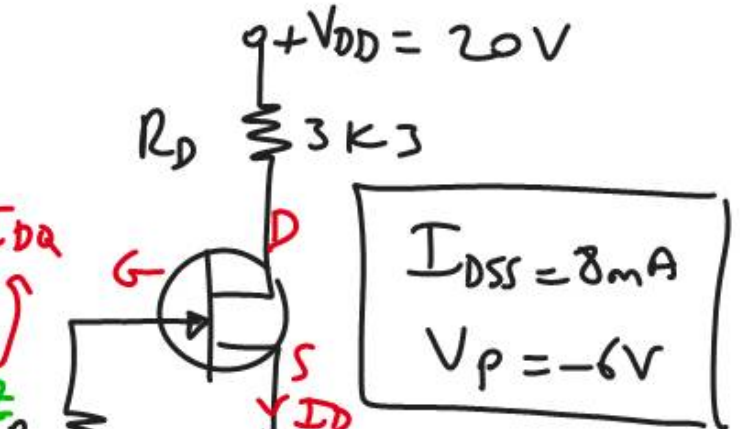

$I_{DSS} = 8mA$
 $V_P = -6V$

$$V_{GS} = V_G - V_S$$

$$V_G = 0V$$

$$V_{GS} = -V_S$$

$$V_{GS} = -I_D \cdot R_S$$

$$V_{GS} = -10^3 \cdot I_D$$

After finding Q in the graphs (characteristics)

$$\frac{I_{DQ}}{I_{DSS}} \cong 0.37 \rightarrow I_{DQ} = 0.37 \times 8mA$$

$$\frac{V_{GSQ}}{|V_P|} \cong -0.4 \rightarrow V_{GSQ} = -0.4 \times 6V$$

① Graphical Solution

a linear equation between I_D and V_{GS} .

1st point is $\rightarrow (0, 0)$

$$V_{GS} = 0 \quad I_D = 0 \rightarrow 0.216A$$

$$V_{GS} = -2V \rightarrow I_D = -\frac{2}{10^3} = +2mA$$

To find on the characteristics:

$$\frac{V_{GS}}{V_P} = \frac{-2V}{(6)} = -\frac{1}{3} = -0.333$$

$$\frac{I_D}{I_{DSS}} = \frac{2 \times 10^{-3}}{8 \times 10^{-3}} = \frac{1}{4} = 0.25$$

2nd point is $= (-0.333, 0.25)$

$$I_{DQ} \cong 2.96mA$$
$$V_{GSQ} = -2.4V$$

$$V_{DD} - I_D R_D - I_D R_S - V_{DS} = 0 \quad \text{Output KVL}$$


$$V_{DD} - I_D (R_D + R_S) - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{DS} = 20V - 2.96 \times 10^{-3} (3.3 + 1) \times 10^3$$

$$V_{DSQ} \cong 20 - 2.96 \times 4.3$$

$$V_{DSQ} \cong 7.27V$$

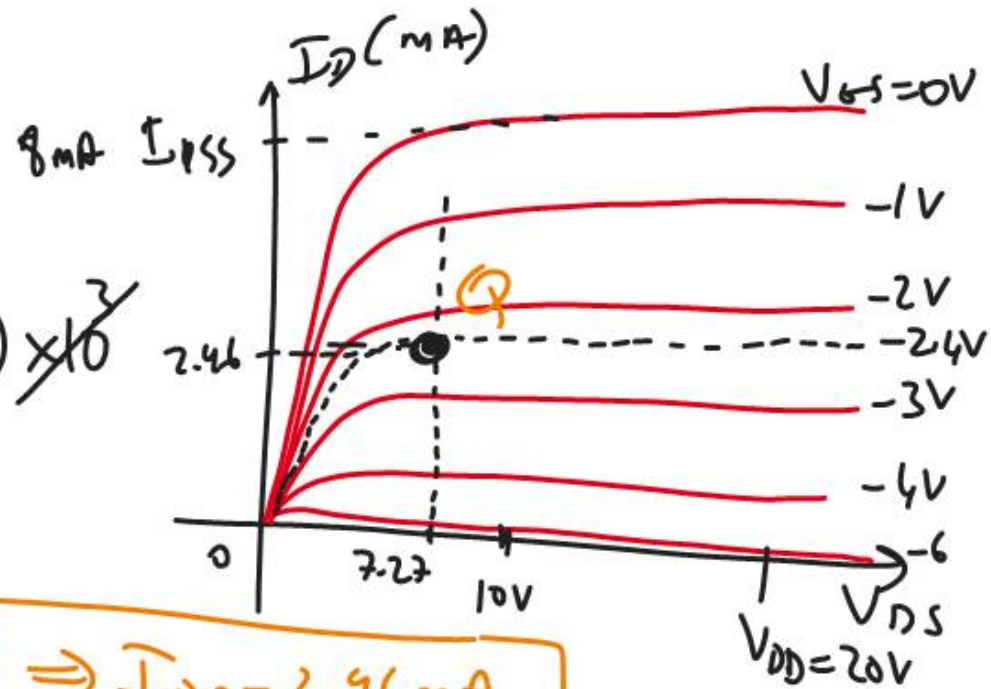

$$\begin{aligned} Q \Rightarrow I_{DQ} &= 2.96 \text{ mA} \\ V_{GSQ} &= -2.4 \text{ V} \\ V_{DSQ} &= +7.27 \text{ V} \end{aligned}$$

2) Analytical method:

$$V_{GS} = -I_D \cdot R_S$$

$$\boxed{V_{GS} = -10^3 I_D} \quad \text{1st Eqn.}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \text{Shockley's Eqn.}$$

$$I_D = 8 \times 10^{-3} \left(1 - \frac{V_{GS}}{-6}\right)^2$$

$$\boxed{I_D = 8 \times 10^{-3} \left(1 + \frac{V_{GS}}{6}\right)^2} \quad \text{2nd equation}$$

Two unknowns $\Rightarrow I_D, V_{GS}$

$$I_D = +8 \times 10^{-3} \left(1 - \frac{10^3 I_D}{6}\right)^2$$

$$= 8 \times 10^{-3} \left(\frac{6 - 10^3 I_D}{6}\right)^2$$

$$I_D = \frac{8 \times 10^{-3}}{36} (6 - I_D \cdot 10^3)^2$$

$$36 I_D = 8 \times 10^{-3} (36 - 12 \times 10^3 I_D + 10^6 I_D^2)$$

$$8 \times 10^{-3} \times 10^6 I_D^2 - 12 \times 10^3 \times 8 \times 10^{-3} I_D - 36 I_D + 8 \times 10^{-3} \times 36 = 0$$

$$8 \times 10^3 I_D^2 - 132 I_D + 8 \times 10^{-3} \times 36 = 0$$

$$ax^2 + bx + c = 0$$

$$I_{D1,2} = \frac{-132 \pm \sqrt{132^2 - 4 \times 8 \times 10^3 \times 36}}{2 \times 8 \times 10^3}$$

$$I_{D1,2} = +8.2 \times 10^{-3} \pm 5.7 \times 10^{-3}$$

I_D can not be greater than $I_{DSS} \Rightarrow 8 \text{ mA}$

$$I_D = (8.25 - 5.7) \times 10^{-3} = \underline{2.55 \text{ mA}}$$

$$\boxed{I_{DQ} = 2.55 \text{ mA}}$$

$$\rightarrow V_{GS} = -I_D \times 10^3$$

$$V_{GS} = -2.55 \times 10^{-3} \times 10^3$$

$$\boxed{V_{GS} = -2.55 \text{ V}}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{DS} = 20 - 2.55 \times 10^{-3} \times 4.3 \times 10^3$$

$$\boxed{V_{DS} = 9.035 \text{ V}}$$

Analytical Solution


$\varphi \Rightarrow$

$$I_{DQ} = 2.55 \text{ mA}$$

$$V_{GSQ} = -2.55 \text{ V}$$

$$V_{DSQ} = 9.035 \text{ V}$$

a VOLTAGE DIVIDER BIASING

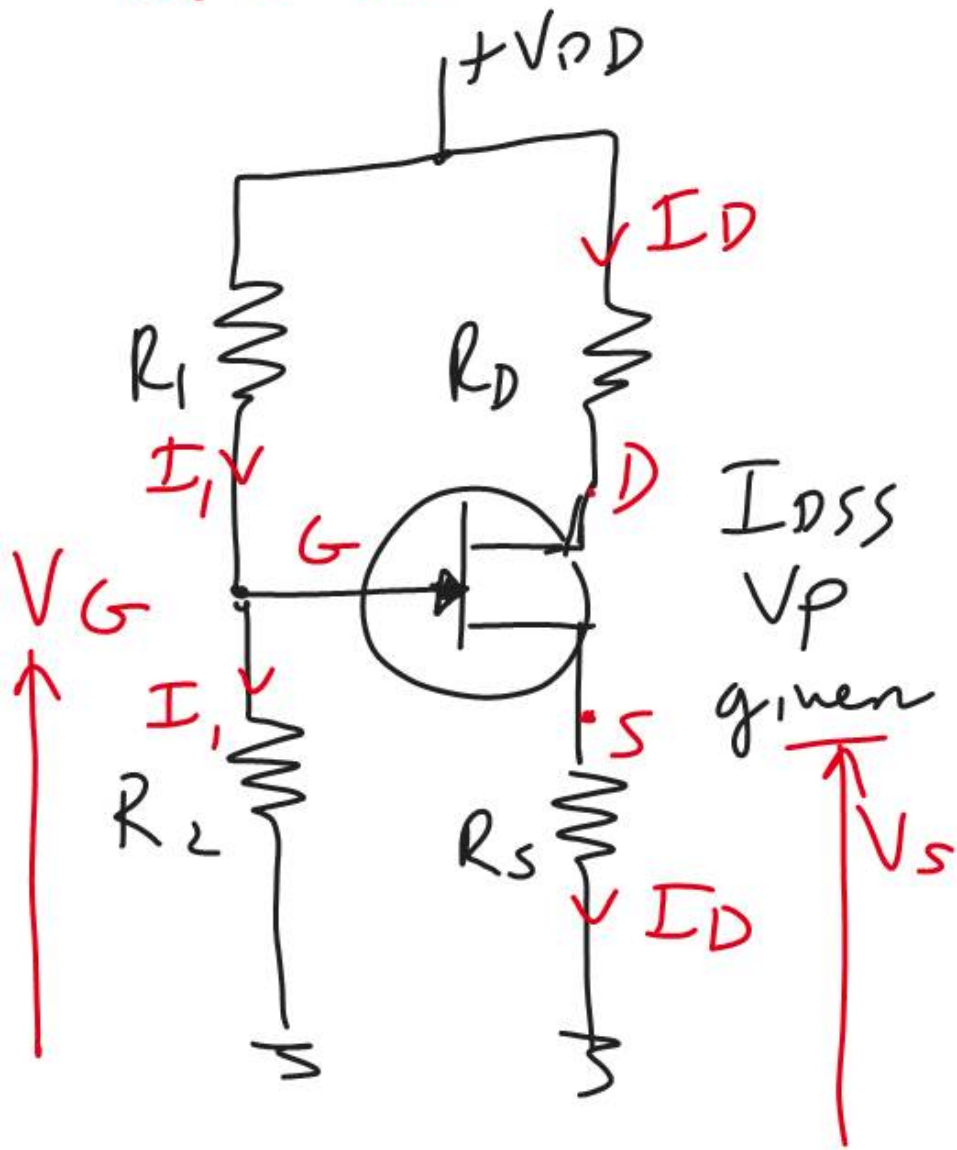


$$V_G = \frac{V_{DD}}{R_1 + R_2} \cdot R_2$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = V_G - I_D \cdot R_S$$

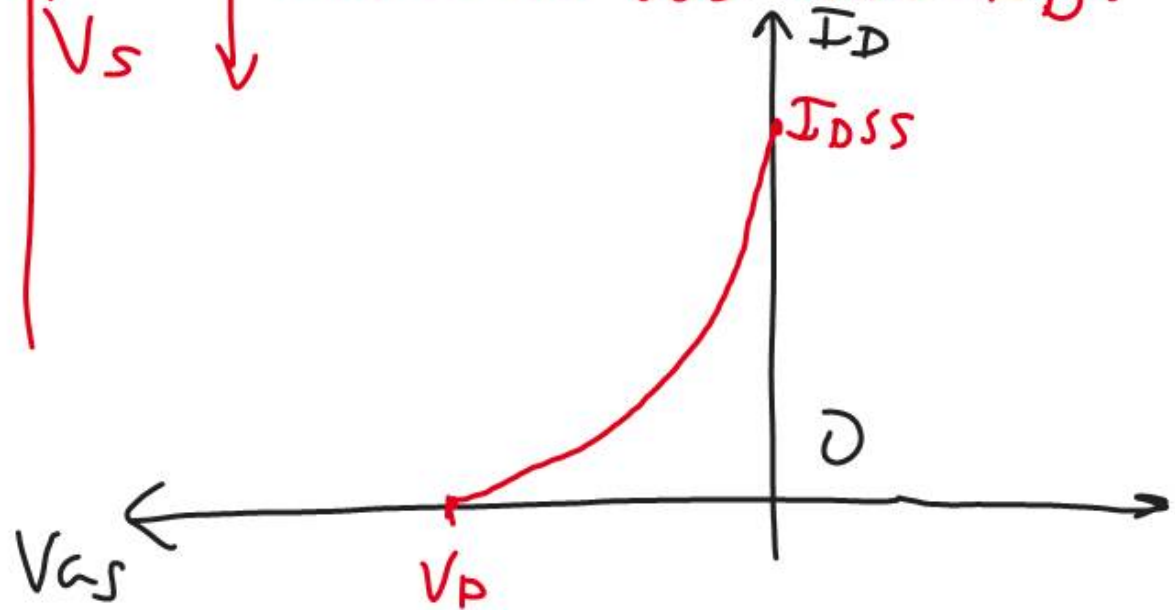a curve equation between V_{GS} and I_D .




Draw the line


$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = 0 \rightarrow I_D = \frac{V_G}{R_S}$$

$$I_D = 0 \rightarrow V_{GS} = V_G$$

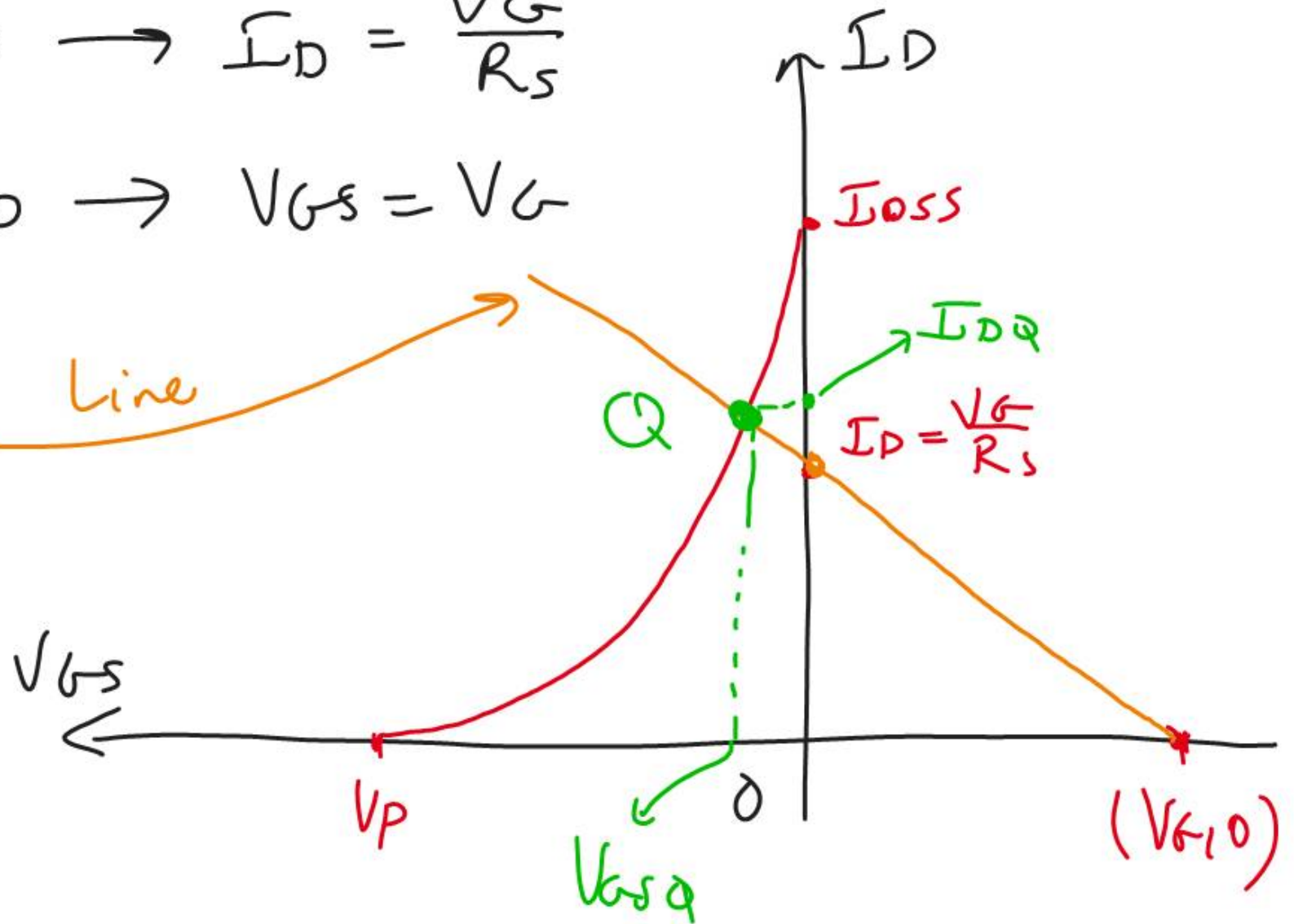

D-MOSFET BIASING


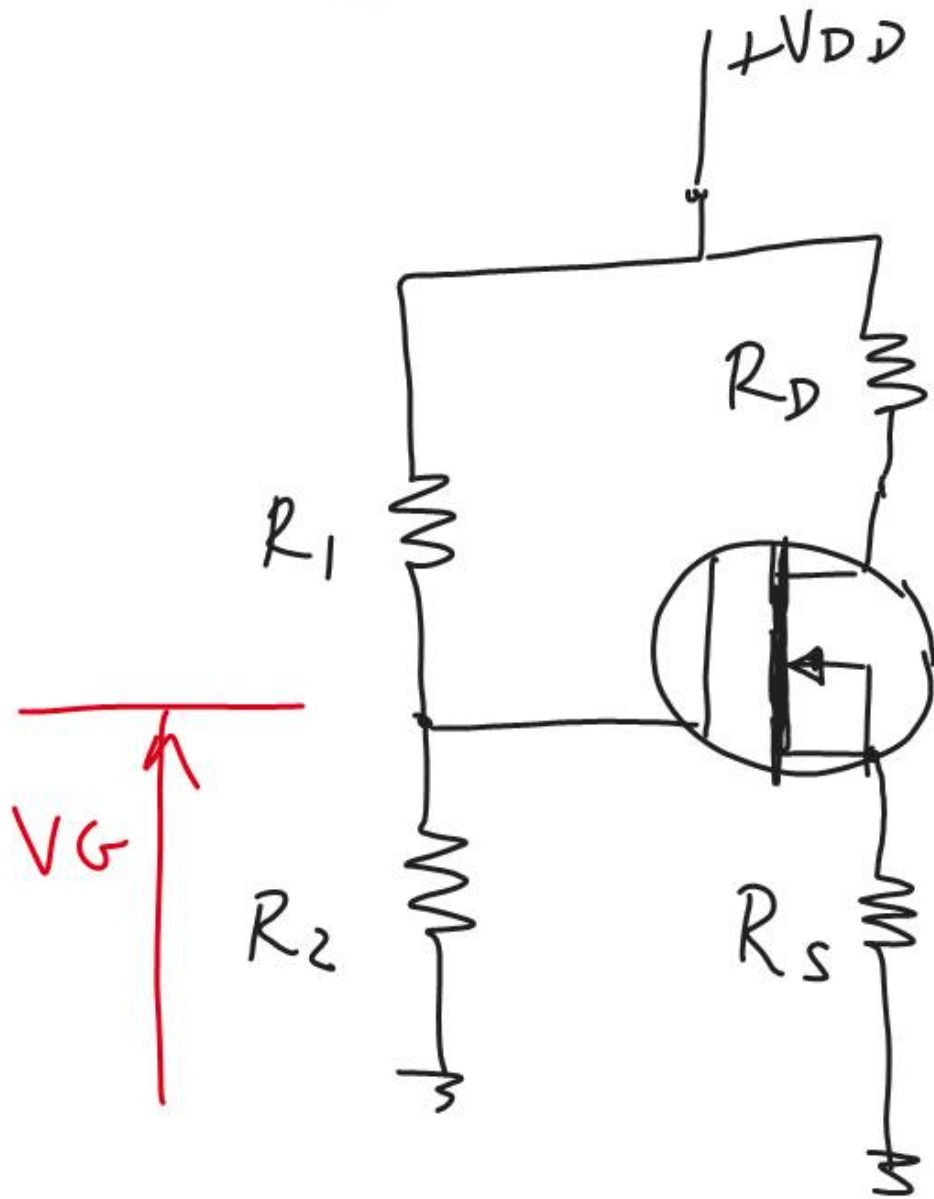


$$V_G = \frac{V_{DD}}{R_1 + R_2} \cdot R_2$$


$$V_{GS} = V_G - V_S$$

$$V_{GS} = V_G - I_D \cdot R_S$$

I_{DSS}
 $V_{GS_{off}}$
 and gives

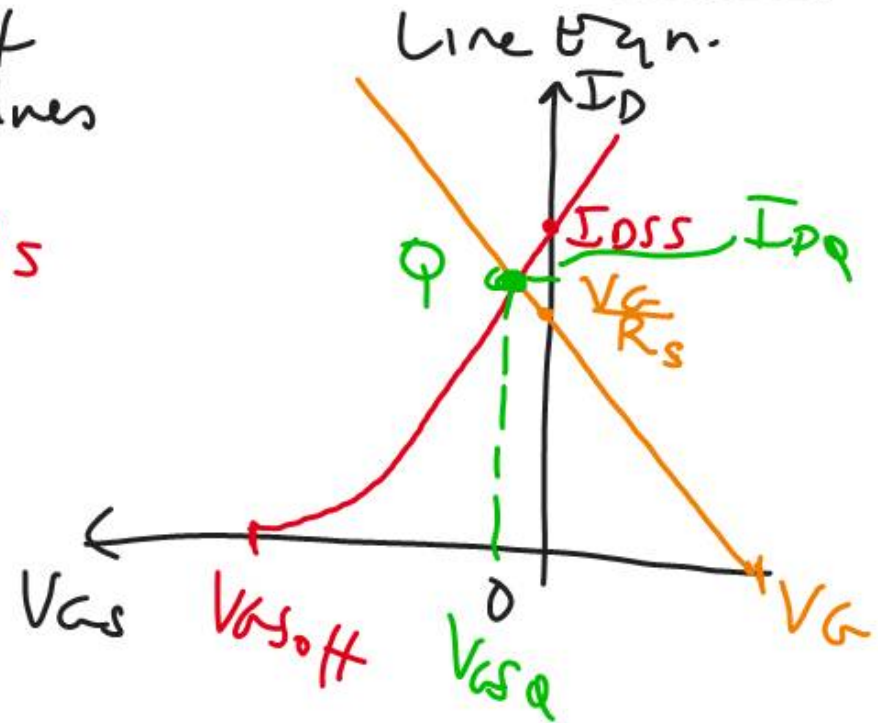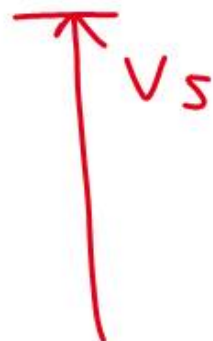

ex

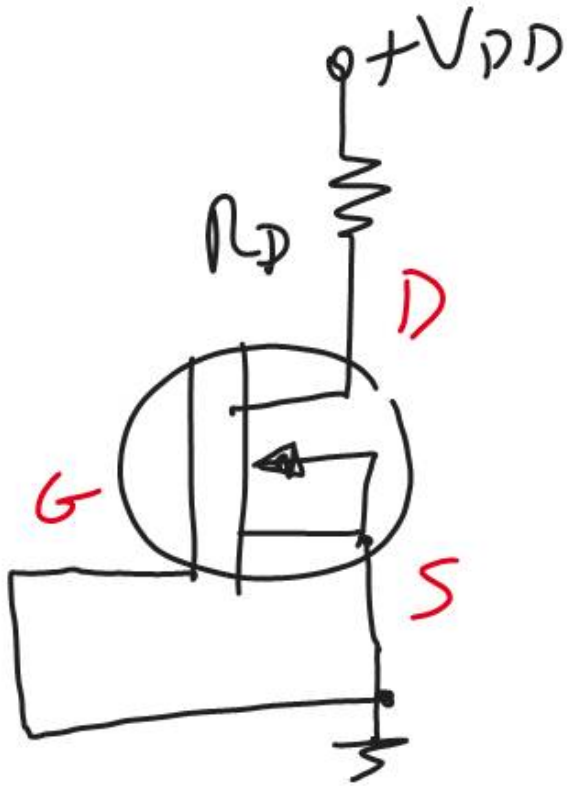


$$V_{GS} = V_G - V_S$$

$$V_{GS} = 0V$$


When $V_{GS} = 0V$

$$I_D = I_{DSS}$$

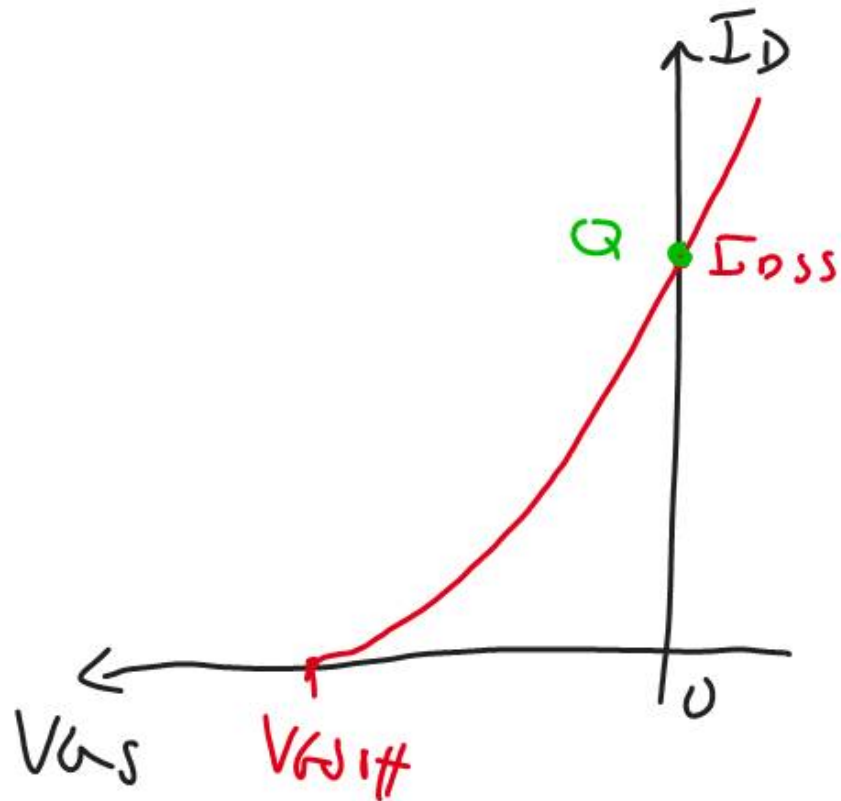

E-MOSFET BIASING

(1) Feedback Biasing

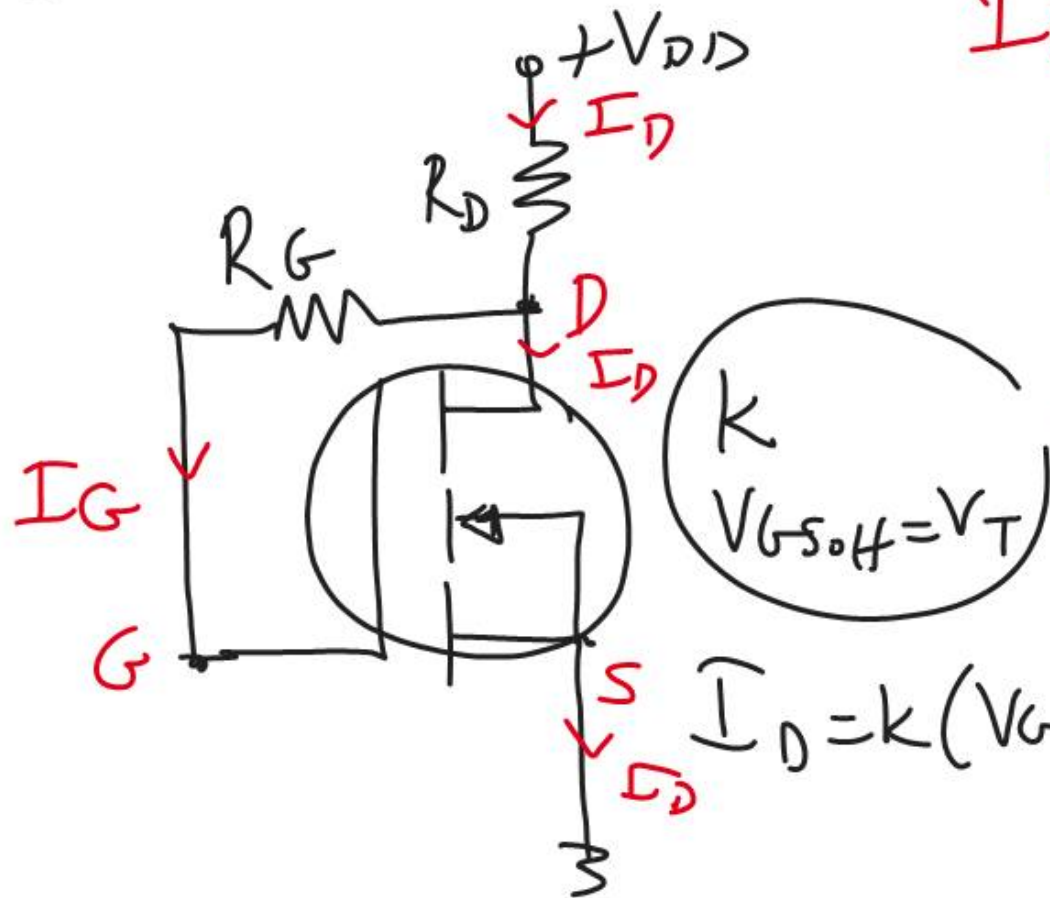

$$I_G = 0 \quad (\text{no gate current})$$

no voltage drop on R_G

$$I_G \cdot R_G = 0$$

$$V_G = V_D$$

$$V_{GS} = V_{DS}$$

output KVL:

$$V_{DD} - I_D R_D - V_{DS} = 0$$


$$V_{DS} = V_{GS}$$

$$\boxed{V_{DD} - I_D R_D - V_{GS} = 0}$$

A line equation between I_D and V_{GS}

given

$$I_D = k(V_{GS} - V_T)^2$$

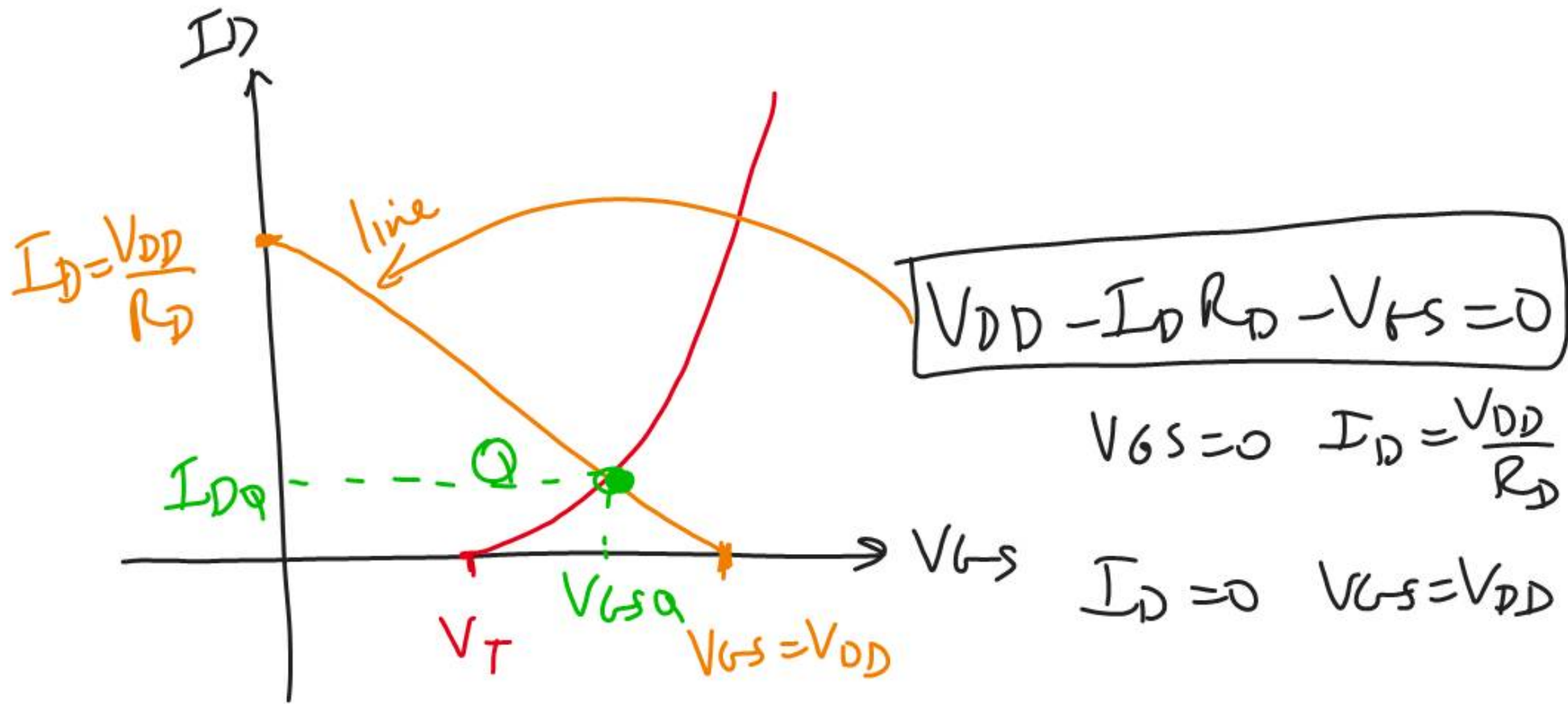


Or use analytical method:

$$I_D = \frac{V_{DD} - V_{GS}}{R_D} \implies I_D = k (V_{GS} - V_T)^2$$

$$\frac{V_{DD} - V_{GS}}{R_D} = k (V_{GS} - V_T)^2$$

$a x^2 + b x + c = 0 \quad x = V_{GS}$

Voltage Divider bias for E-MOSFET

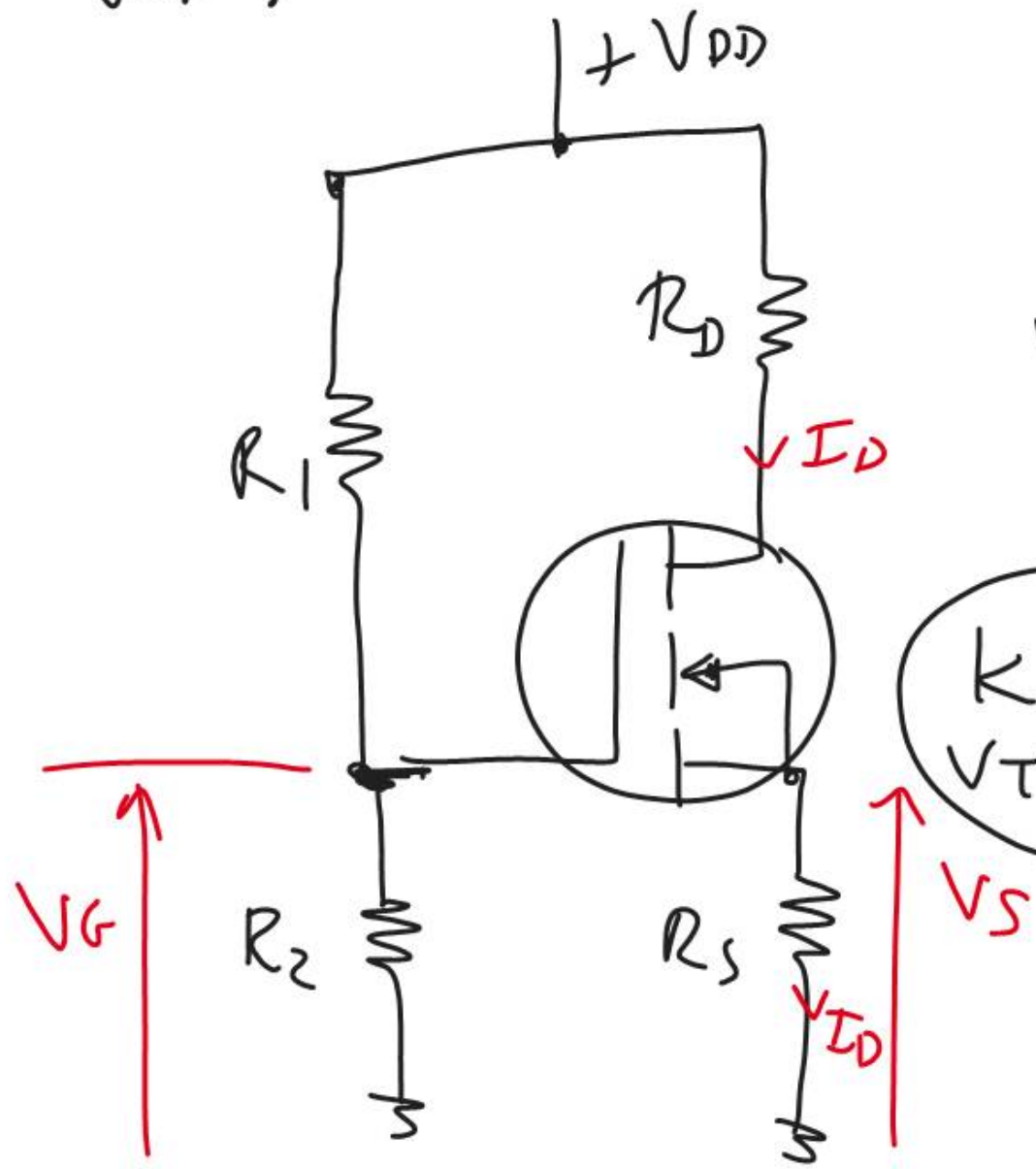

$$V_G = \frac{V_{DD}}{R_1 + R_2} \cdot R_2$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = V_G - I_D R_S$$

Line

K , and V_T are given