
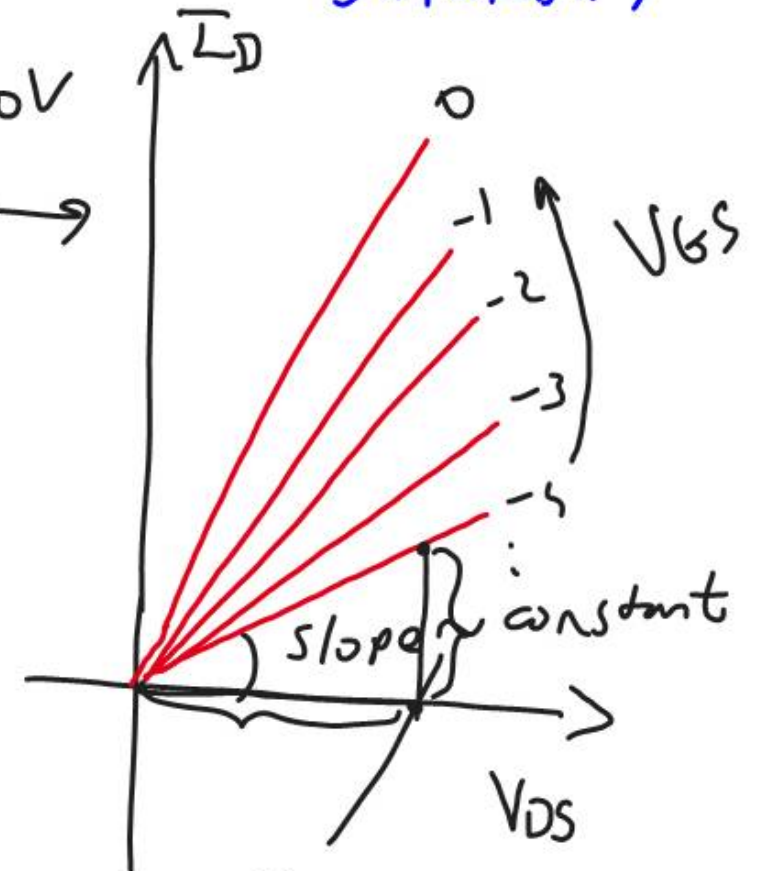


FET as a voltage-controlled resistor

30.04.2011

©

SATURDAY

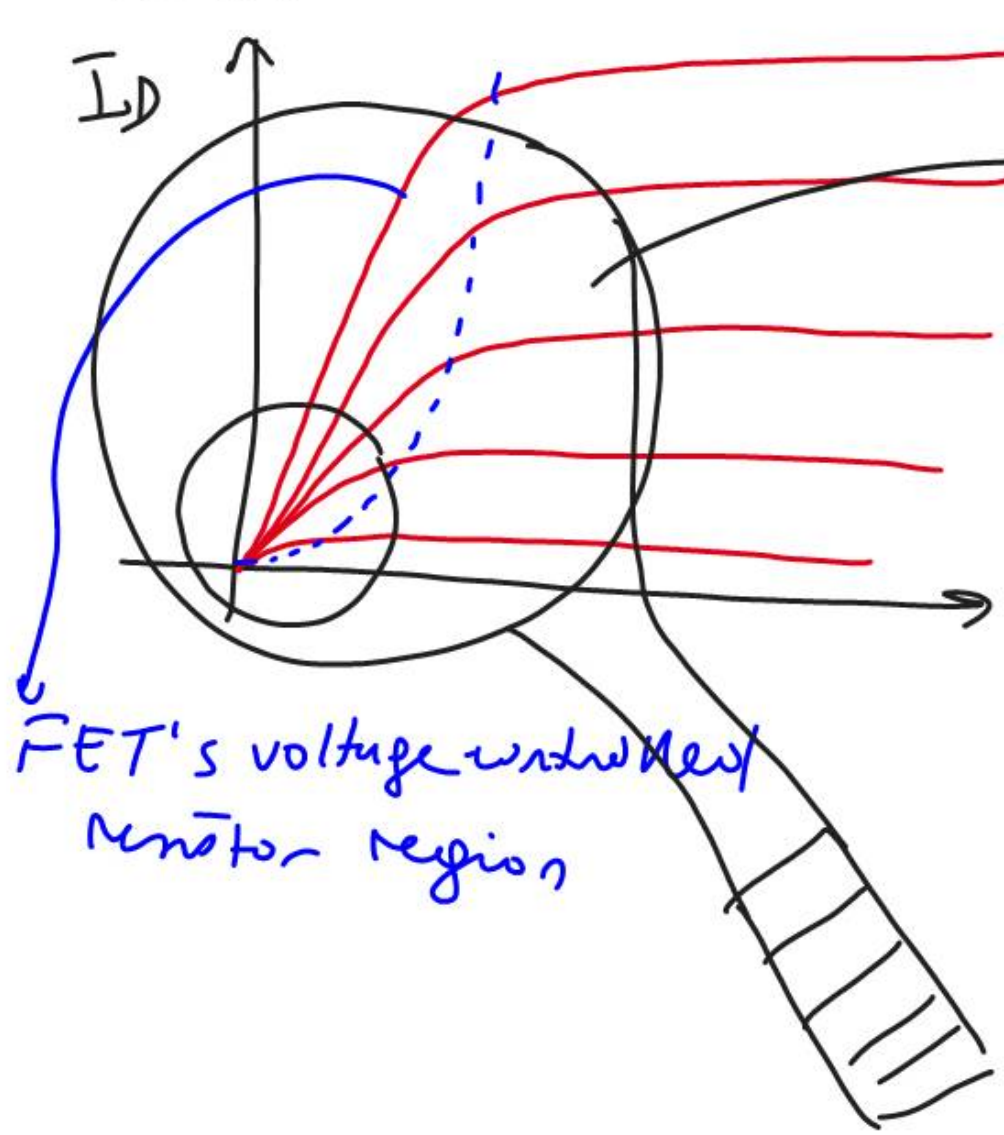


changing $V_{GS} \rightarrow$ changing slope


Slope $\alpha = \frac{\Delta I_D}{\Delta V_{DS}} \equiv \frac{I_D}{V_{DS}}$ constant for each V_{GS}

$$R = \frac{V}{I} \rightarrow \frac{1}{R} = \frac{I}{V}$$

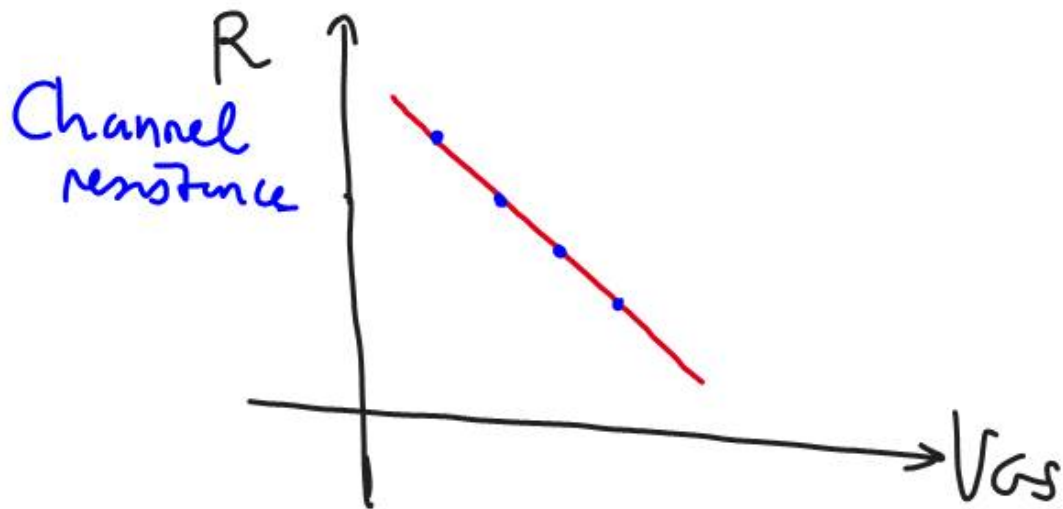
as slope gets higher the channel resistance gets lower:






ex of application

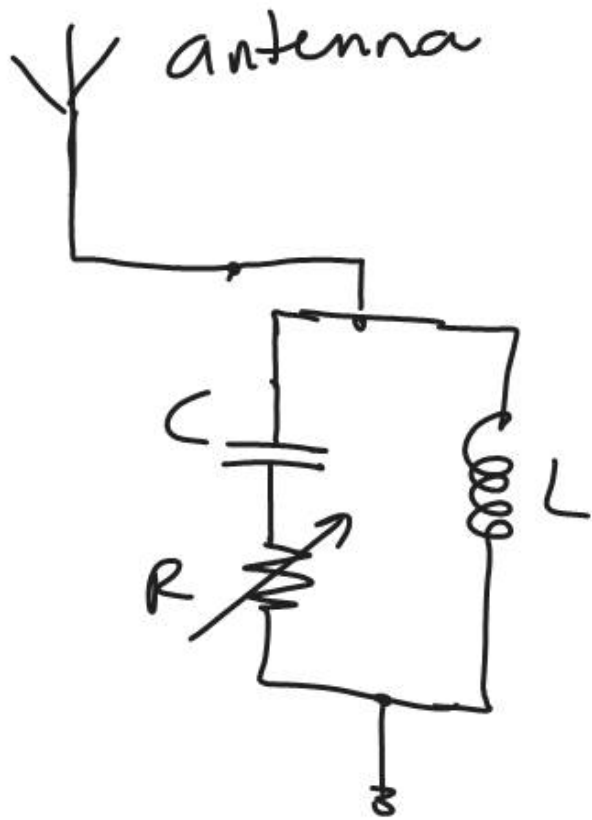

Filter.

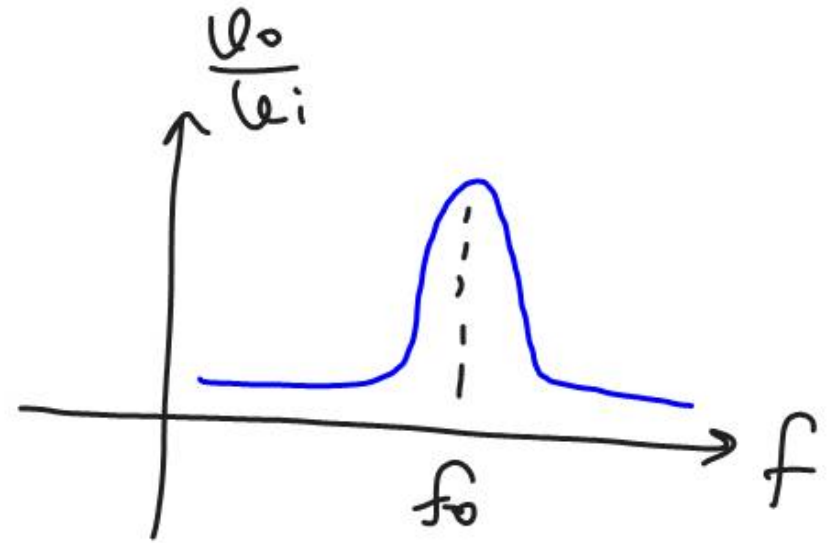

Another application

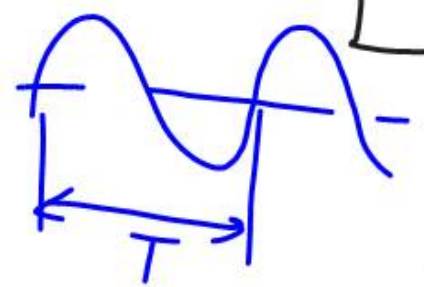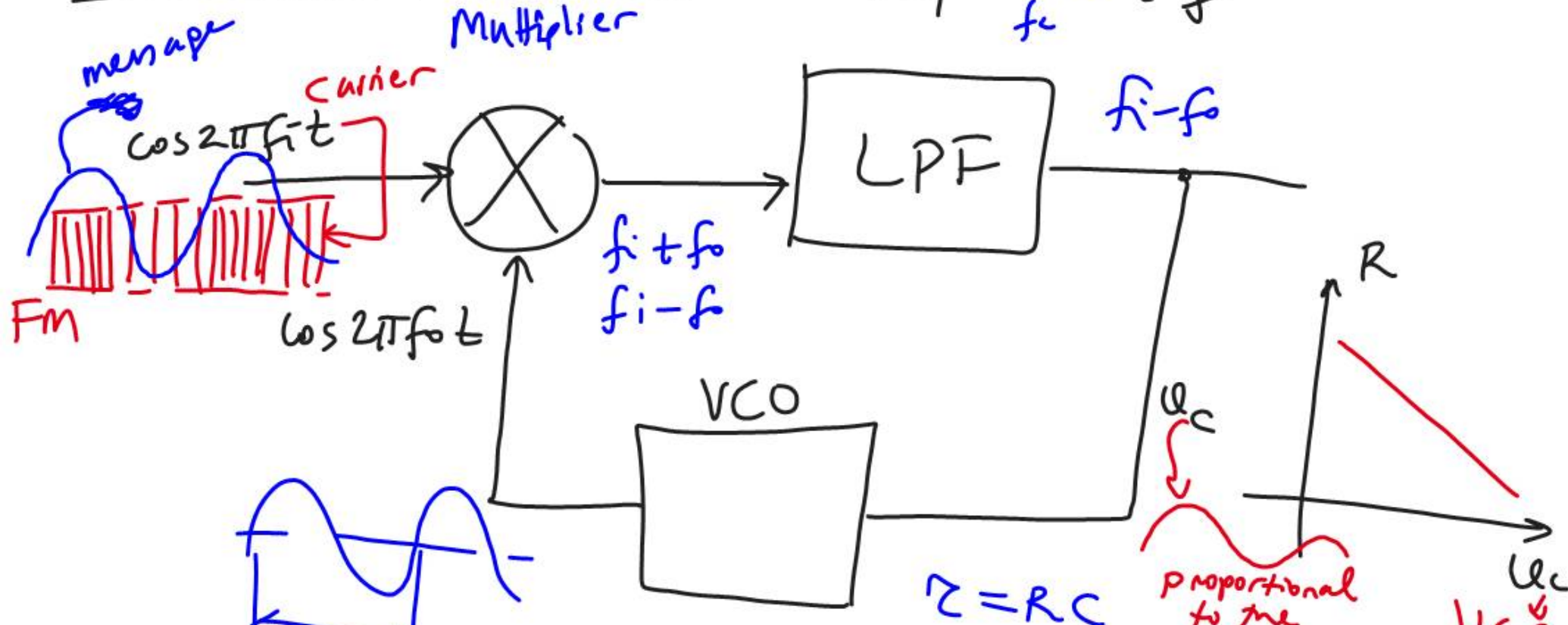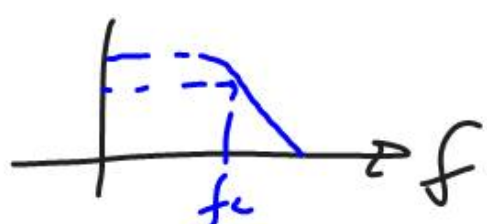

$T \propto RC$



A voltage-controlled oscillator

$V_c =$ control voltage


$f_o =$ output frequency controlled by V_c

proportional to the message signal (FM demodulation)

Phase Locked Loop (PLL)

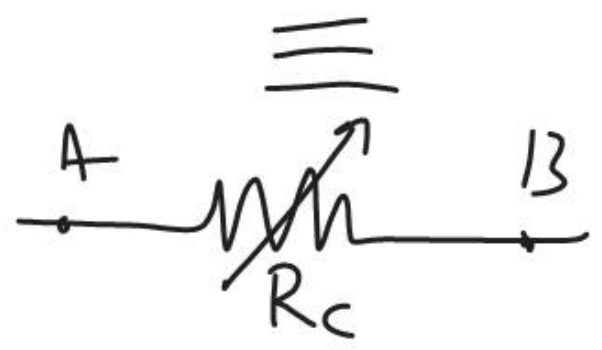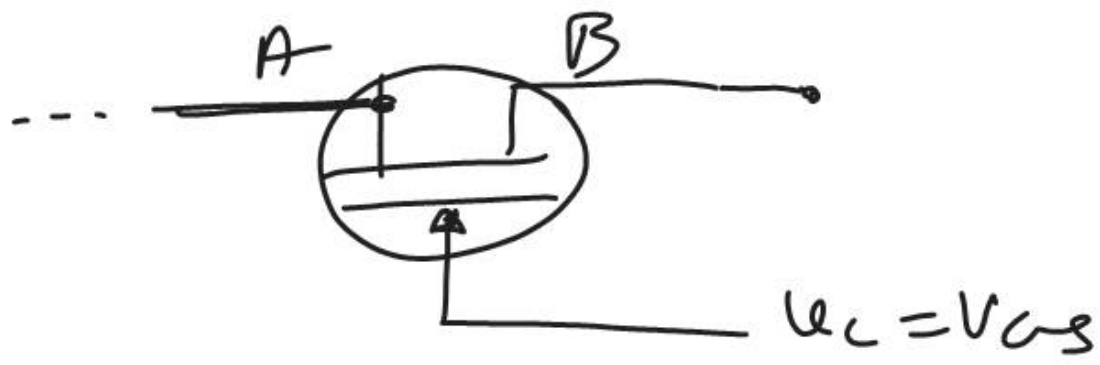

ex

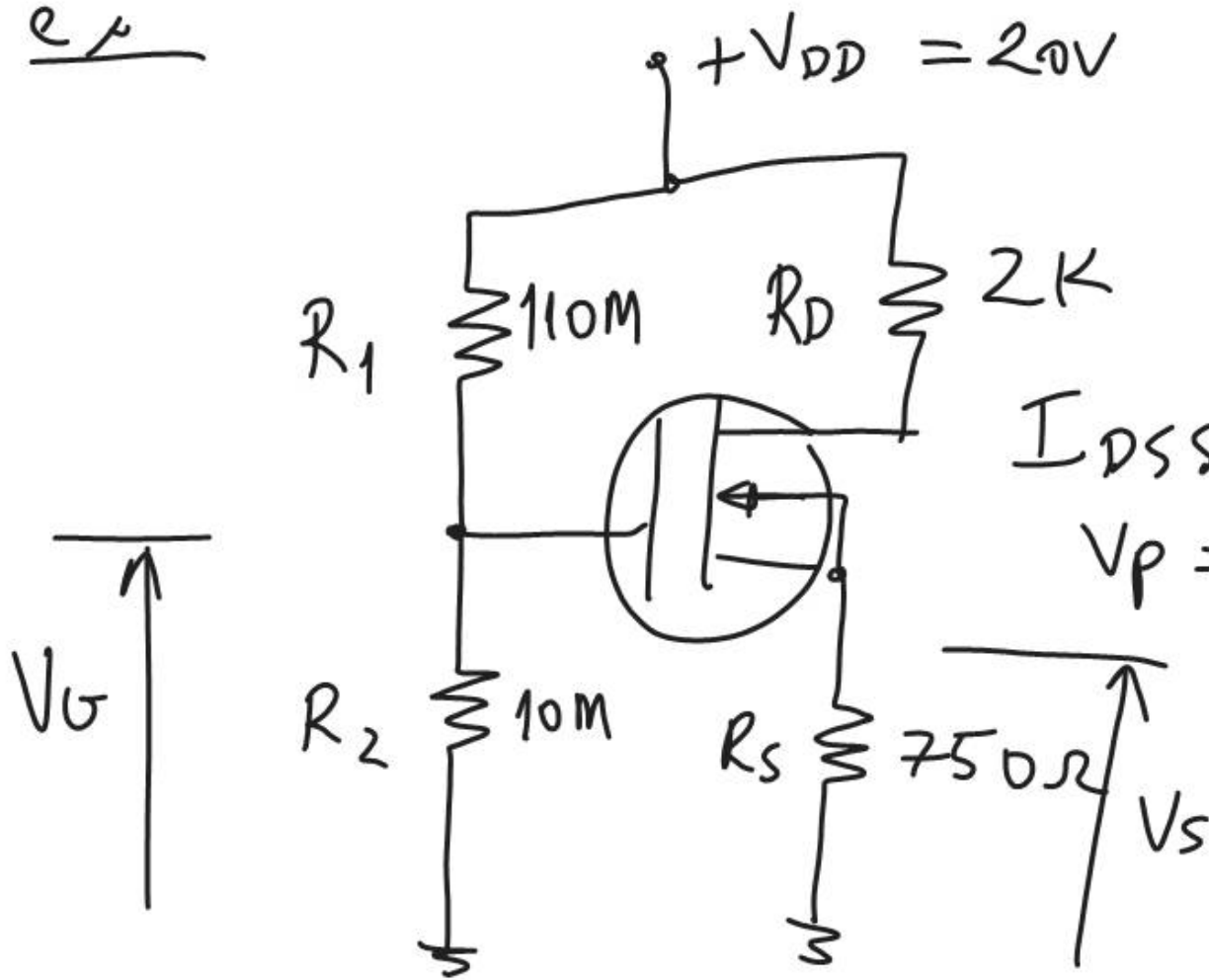

$$I_{DSS} = 6\text{mA}$$

$$V_P = V_{GSoff} = -3\text{V}$$


$$V_G = \frac{V_{DD} \cdot R_2}{R_1 + R_2}$$

$$V_G = \frac{20}{120 \times 10^6} \times 10 \times 10^6$$

$$V_G = 1.7\text{V}$$

Determine the quiescent point (Φ)

$$V_S = I_D \cdot R_S = 750 I_D$$

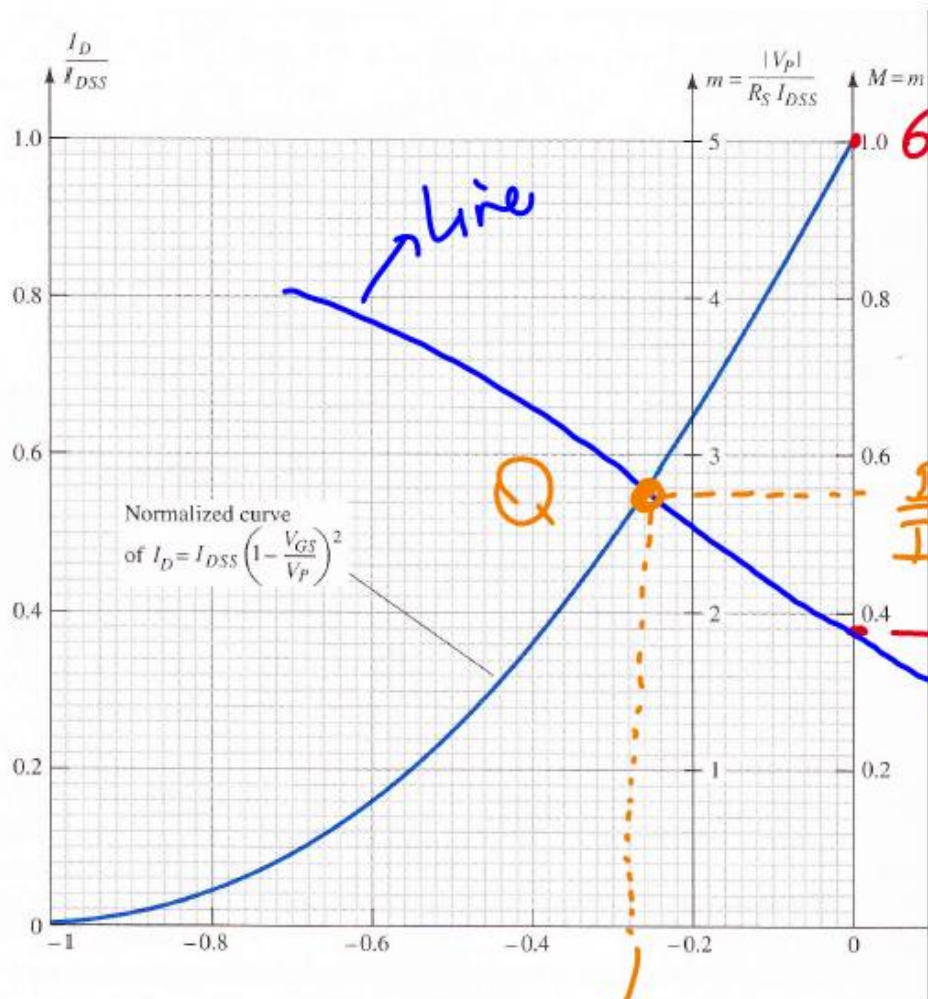

$$V_{GS} = V_G - V_S$$

$$V_{GS} = 1.7 - I_D \cdot 750$$

Line eqn.

$$I_D = \frac{1.7}{750} = 2.3 \text{ mA}$$

$$\frac{2.3 \text{ mA}}{6 \text{ mA}} = 0.38$$

$$I_D = 0 \quad V_{GS} = 1.7$$

$$\frac{1.7}{3.0} = 0.57$$

$$V_P = -3 \text{ V}$$

$$\frac{V_{GS}}{|V_P|} = \frac{-0.28}{3}$$

$$I_{DQ} = 0.56 \times I_{DSS} = 0.56 \times 6 \text{ mA} = 3.4 \text{ mA}$$

$$V_{GSQ} = 0.28 \times |V_P| = -0.28 \times 3 = -0.84 \text{ V}$$

$$I_{DQ} = 3.4 \text{ mA}$$

$$V_{GSQ} = -0.84 \text{ V}$$

$$V_{DSQ} \approx 14 \text{ V}$$

Q point


Output KVL

$$V_{DD} - I_D \cdot (R_D + R_S) - V_{DS} = 0$$


$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{DS} = 20 - 3.4 \times 10^{-3} (1 + 0.75) \times 10^3$$
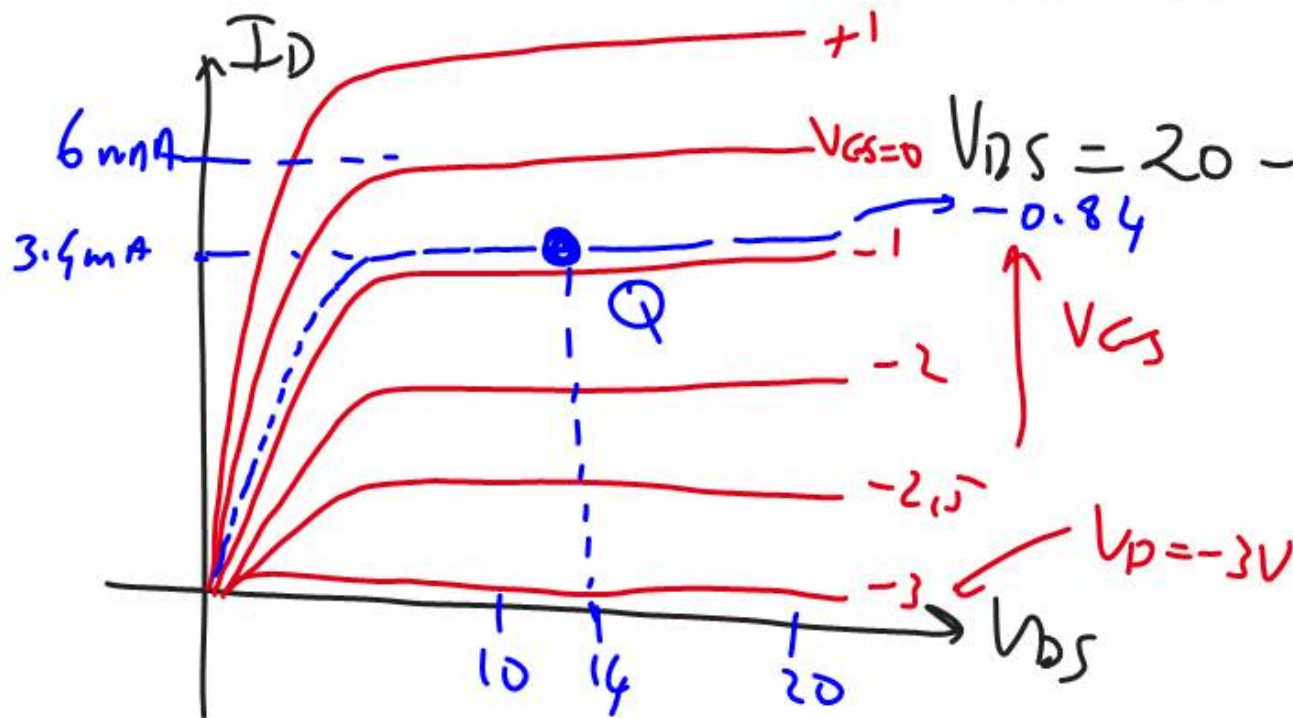
$$V_{DS} = 20 - 5.95 \approx \underline{14 \text{ V}}$$



ex:

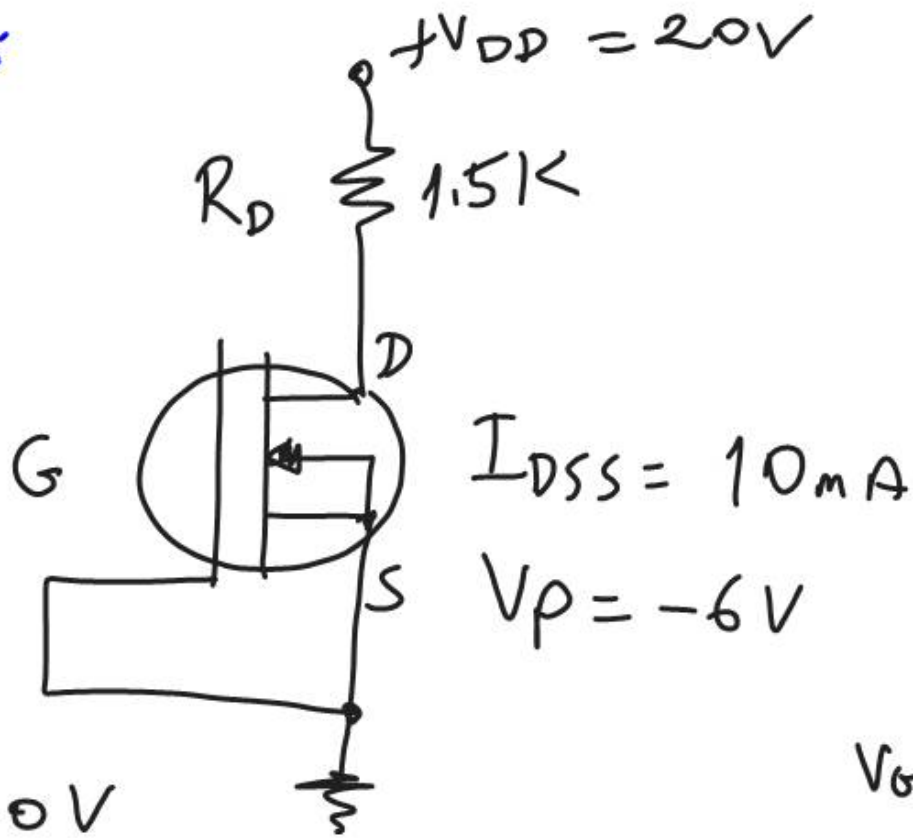


$$V_G = 0V$$

$$V_S = 0V$$

$$V_{GS} = 0 - 0 = 0$$

Determine Q

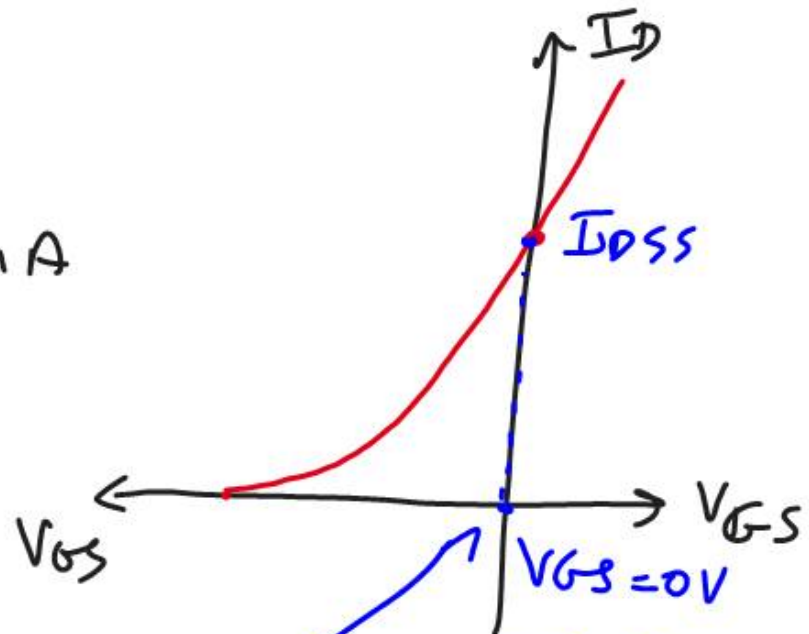

$$\Rightarrow I_D = I_{DSS}$$

Q

$$I_{DQ} = 10mA$$

$$V_{GSQ} = 0V$$

$$V_{DSQ} = 5V$$


$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS} = 20 - 10 \times 10^{-3} \times 1.5 \times 10^3$$

$$V_{DS} = 5V$$

ex

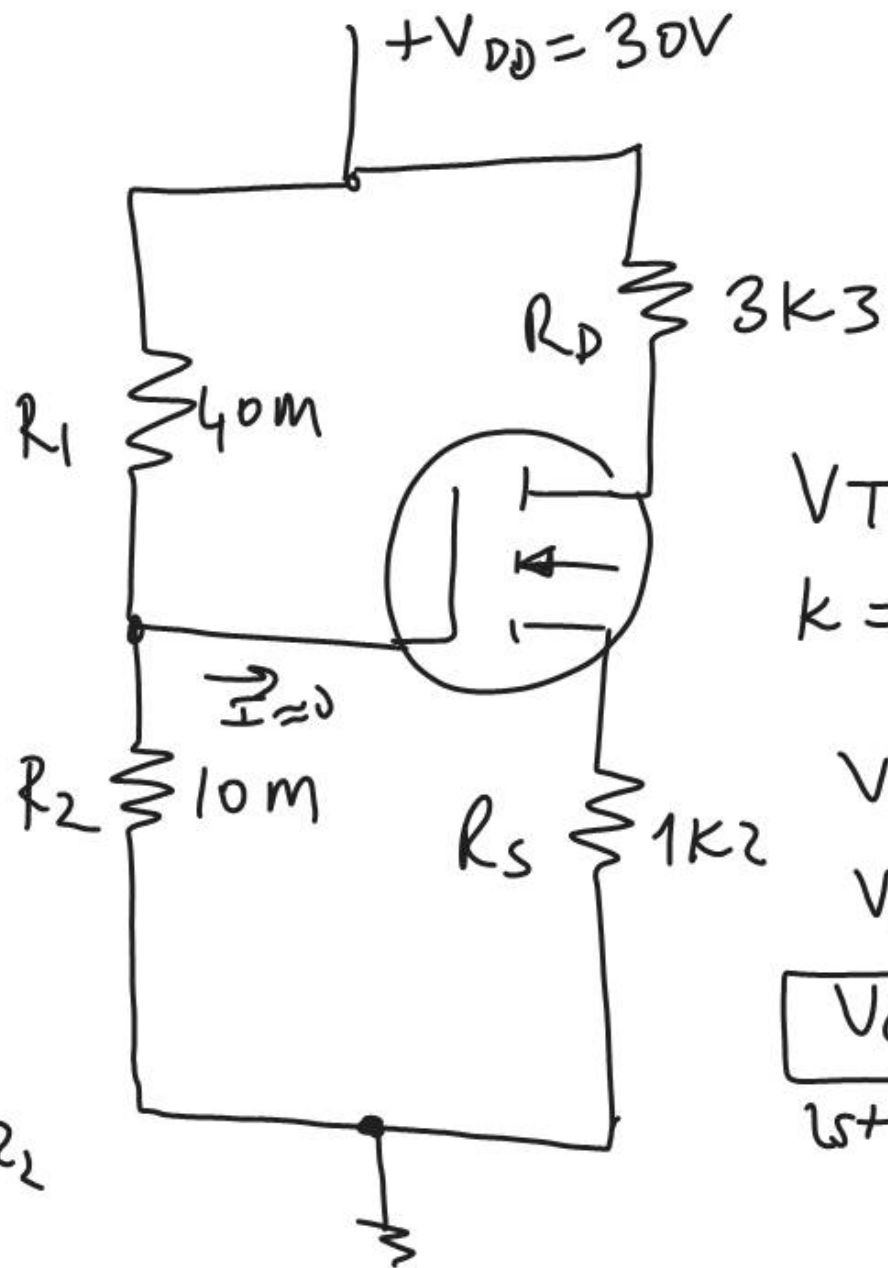

$$V_T = 3\text{V}$$

$$k = 0.4 \times 10^{-3} \text{ A/V}^2$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = 6 - I_D \times 1.2 \times 10^3$$

$V_{GS} = 6 - 1200 I_D$

 Line
1st eqn.



$$V_G = \frac{V_{DD} \cdot R_2}{R_1 + R_2}$$

$$V_G = \frac{30}{50 \times 10^6} \times 10 \times 10^6 = \underline{6\text{V}}$$

2nd Eqn: $I_D = k(V_{GS} - V_T)^2$

$$I_D = 0.4 \times 10^{-3} (V_{GS} - 3)^2$$

From the first Eqn:

$$V_{GS} = 6 - 1200 I_D$$

$$I_D = 0.4 \times 10^{-3} (6 - 1200 I_D - 3)^2$$

$$I_D = 0.4 \times 10^{-3} (3 - 1200 I_D)^2$$

→ The roots
can be calculated
and I_{DQ} , V_{GSQ}
are obtained.


$$ax^2 + bx + c = 0$$

where $x = I_D$

$$\text{and } V_{DD} = I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

SMALL SIGNAL AMPLIFICATION

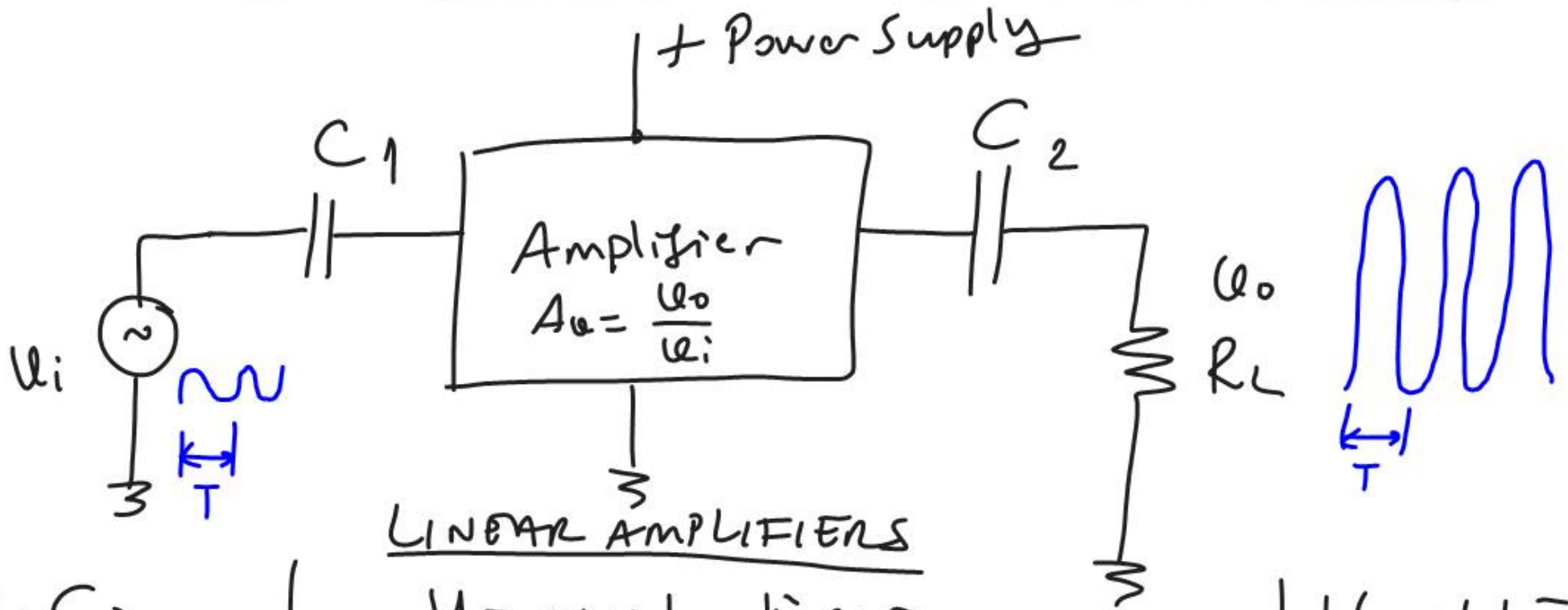

LINEAR AMPLIFIERS

$$y = ax + b \text{ linear}$$

$$\rightarrow u_o = A_u \cdot u_i + b \rightarrow \text{a DC voltage}$$

if $A_u > 0 \rightarrow$ zero phase shift

if $A_u < 0 \rightarrow 180^\circ$ phase shift

C_1, C_2
are blocking
capacitors.
They separate
the stages in
terms of DC

If not linear,
and only
power amplification is the
concern, then
POWER AMPLIFIERS
are
used