

$$I_C = \beta I_B \quad \text{①}$$

VOLTAGE DIVIDER BIAS 05.05.2011

$$I_D = \frac{I_C}{\beta} = \frac{4.25 \text{ mA}}{120}$$

$$I = \frac{20 - (-20\text{V})}{8.2\text{k} + 2.2\text{k}}$$

$$I = 3.85 \text{ mA}$$

$$V_B = 20 - I \cdot 8.2\text{k} = -11.5\text{V}$$


$$V_E = V_B - 0.7\text{V} = -12.23\text{V}$$

$$I_E = \frac{V_E - (-20\text{V})}{1.8\text{k}} = 4.25 \text{ mA}$$

$$I_E \approx I_C$$

$$V_C = V_{CC} - I_C \cdot 2.7\text{k}$$

$$V_{BE} = 0.7\text{V}$$

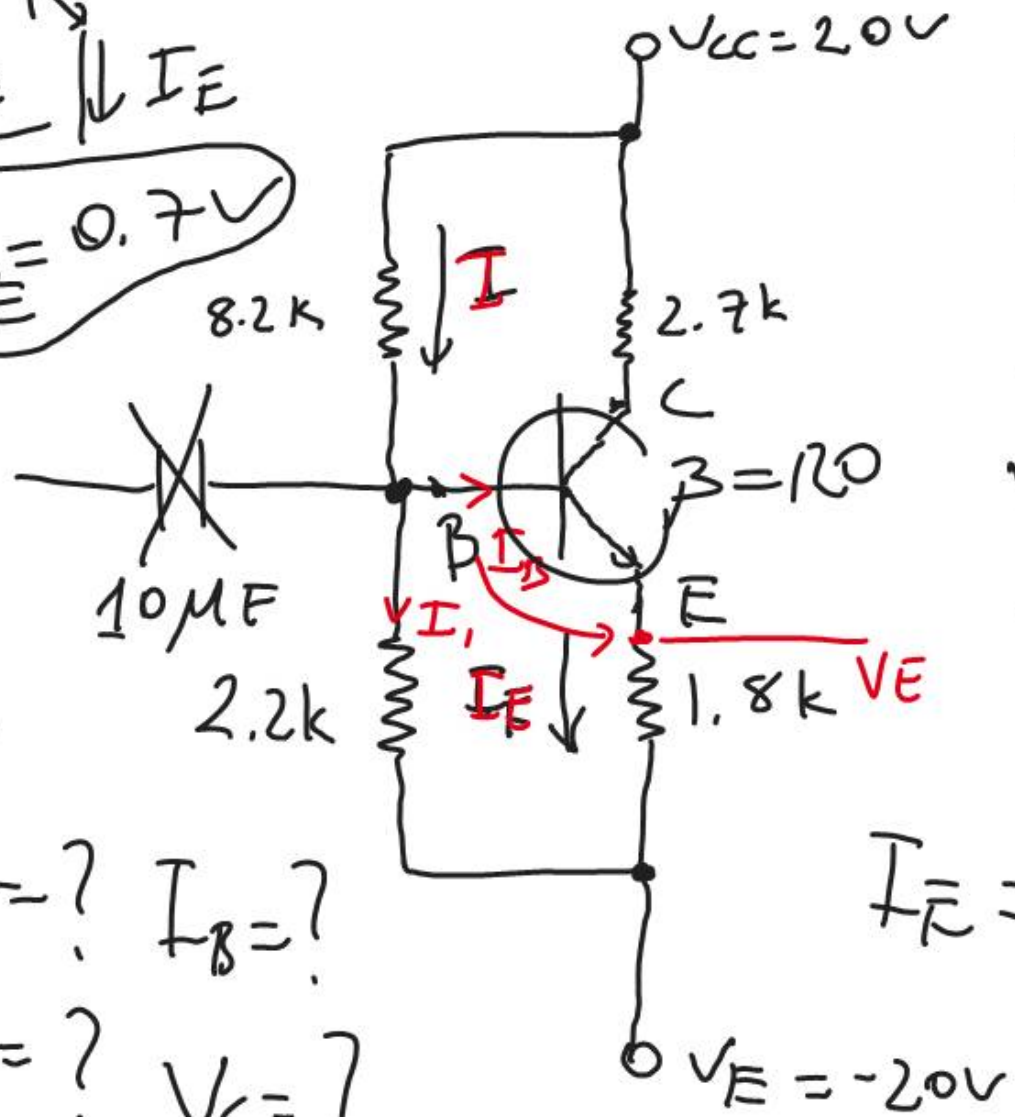


- ✓  $V_B = ?$   $I_B = ?$
- ✓  $I = ?$   $V_C = ?$
- $V_{IC} = ?$   $V$




①  $V_B - V_E = 0.7V$     ③  $I_C \approx I_E$

②  $I_C = \beta I_B$

A common collector Config

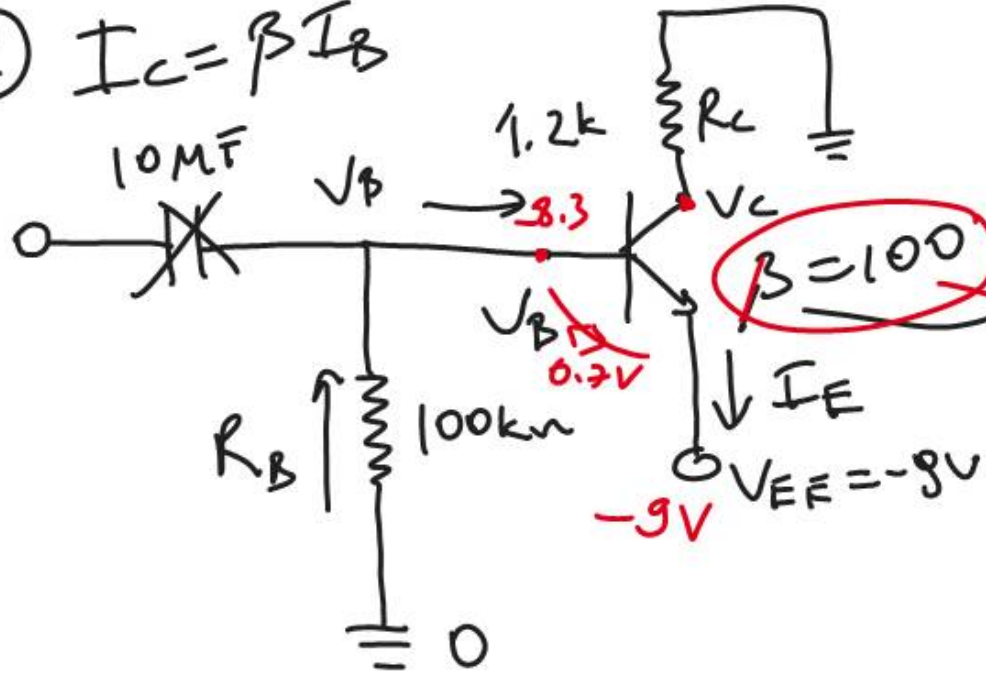

$\beta \gg 1$   
 $\equiv$

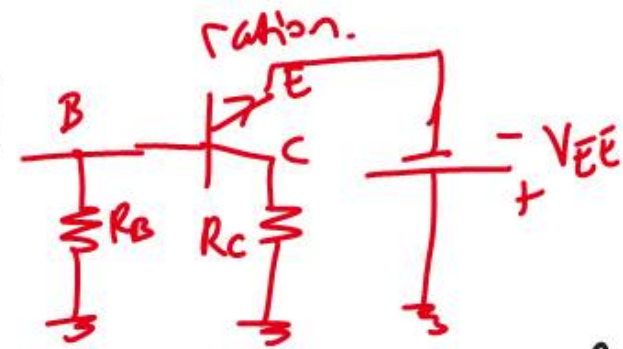

$$I_B = \frac{0 - V_B}{100k} = \frac{8.3}{\frac{100k}{10^5}} = 83 \mu A$$

- $V_B = ?$
- $V_{I_B} = ?$
- $V_{I_C} = ?$
- $V_C = ?$

$V_B - V_E = 0.7V$   
 $V_B - (-9V) = 0.7V$   
 $V_B = -8.3V$

$I_C = 83 \times 10^{-6} \times 10 = 8.3 mA$

$\frac{0 - V_C}{1.2k} = 8.3 mA$

INPUT KVL:

$$20V - I_E \times 4.2 \times 10^3 - I_B \times 680 \times 10^3 - V_{BE} = 0$$

$$I_E = (\beta + 1) I_B$$

$$I \approx I_C$$

$$\frac{20 - V_C}{4.7k} = I_B (\beta)$$

$$= \frac{V_C - 0.7}{680k} \times 120$$

$$I_C = \frac{20 - V_C}{4.7k}$$

$$I_C = (\beta + 1) I_B$$

$$\times 20 - I_E \cdot 4.2 \times 10^3 - V_{CE} = 0 \quad \text{OUTPUT KVL}$$

$$I_{CE}$$

$$I = I_B + I_C \quad I_B = ?$$

$$I = I_E \quad V_C = ?$$


$$V_E = ?$$

$$V_E = 0V$$

$$V_{CE} = ?$$


$$\beta = 120$$

$$I = I_E \quad \beta \gg 1$$

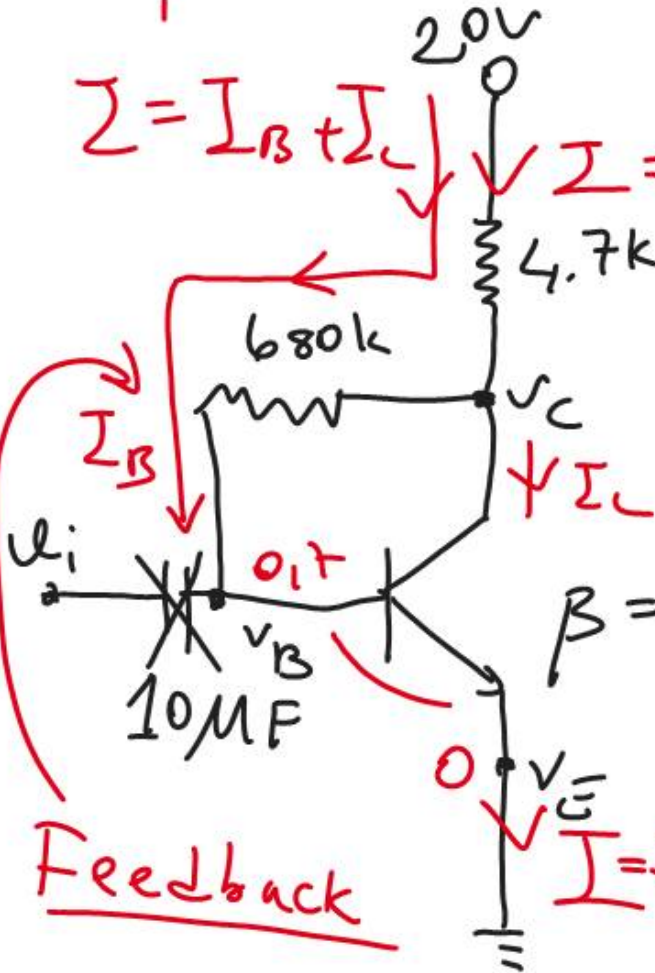

Feedback

# DC Analysis

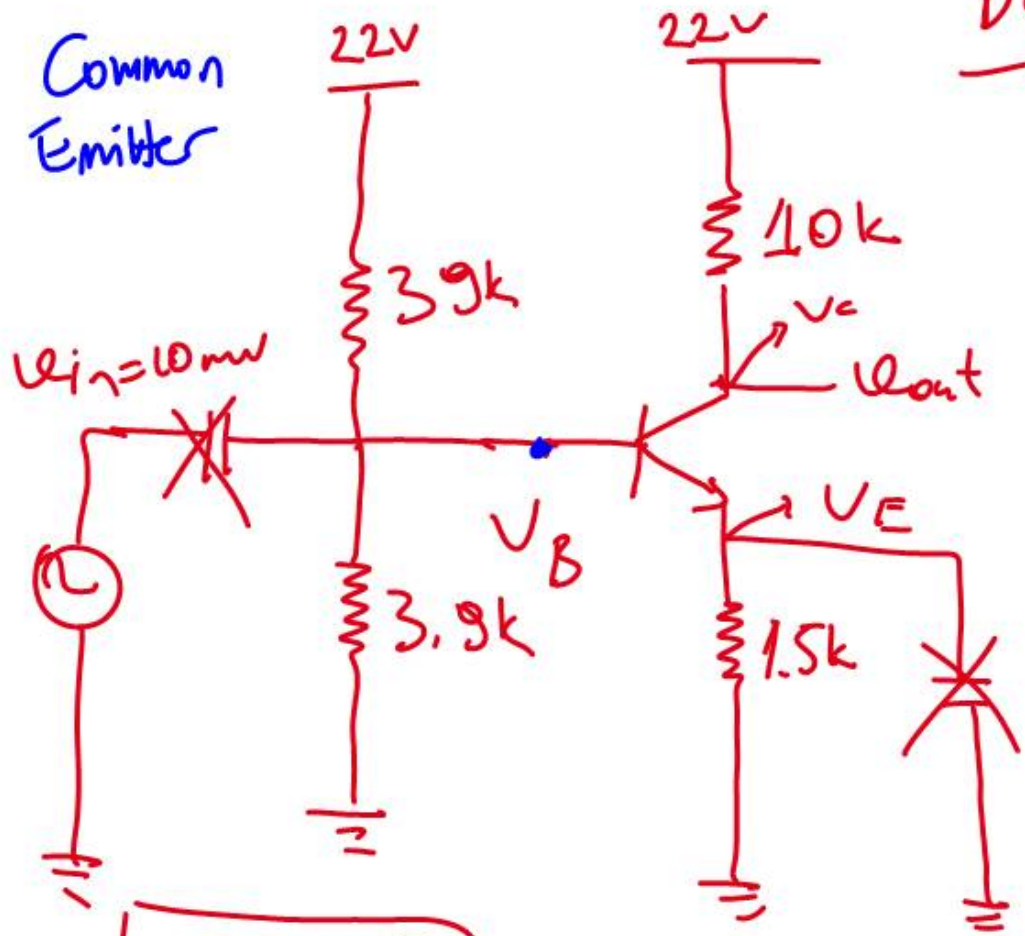

$$V_B = \frac{3.9\text{k}}{3.9\text{k} + 3.9\text{k}} \times 22\text{V}$$

$$V_E = V_B - 0.7\text{V}$$


$$I_E = \frac{V_E}{1.5\text{k}}$$

$$I_E \approx I_C$$

$$V_C = 22 - I_C \cdot 10\text{k}$$

$$V_{CE} = V_C - V_E$$

# EMITTER RESISTOR FEEDBACK

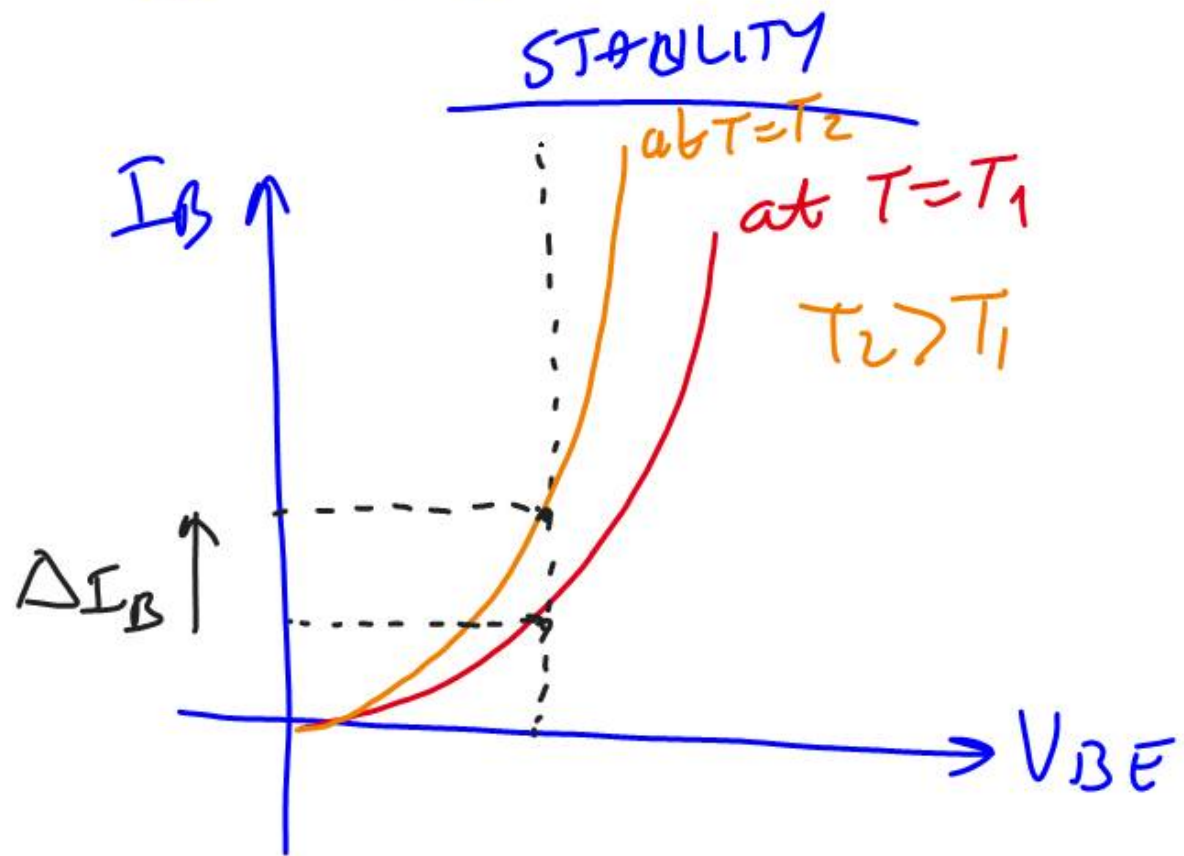

increasing temperature increases  $I_B$  at the same  $V_{BE}$ .

$$I_C = \beta \cdot I_B$$


So  $I_C$  increases

Increasing  $I_C$  heats up the transistor,  
 in Heated transistor ( $T \uparrow$ )  $I_B$  increases more, so does  $I_C$   
 Increasing  $I_C$  heats up transistor more  
**Thermal Runaway occurs and transistor is damaged.**

However, an emitter resistor  $R_E$  prevents the

THERMAL RUNAWAY.

→ Stability problem

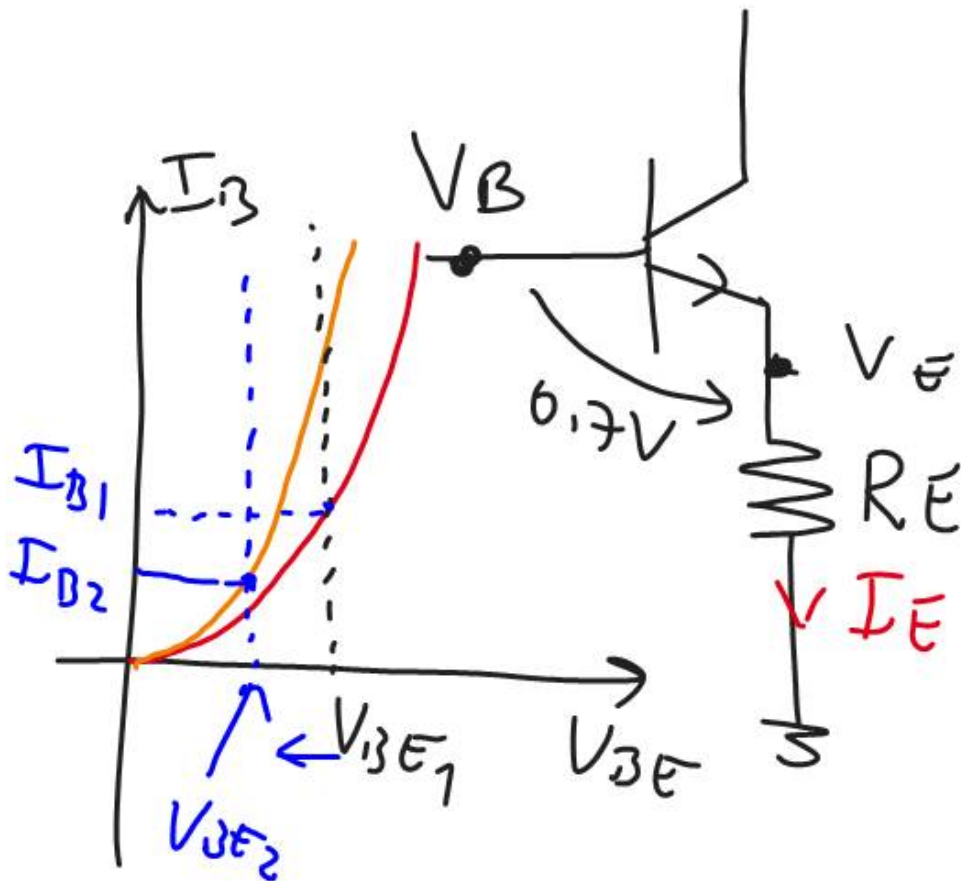

$$V_E = I_E \cdot R_E$$

$$V_E = V_B - 0.7V$$

↑  
constant.

as  $I_B \uparrow$ , and  $I_C \uparrow$ ,  $I_E \uparrow$

then  $V_E = I_E \cdot R_E \uparrow$

$V_B - V_E = V_{BE}$  decreases

↓  $V_{BE}$   $\uparrow$  and  $I_B$  decreases.

NO THERMAL RUNAWAY!