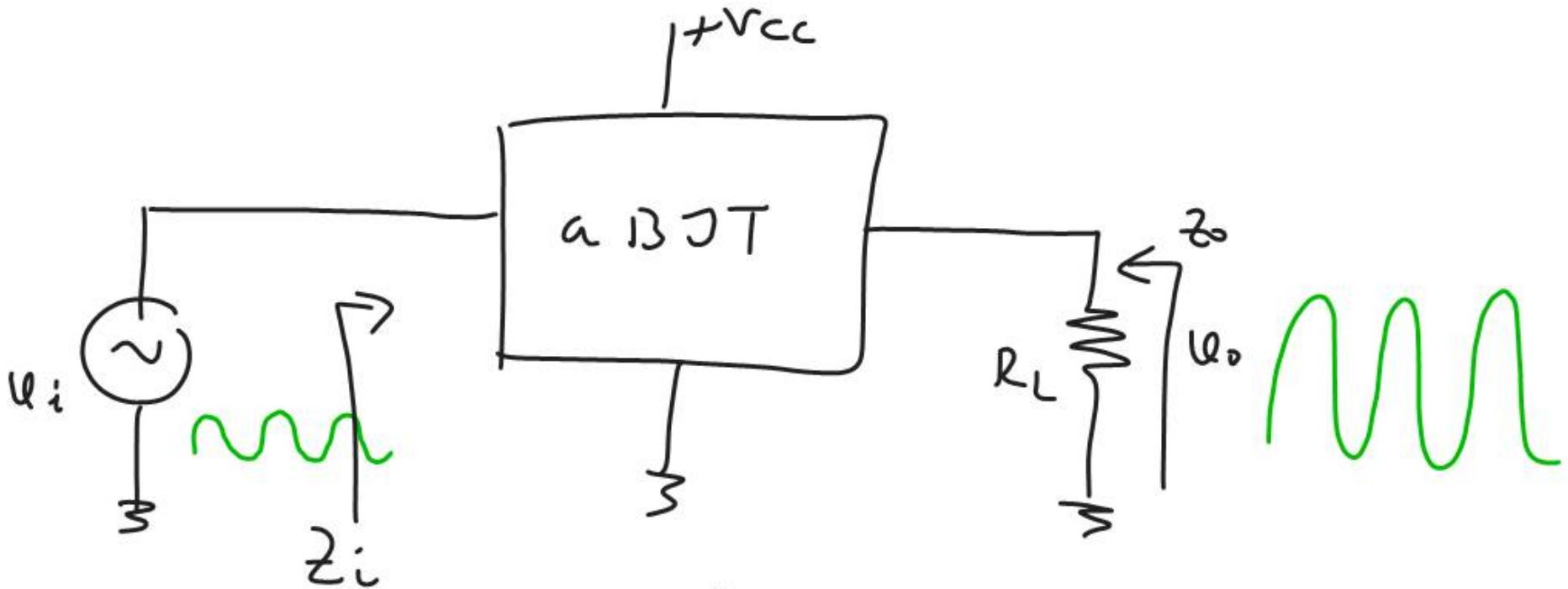


# BJT (BIPOLAR JUNCTION TRANSISTORS) 16.05.2011

©


## LINEAR AMPLIFIERS



$$u_o = A_u \cdot u_i$$

$$A_u = \frac{u_o}{u_i} \quad \text{Voltage gain}$$

# A common-emitter BJT amplifier:

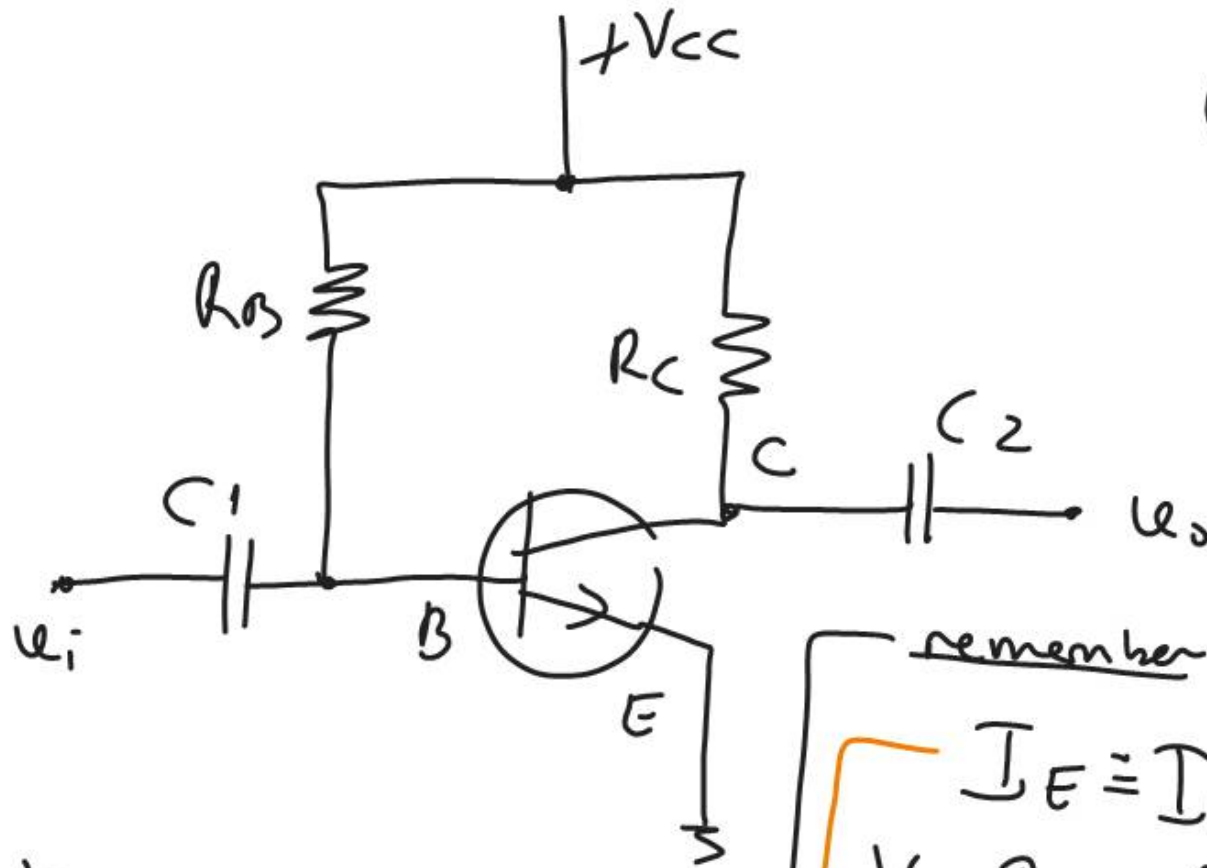

① DC analysis is to find the  $r_e$  (Base emitter dynamic resistance)

$$r_e = \left. \frac{dV_{BE}}{dI_E} \right|_{V_{CE} = \text{const}}$$

remember:

$$I_E \approx I_0 \cdot e^{V_{BE}/V_T}$$

$$V_T = \text{Thermal voltage} = \frac{kT}{q} \approx 26 \text{ mV at } 300^\circ \text{K}$$

$$\frac{dI_E}{dV_{BE}} = \frac{I_0}{V_T} \cdot e^{V_{BE}/V_T} = \frac{I_E}{V_T}$$


$$\frac{dI_E}{dV_{BE}} = \frac{I_E}{V_T}$$

$$r_e = \frac{dV_{BE}}{dI_E} = \frac{V_T}{I_E}$$

Dyn objective is to find  $I_E$
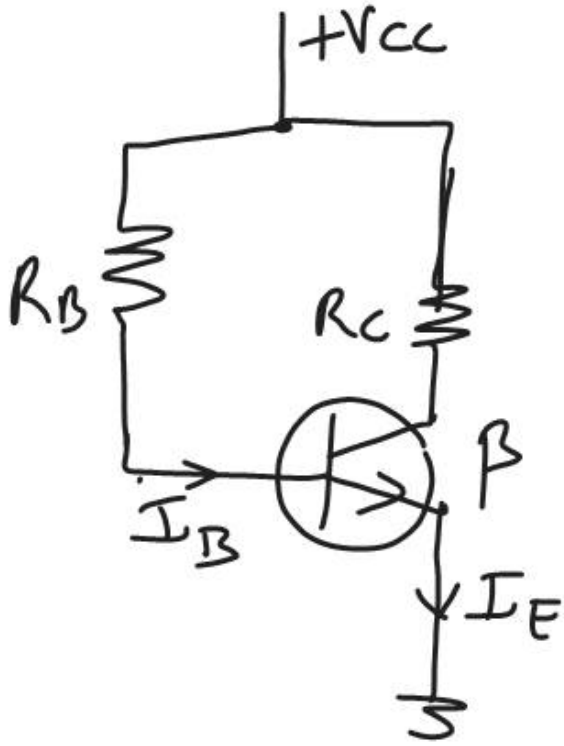
## DC analysis

Bypass capacitors, coupling capacitors  $\rightarrow$  OPEN



Input KVL:

$$V_{CC} - I_B R_B - V_{BE} = 0$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_E = (\beta + 1) I_B \approx \beta \cdot I_B$$


$$r_e = \frac{V_T}{I_E} \quad \text{so } r_e \text{ is found.}$$
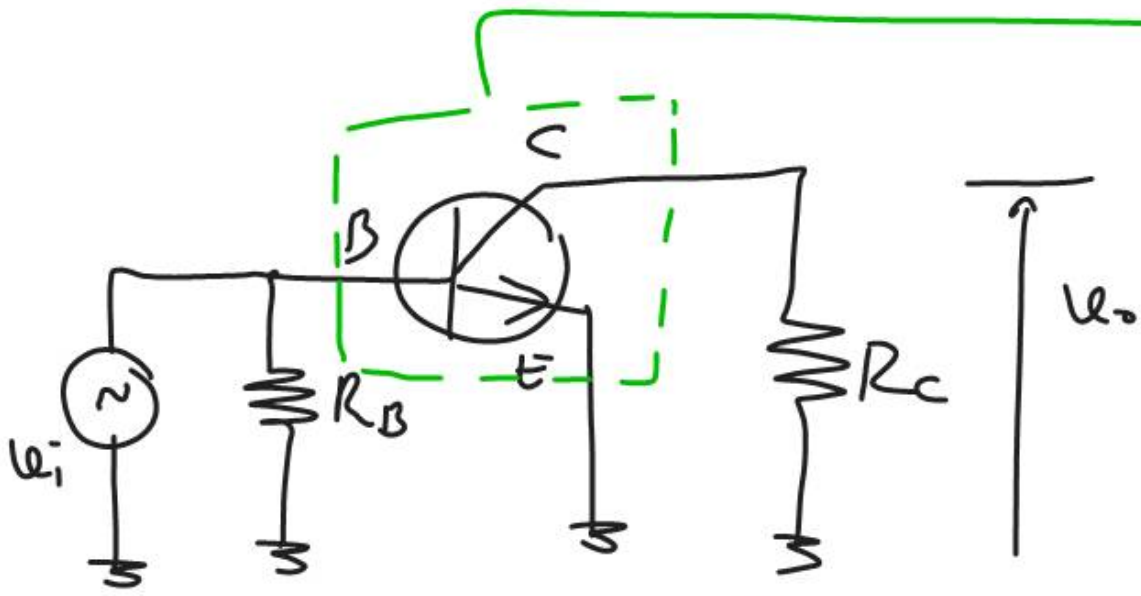
## ② AC Analysis

Coupling, bypass capacitors  $\rightarrow$  SHORT CIRCUIT  
 Short circuit the DC power supply to the ground.



Replace with ac equivalent

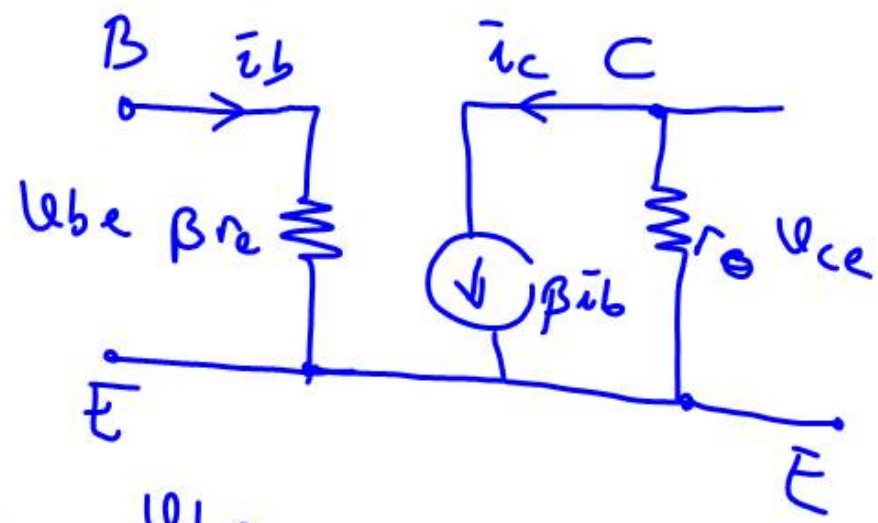


$$h_{ie} = h_{fe} r_e$$

$$h_{fe} \approx \beta$$

HYBRID  
 PARAMETERS

$$\frac{v_{be}}{i_b} = \beta r_e$$

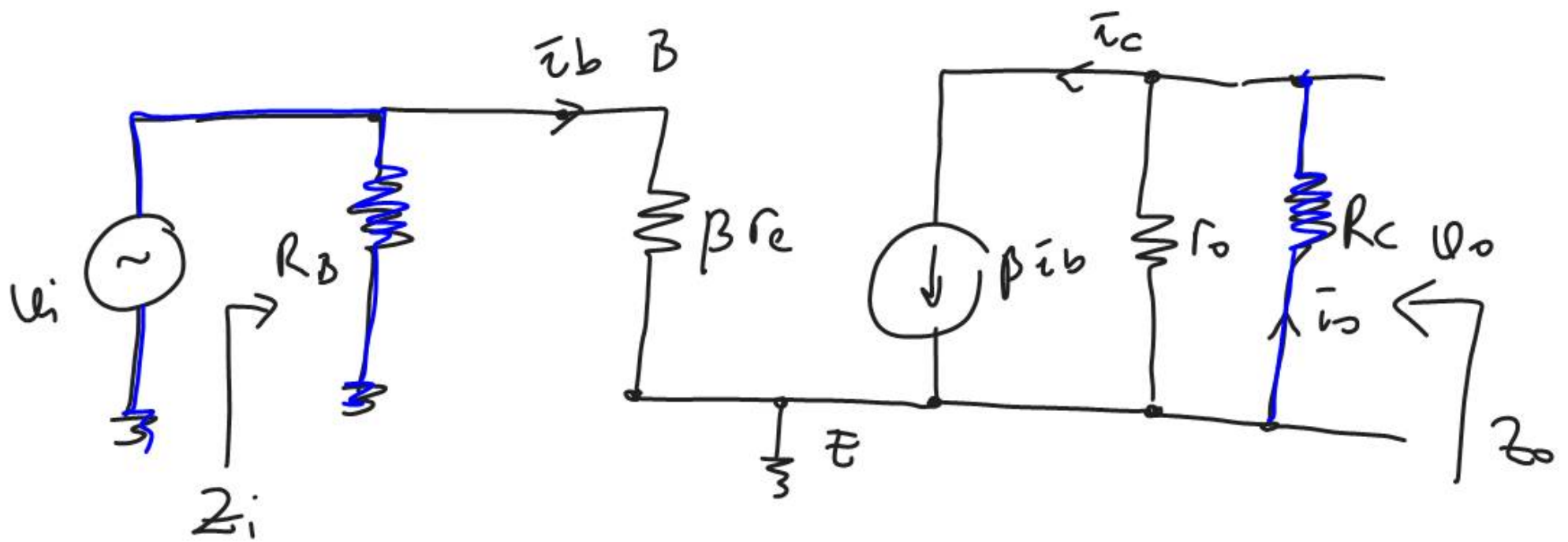

$$Z_i = R_B \parallel \beta r_e$$

$$Z_o \cong r_o \parallel R_C ; \text{ if } r_o \gg 10 R_C \Rightarrow Z_o \cong R_C$$

$$\left. \begin{array}{l} u_o = -i_o \cdot R_C \\ \text{if } r_o \gg R_C \Rightarrow i_o \approx i_c \end{array} \right\} \Rightarrow u_o \approx -i_c \cdot R_C \left. \begin{array}{l} \\ i_c = \beta i_b \end{array} \right\} \Rightarrow \begin{array}{l} u_o = -\beta i_b \cdot R_C \\ u_i = i_b \cdot \beta \cdot r_e \\ i_b = \frac{u_i}{\beta r_e} \end{array}$$

$$V_o = -\beta \bar{v}_b \cdot R_c$$

$$\bar{v}_b = \frac{v_i}{\beta r_e}$$

$$V_o = -\cancel{\beta} \cdot \frac{v_i}{\cancel{\beta} r_e} \cdot R_c$$

$$V_o = -\frac{R_c}{r_e} \cdot v_i$$

$$A_v = \frac{V_o}{v_i} = -\frac{R_c}{r_e}$$

Voltage  
gain

Typical values:

$$R_c = 3 \text{ k}\Omega$$

$$r_e = 5 \Omega$$

$$A_v = -\frac{3 \times 10^3}{5} = -\frac{3000}{5}$$


$$A_v = -600$$

BJT can amplify the  
voltages/signals  
very effectively
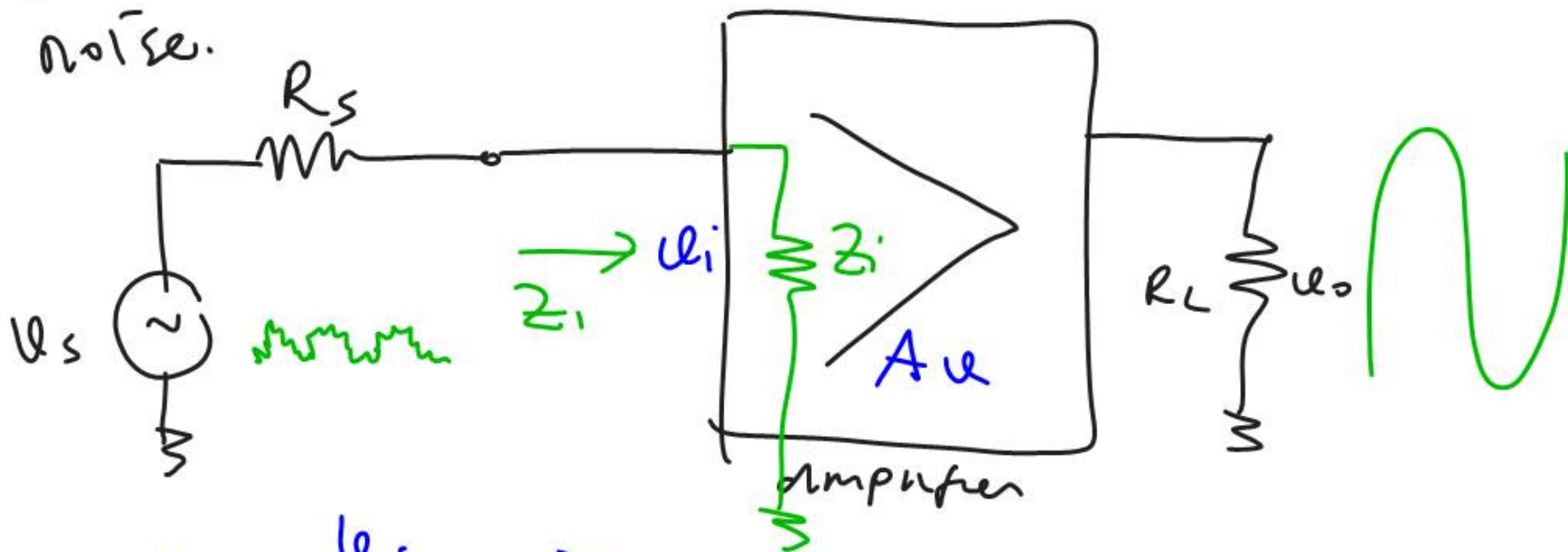
# INFORMATION

Normally signals of very small magnitudes ~~are~~ are desired to be amplified.

These small signals are generally buried in the noise.



$$v_i = \frac{v_s}{R_s + z_i} \cdot z_i$$

$$A_v = \frac{v_o}{v_i}$$

if  $z_i \gg R_s$   $R_s + z_i \approx z_i$ ; however if  $z_i \approx R_s$

$$v_i \approx v_s$$

$$v_o \approx \frac{1}{2} v_s$$