
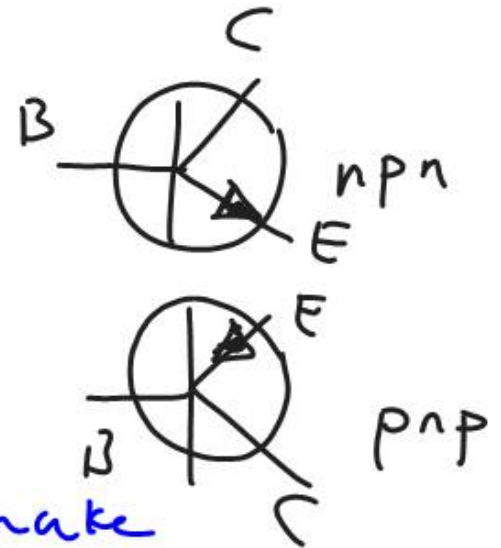


# Common-Base Configuration

21.05.2011  
©

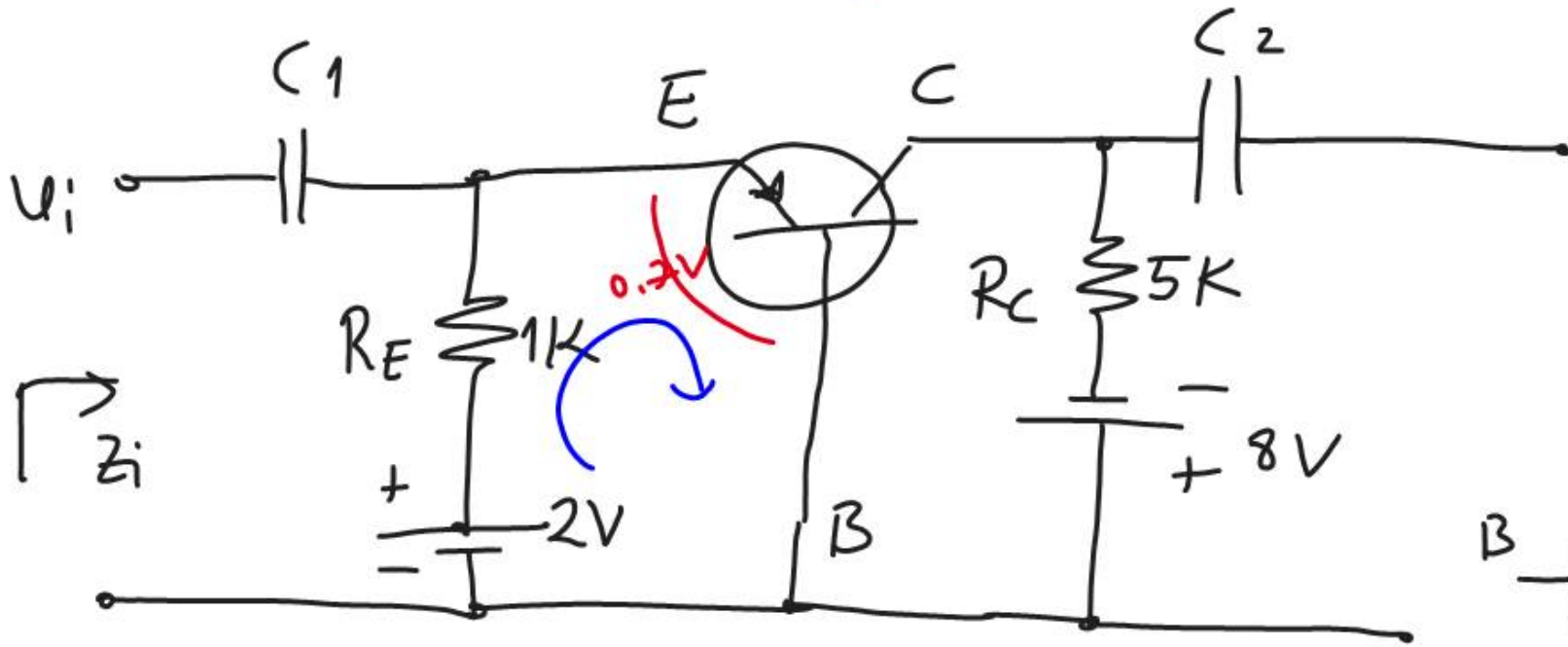

$$\alpha = 0.98$$

$$\alpha = \frac{I_C}{I_E} = \frac{I_C}{I_B} \cdot \frac{I_B}{I_E} = \beta \cdot \frac{1}{\beta+1} = \frac{\beta}{\beta+1}$$

$$I_E = I_B + I_C$$

$$\beta = \frac{I_C}{I_B}$$

a) to find  $r_e$  we make  
DC analysis:

input KVL:


$$I_E = \frac{2 - 0.7}{1K} = \frac{1.3}{10^3}$$

$$2V - I_E \cdot R_E - V_{EB} = 0$$

$$r_e = \frac{28 \times 10^{-3}}{1.3 \times 10^{-3}} = 20\Omega$$

$$I_E = 1.3 \text{ mA}$$

AC analysis:

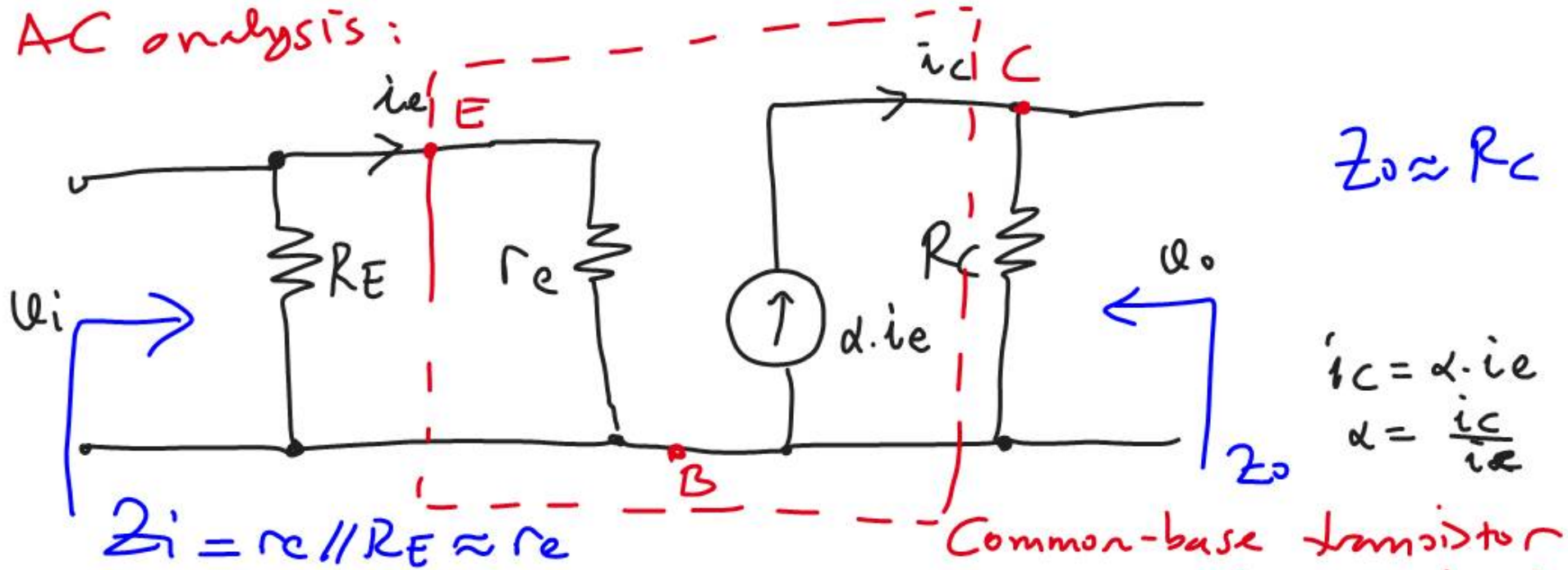

$$v_o = i_c \cdot R_C$$

$$v_i = i_e \cdot r_e$$

$$v_i \approx i_c \cdot r_e \Rightarrow i_c \approx \frac{v_i}{r_e}$$



$$v_o \approx \frac{v_i}{r_e} \cdot R_C \Rightarrow A_v = \frac{v_o}{v_i} = \frac{R_C}{r_e}$$

$$A_v \approx \frac{5 \times 10^3}{20} = \frac{50 \times 10^2}{20}$$

$$A_v \approx 250$$

↑ 0° phase shift in voltage gain!

# ex Cascode Configuration

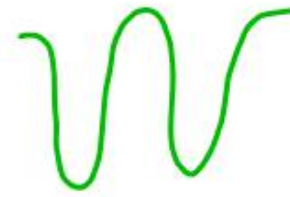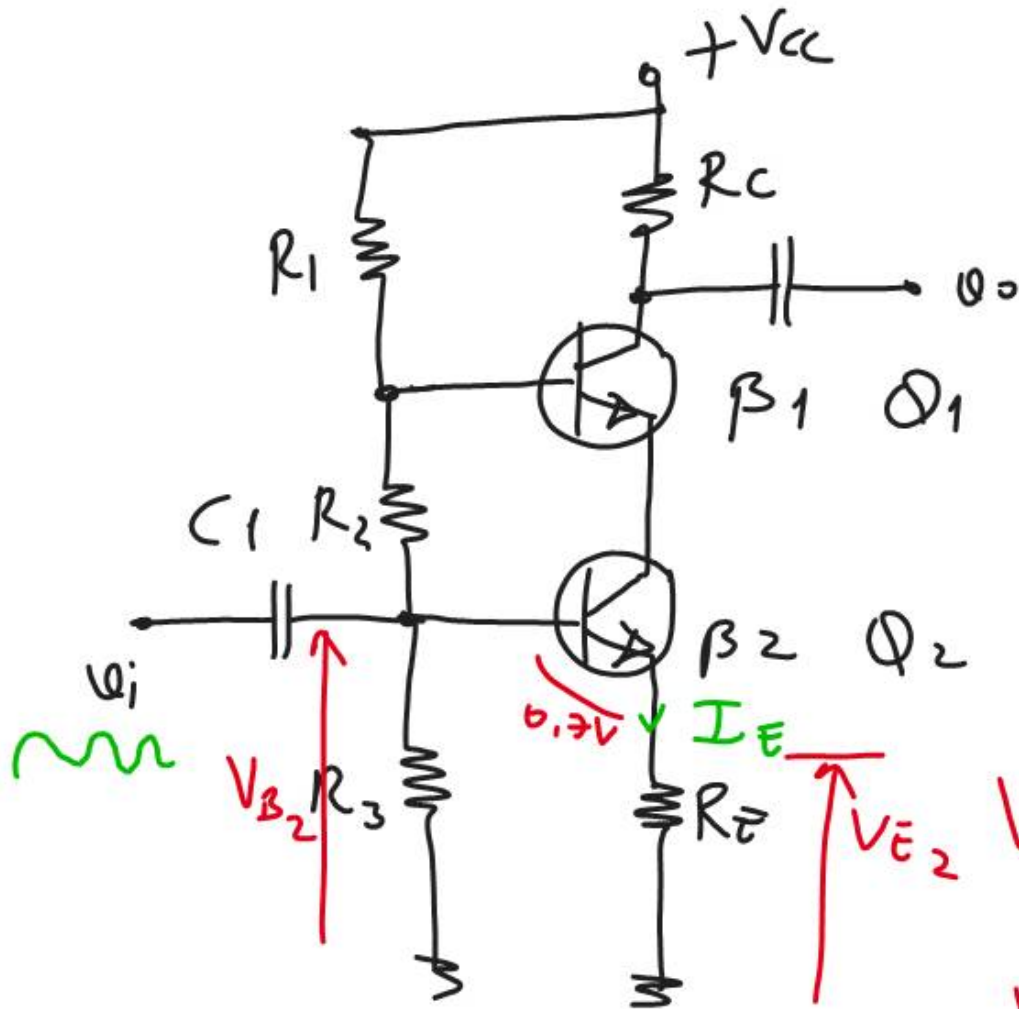

$$A_v = \frac{v_o}{v_i}$$


## DC analysis:

$$V_{B2} \approx \frac{V_{CC}}{R_1 + R_2 + R_3} \cdot R_3$$


$$V_{B2} - 0.7V = V_{E2}$$

$$\bar{I}_E = \frac{V_{E2}}{R_E} \quad r_e = \frac{V_T}{I_E} \checkmark$$

AC Analysis:

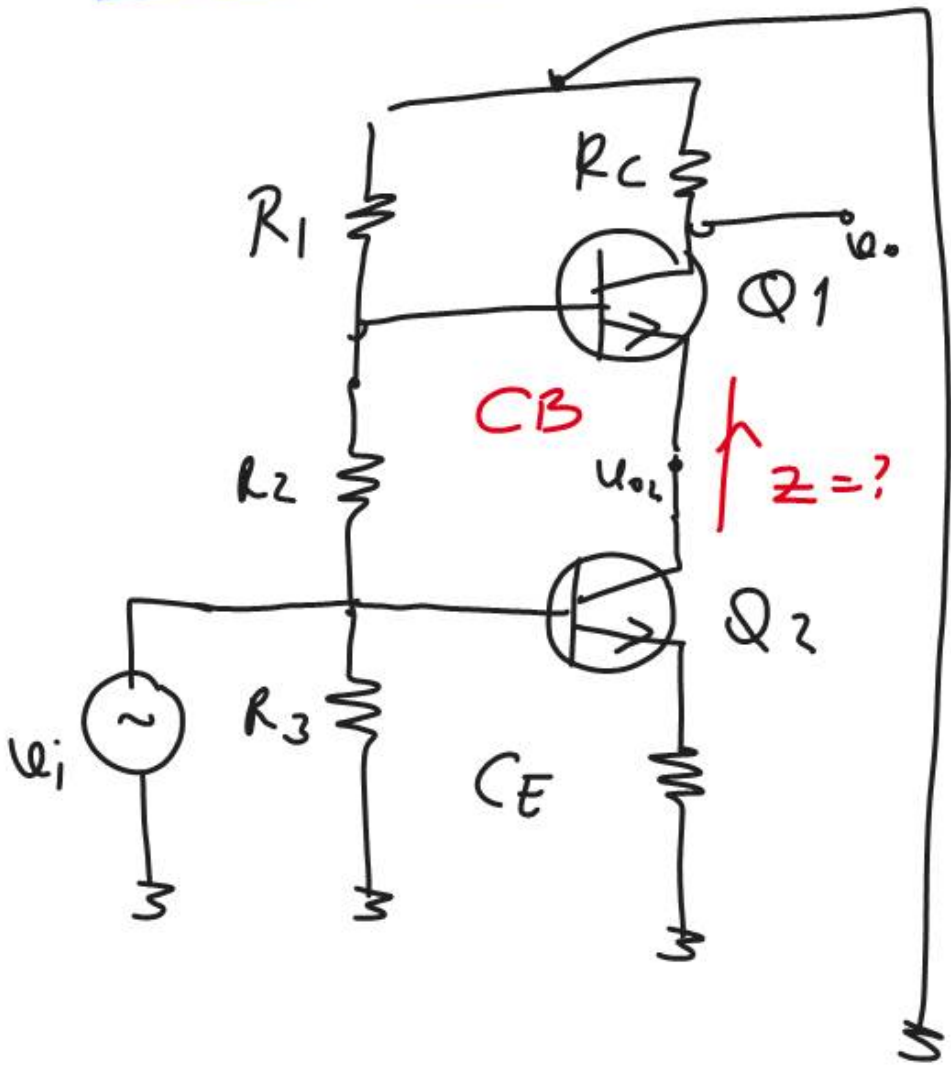

Q2

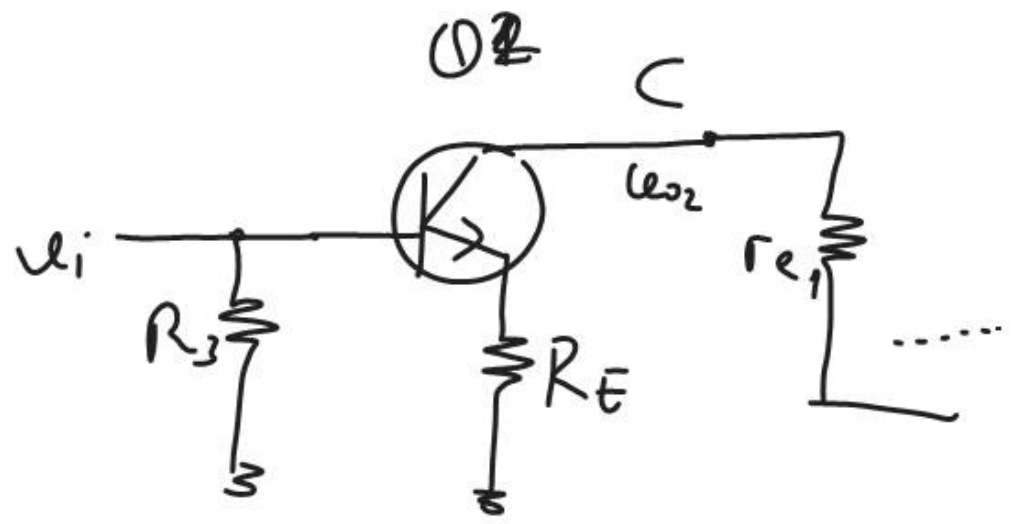


CE with RE (not bypassed)

$$A_u = \frac{-R_c}{r_{e1} + R_E} = -\frac{(r_{e1})}{r_{e2} + R_E} = -\frac{r_e}{r_{e1} + R_E}$$

$$I_{E1} = I_{E2} = I_C \Rightarrow r_{e1} = r_{e2} = r_e$$

$$\boxed{\frac{v_{o2}}{v_i} = -\frac{r_e}{r_{e1} + R_E}}$$

Q1


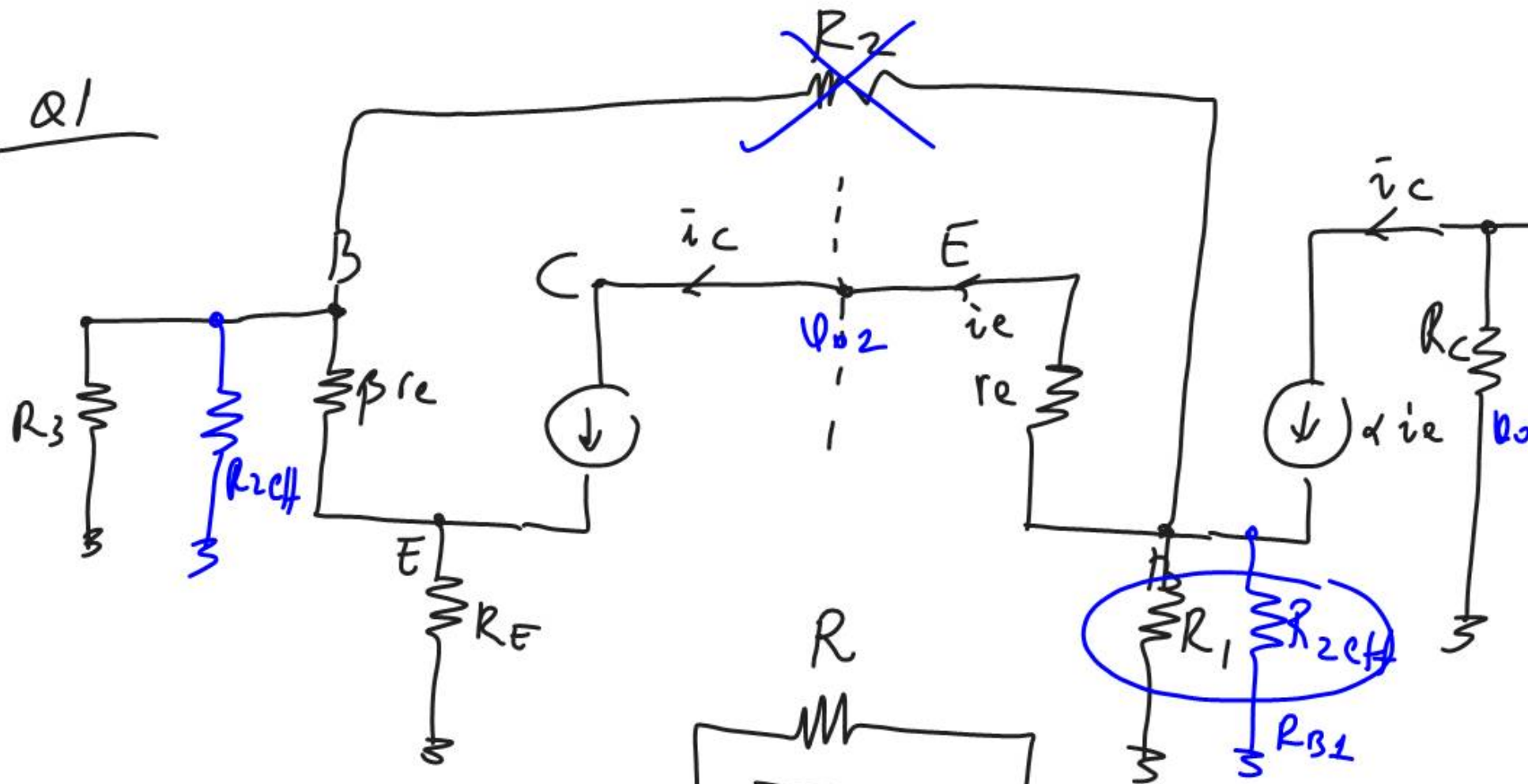


$$U_o = -i_c \cdot R_c \approx -i_e \cdot R_c$$

$$U_{o2} = -i_e \cdot r_e - i_b \cdot R_{B1}$$

$$= -i_e \cdot r_e - \frac{i_e}{\beta + 1} \cdot R_{B1} = -i_e \left( r_e + \frac{R_{B1}}{\beta + 1} \right)$$
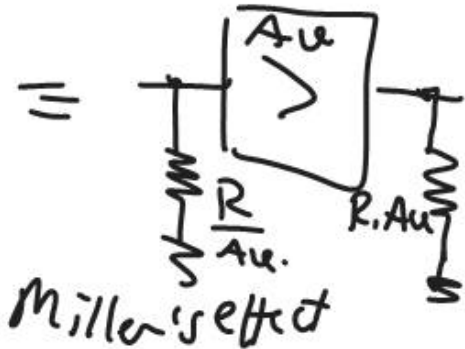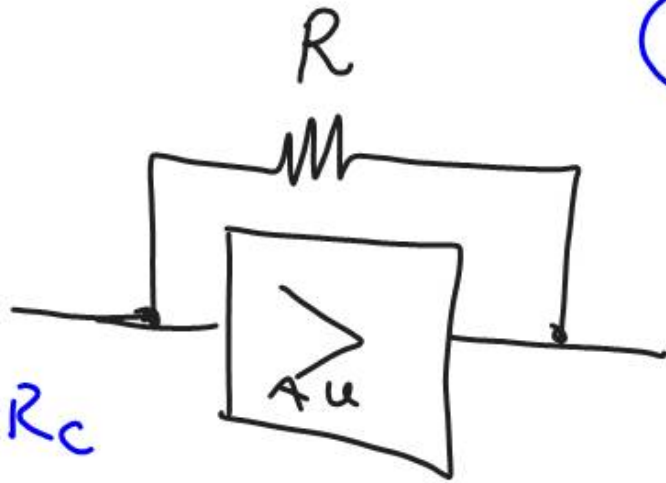
$$i_e = -U_{o2} / \left( r_e + \frac{R_{B1}}{\beta + 1} \right)$$




$$\frac{u_o}{u_{o2}} = \frac{R_c}{r_e + \frac{R_{B1}}{\beta + 1}} \rightarrow u_o = + \frac{R_c}{r_e + \frac{R_{B1}}{\beta + 1}} \cdot u_{o2}$$

$$u_{o2} = - \frac{r_e}{r_e + R_E} \cdot u_i$$

$$u_o = + \frac{R_c}{r_e + \frac{R_{B1}}{\beta + 1}} \cdot \left( - \frac{r_e}{r_e + R_E} \right) u_i$$

$$A_{uT} = \frac{u_o}{u_i} = - \frac{R_c \cdot r_e}{\left( r_e + \frac{R_{B1}}{\beta + 1} \right) (r_e + R_E)}$$

ex

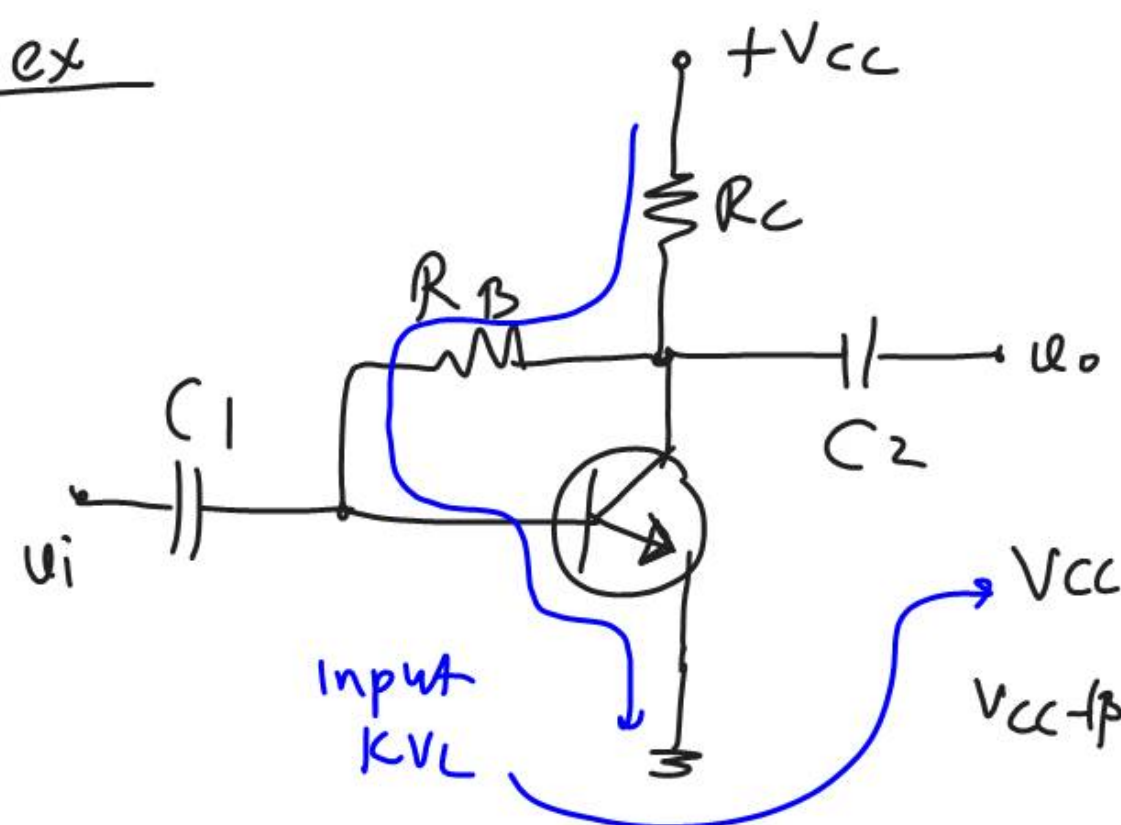

Common-emitter.

DC analysis

$$V_{CC} - I_E R_C - I_B R_B - V_{BE} = 0$$


$$V_{CC} - (\beta + 1) I_B R_C - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_C}$$

$$I_E = (\beta + 1) I_B$$

$$r_e = \frac{V_T}{I_E}$$

# AC analysis

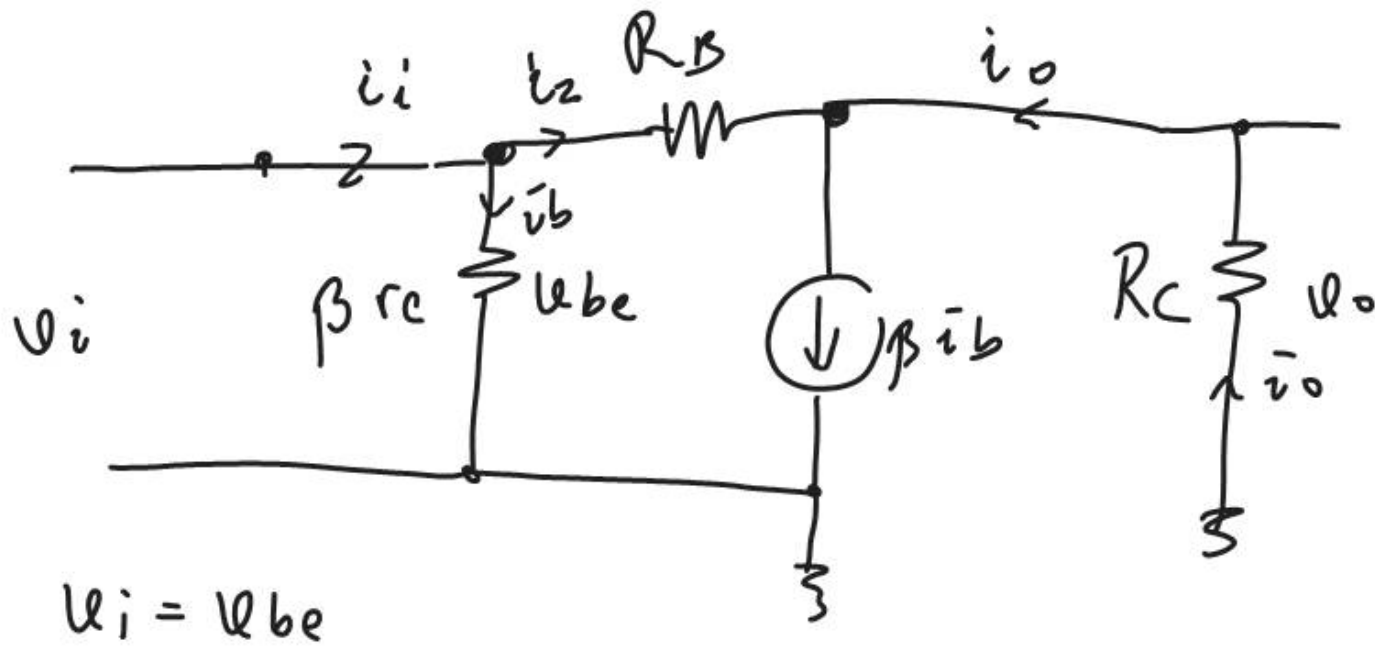


Calculate  $Z_i$ ,  $Z_o$ , and  $A_{v_e} = \frac{v_o}{v_i}$





For a good amplifier  
 $R_i \rightarrow \infty$   $A_u$  should be big.  
 $R_o \rightarrow 0$

In reality  $\Rightarrow$

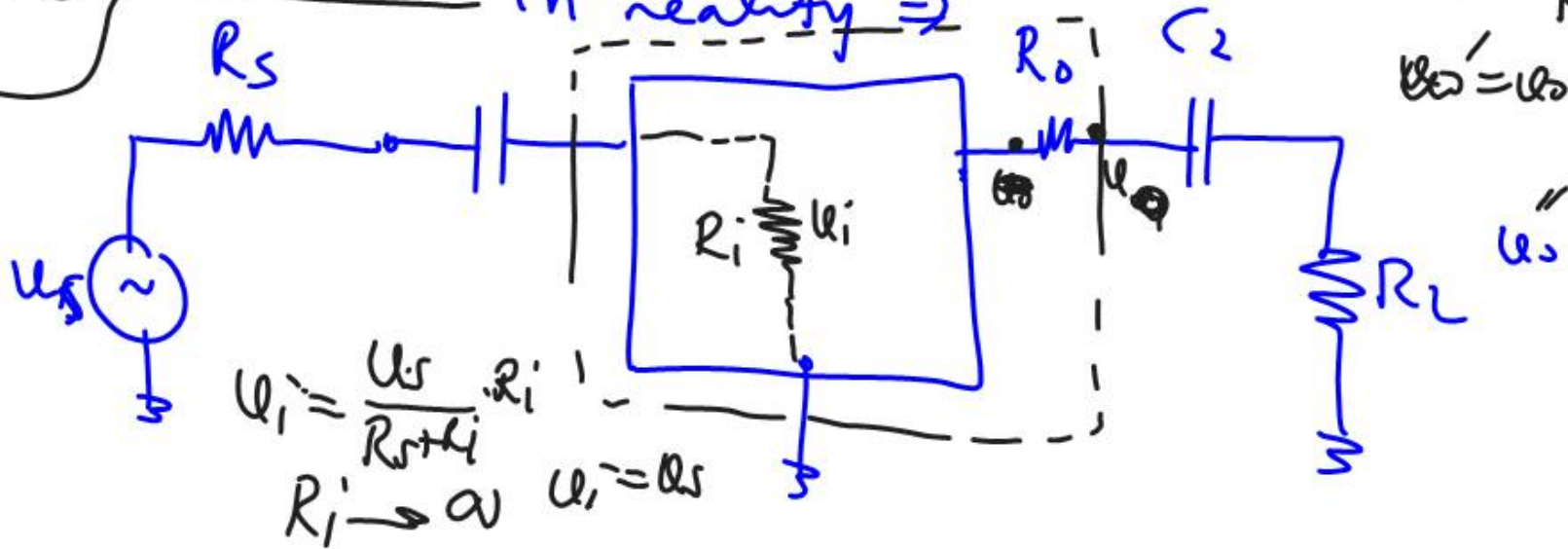

$$u_i = \frac{u_s \cdot R_i}{R_o + R_i}$$

$$R_i \rightarrow \infty \quad u_i = u_s$$

$$u_o' = \frac{u_o}{R_o + R_L} \cdot R_L$$

$$u_o' = u_o \Rightarrow R_o \rightarrow 0$$

