
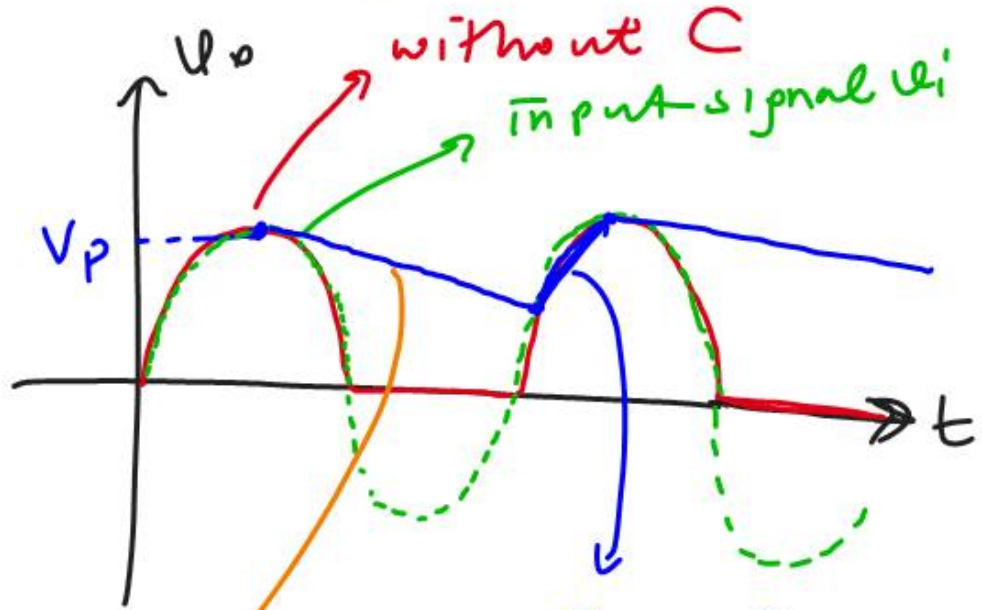


08.03.2011

CZ 3

# A Rectifier with a Filter

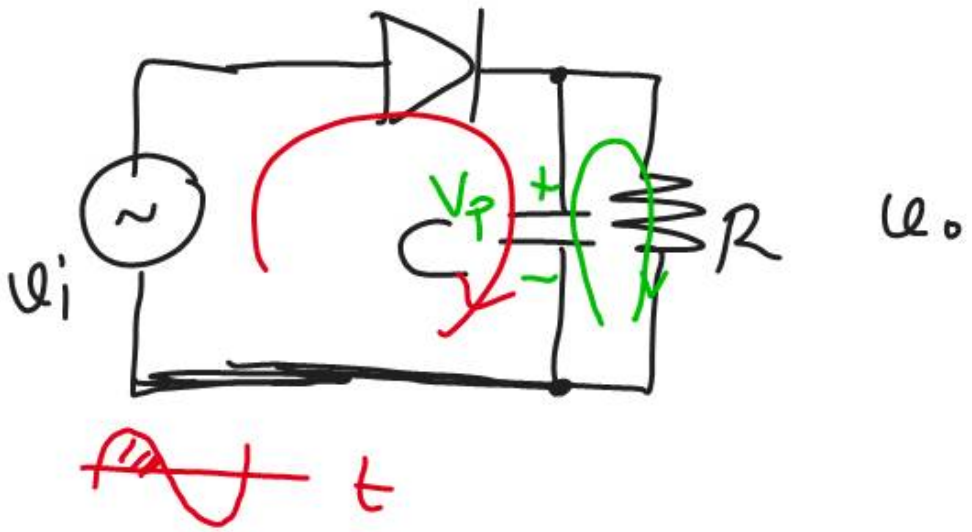

Capacitor charging

$$u_c = u_o = V_p (1 - e^{-t/\tau_c})$$


$$\tau = r_d \cdot C$$

$$r_d = \frac{dI}{dV}$$

(diode dynamic resistance)  
 $\sim 3-5 \Omega$


Capacitor discharges through \$R\$ (Diode is RB)

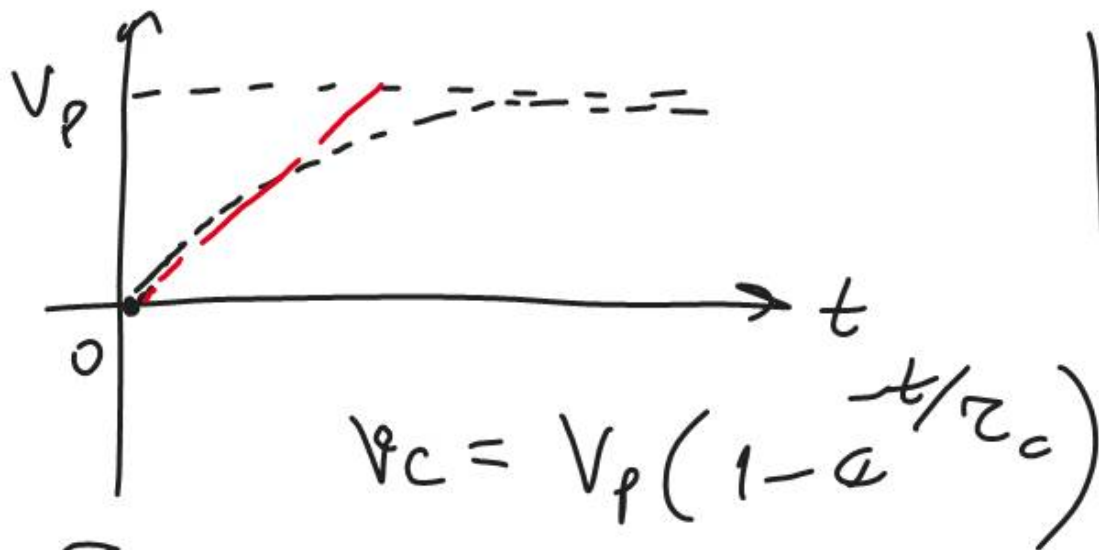Capacitor Charges through the diode up to \$V\_p\$



$$\tau_c = r_d \cdot C$$

CHARGING

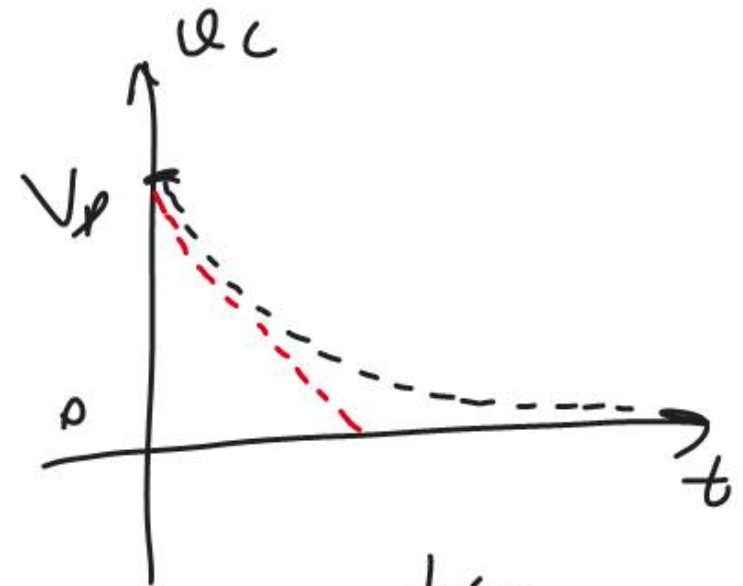


$$\tau_D = R \cdot C$$

$$\tau_D = R \cdot C$$


DISCHARGING

$$\tau_D \gg \tau_c$$

$$R \cdot C \gg r_d \cdot C$$

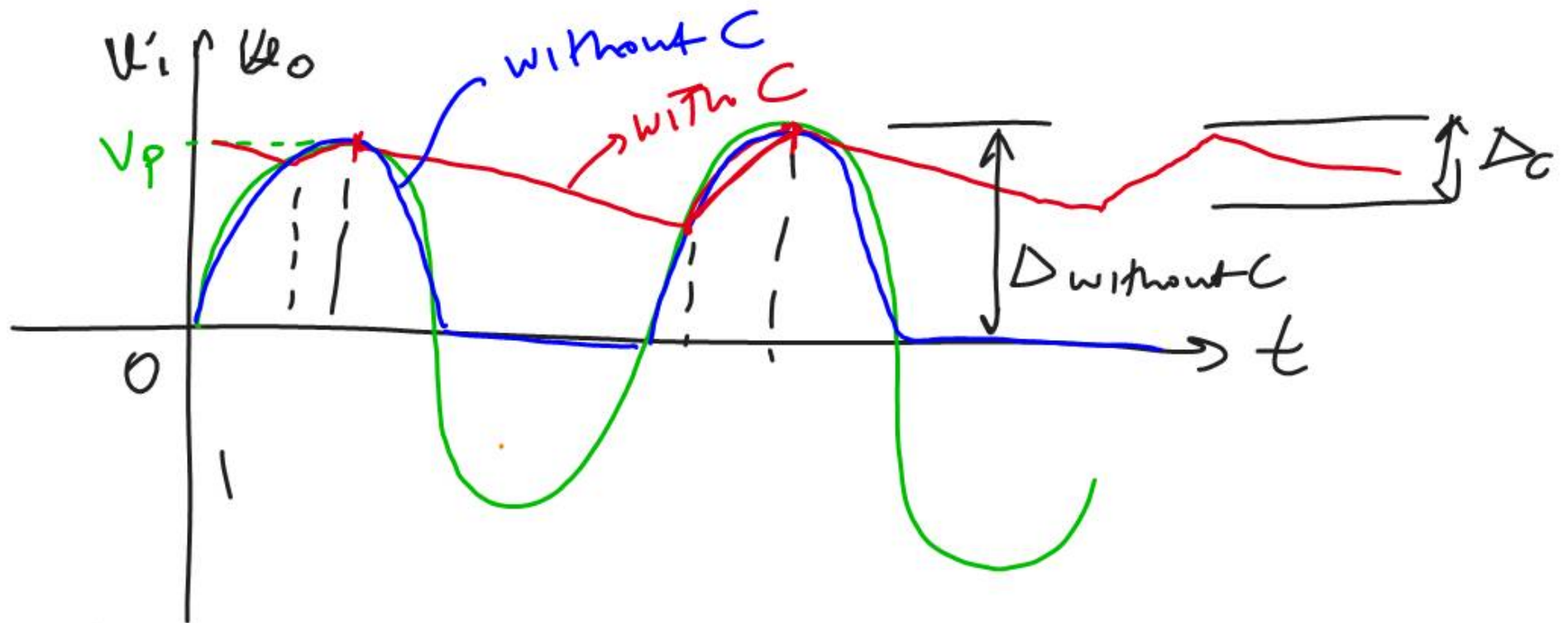


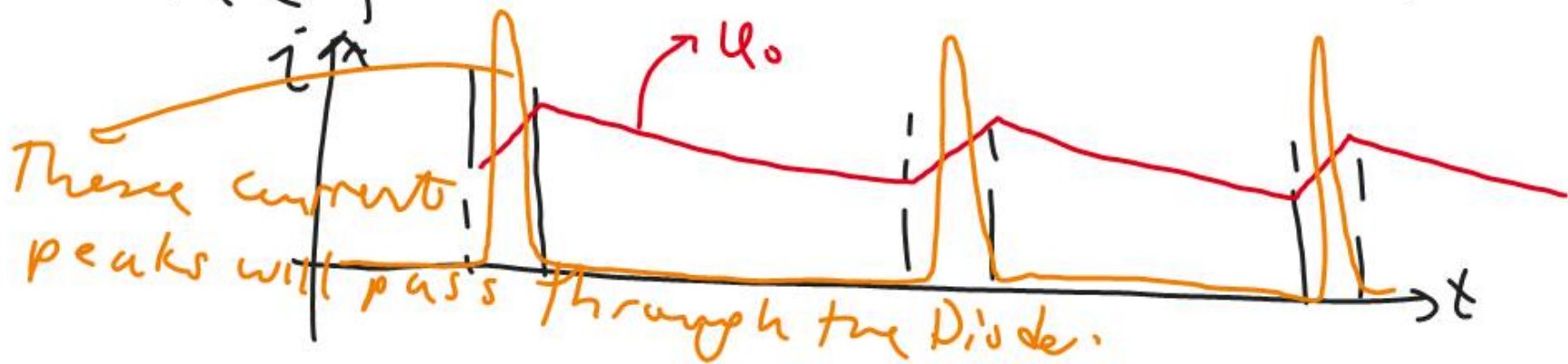With the C added, the ripple at the output voltage is reduced (R and C form a low pass RC filter which smooths the output voltage)





Therefore in reducing RIPPLE we have the price to pay for:

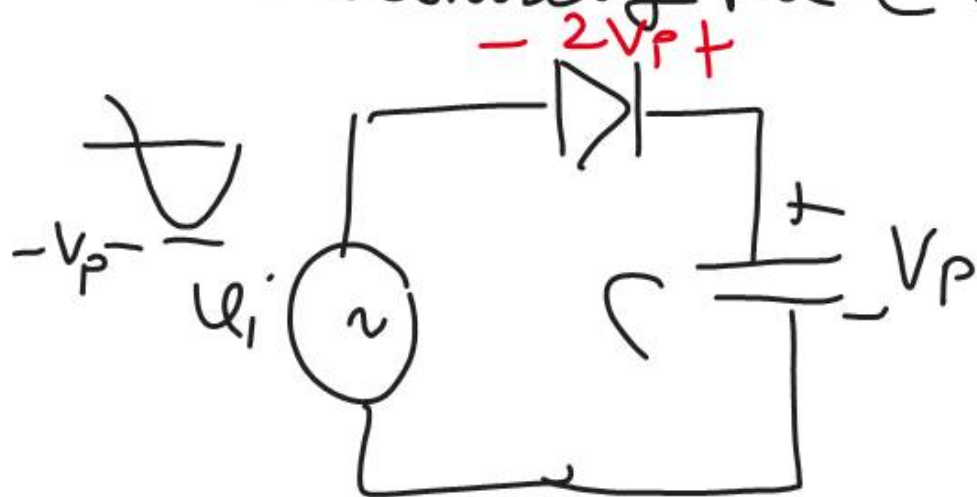- Peak current through the diode (because of C charging)
- Peak inverse voltage (PIV) doubled because of the C: ( $PIV \approx 2V_p$ )




# A full-wave rectifier with filter

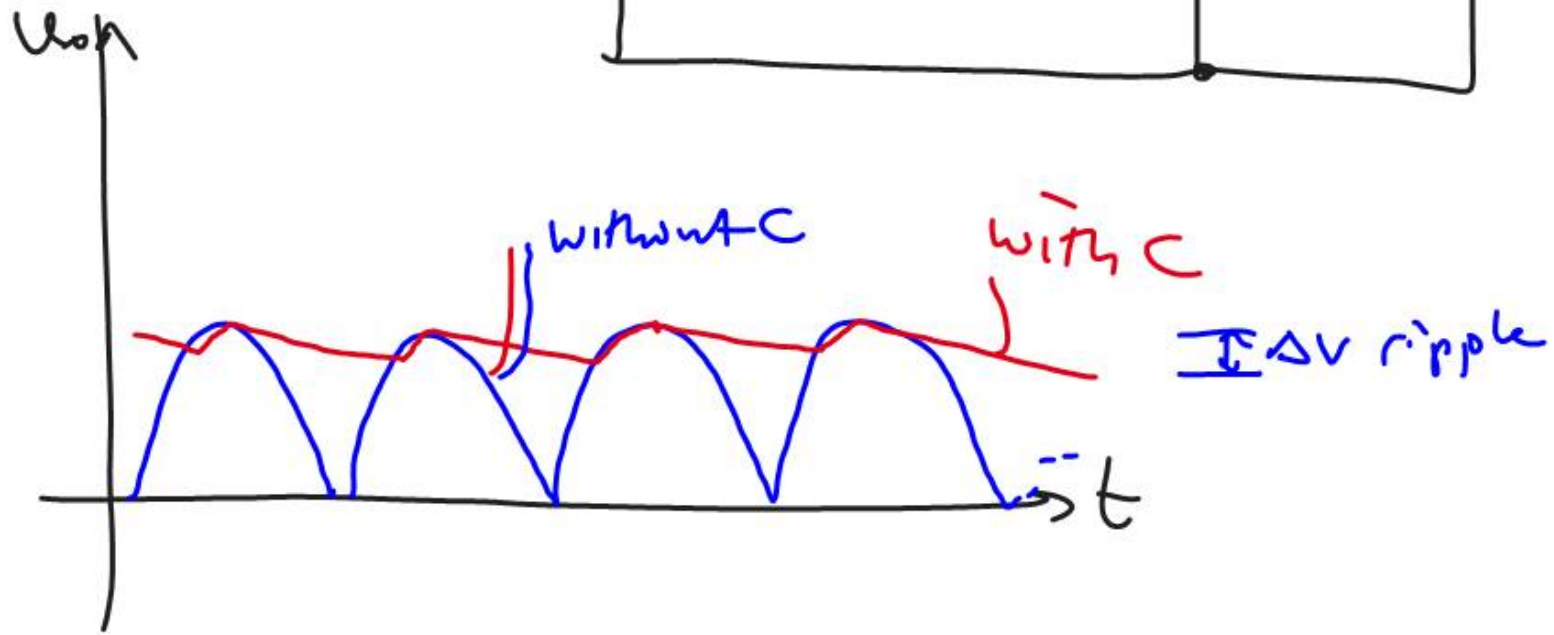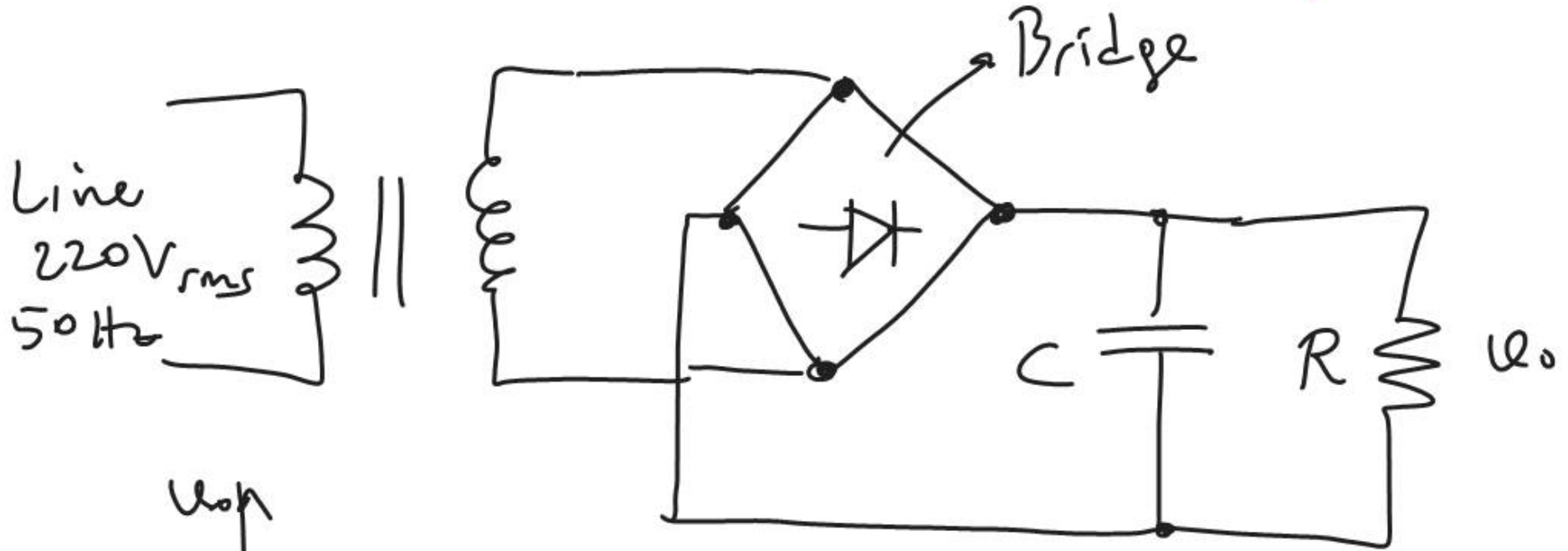
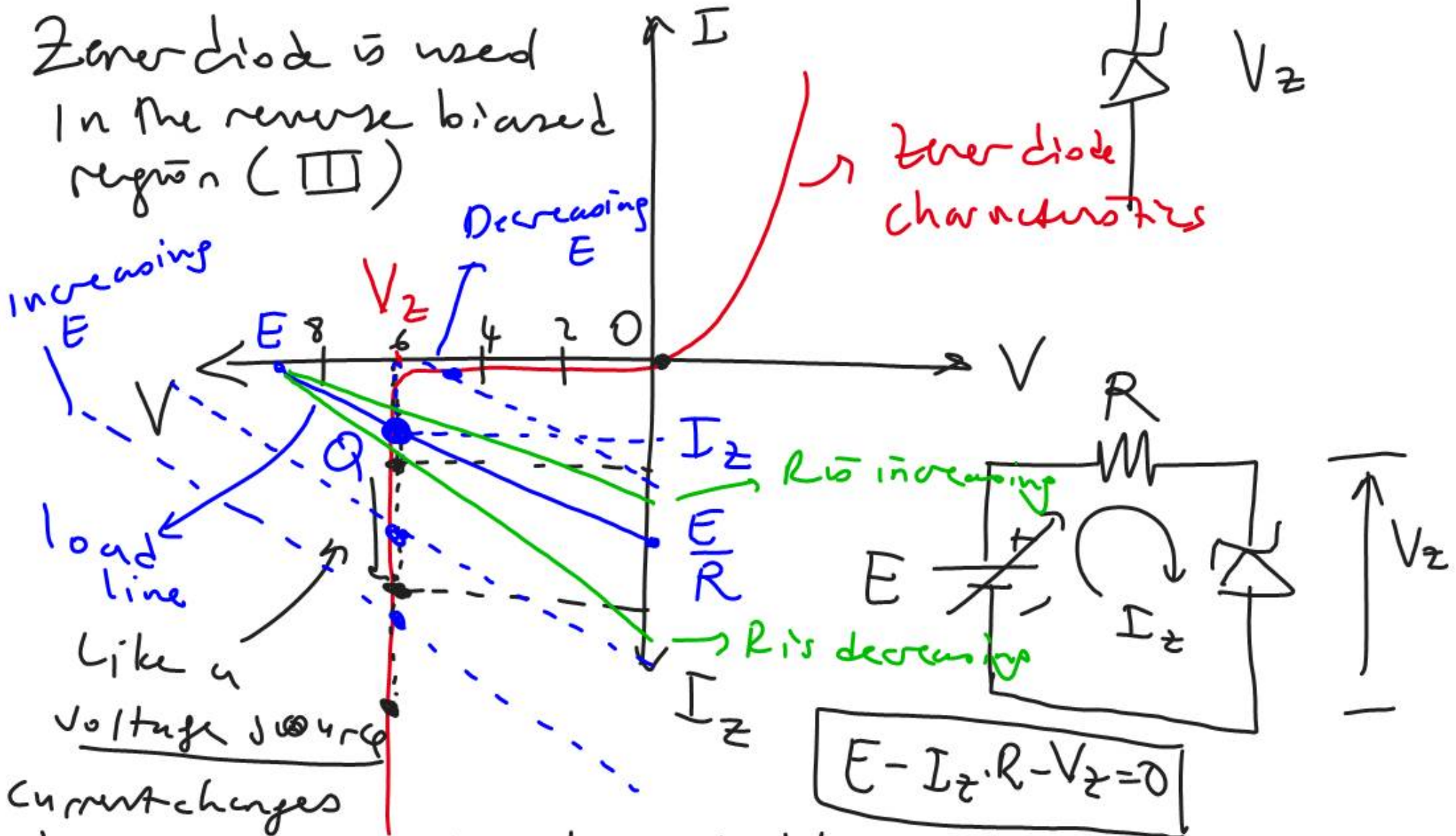
# The ZENER DIODE

Zener diode is used  
in the reverse biased  
region (III)




current changes

but voltage will always be constant! When  $I_z = 0$   $E = V_z$   
 $V_z = 0$   $I_z = E/R$



$$E - I_z \cdot R - V_z = 0$$

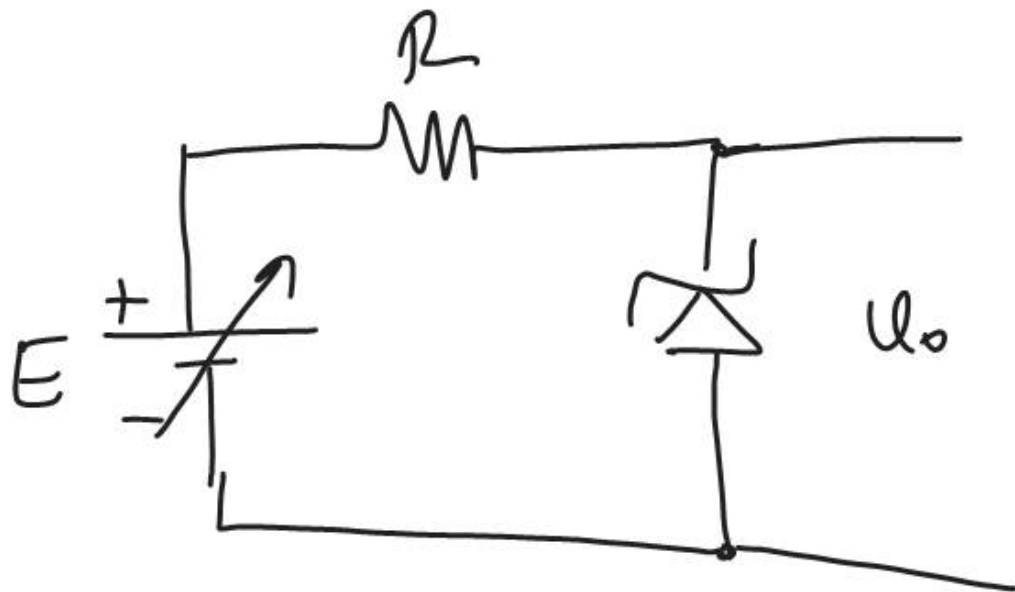Zener diode is used as a REGULATOR  
(to obtain a constant voltage)





$$\text{if } E > V_z \\ U_0 = V_z$$

ex

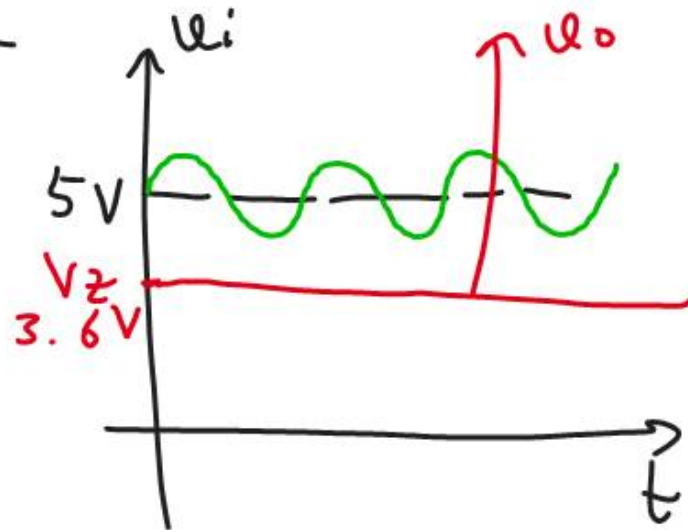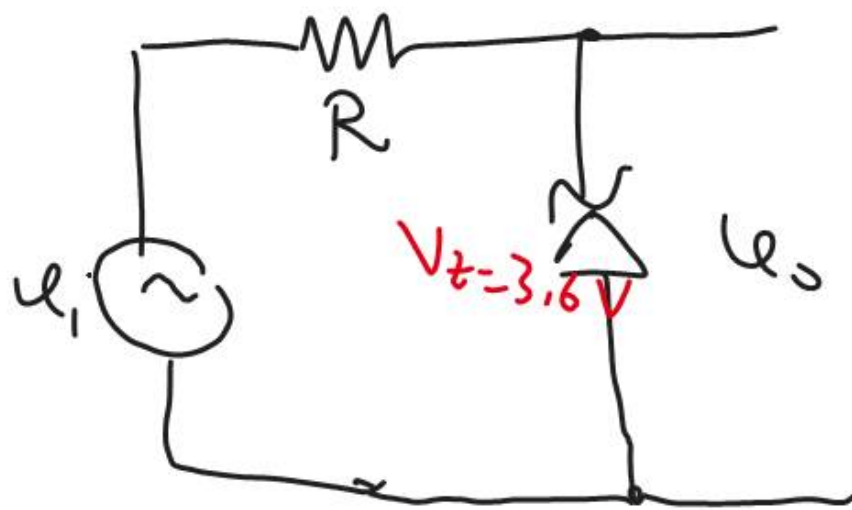

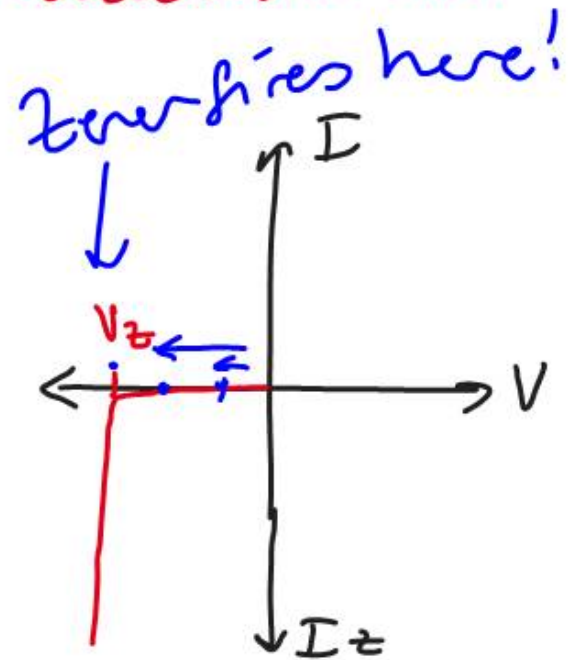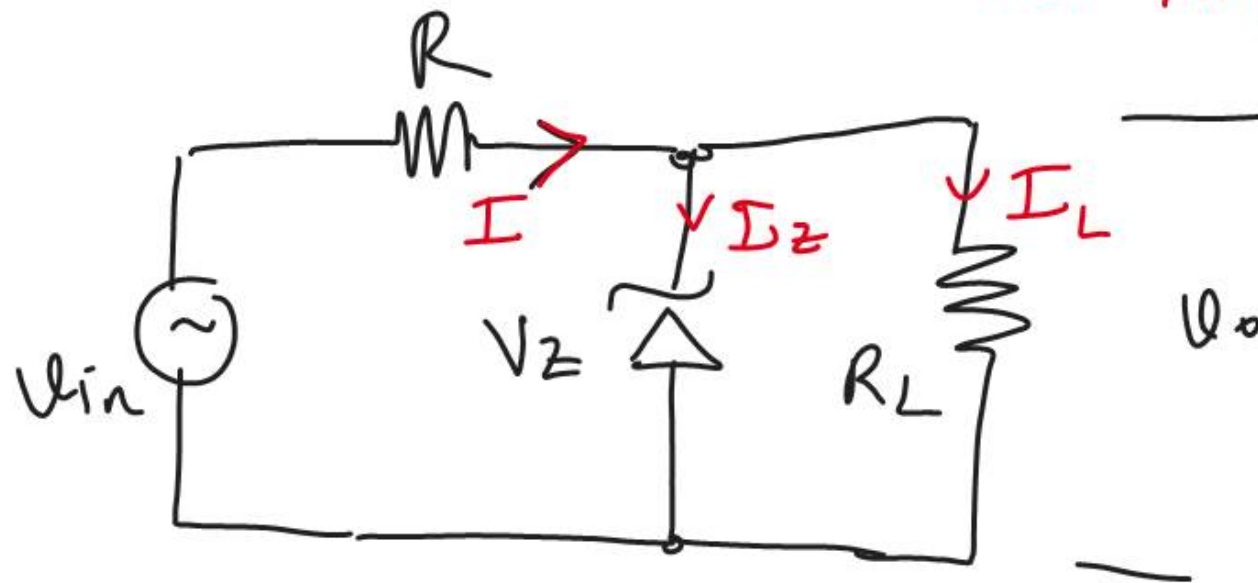When we have a  $R_L$  in parallel with  $V_Z$ :



$$U_o = \frac{U_{in}}{R + R_L} \cdot R_L$$


when Zener does not fire  
(i.e. when it is open-circuit)

$$\frac{U_{in}}{R + R_L} \cdot R_L \geq V_Z \Rightarrow \text{for the Zener to fire}$$

When Zener fires  $U_o = V_Z$



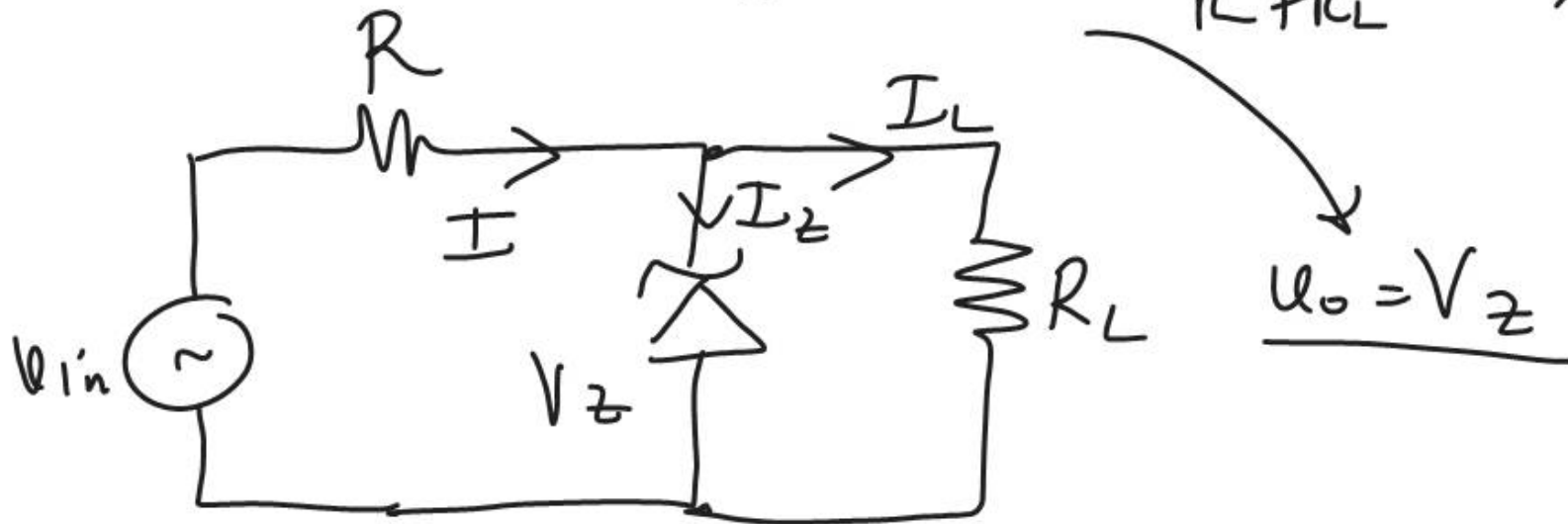When Zener fires (i.e. when  $\frac{U_{in}}{R+R_L} \cdot R_L \geq V_Z$ )




$$I_L = \frac{V_Z}{R_L} \text{ constant.}$$

$$I = I_L + I_Z$$

$$I = \frac{U_{in} - V_Z}{R}$$

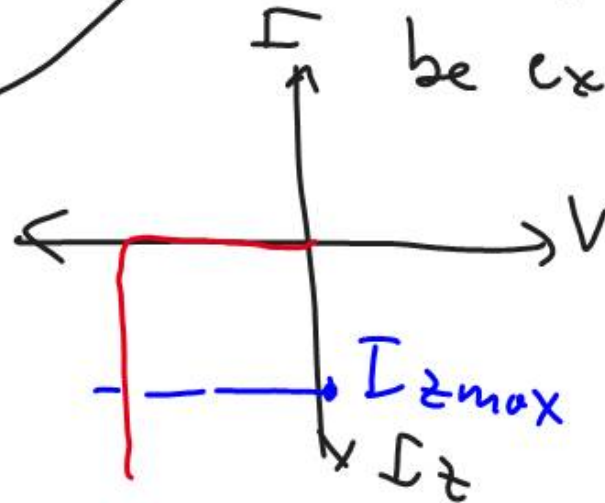There is a limit for  $I_Z$   
 $I_{Zmax}$  should not be exceeded!



A Zero can regulate the input voltage change, or a change in  $R_L$ :

It provides:

1 - Line Regulation ( $V_{in}$  changes,  $R_L$  constant)

2 - Load Regulation ( $V_{in}$  constant,  $R_L$  changes)

1. LINE REGULATION with ZENER DIODE