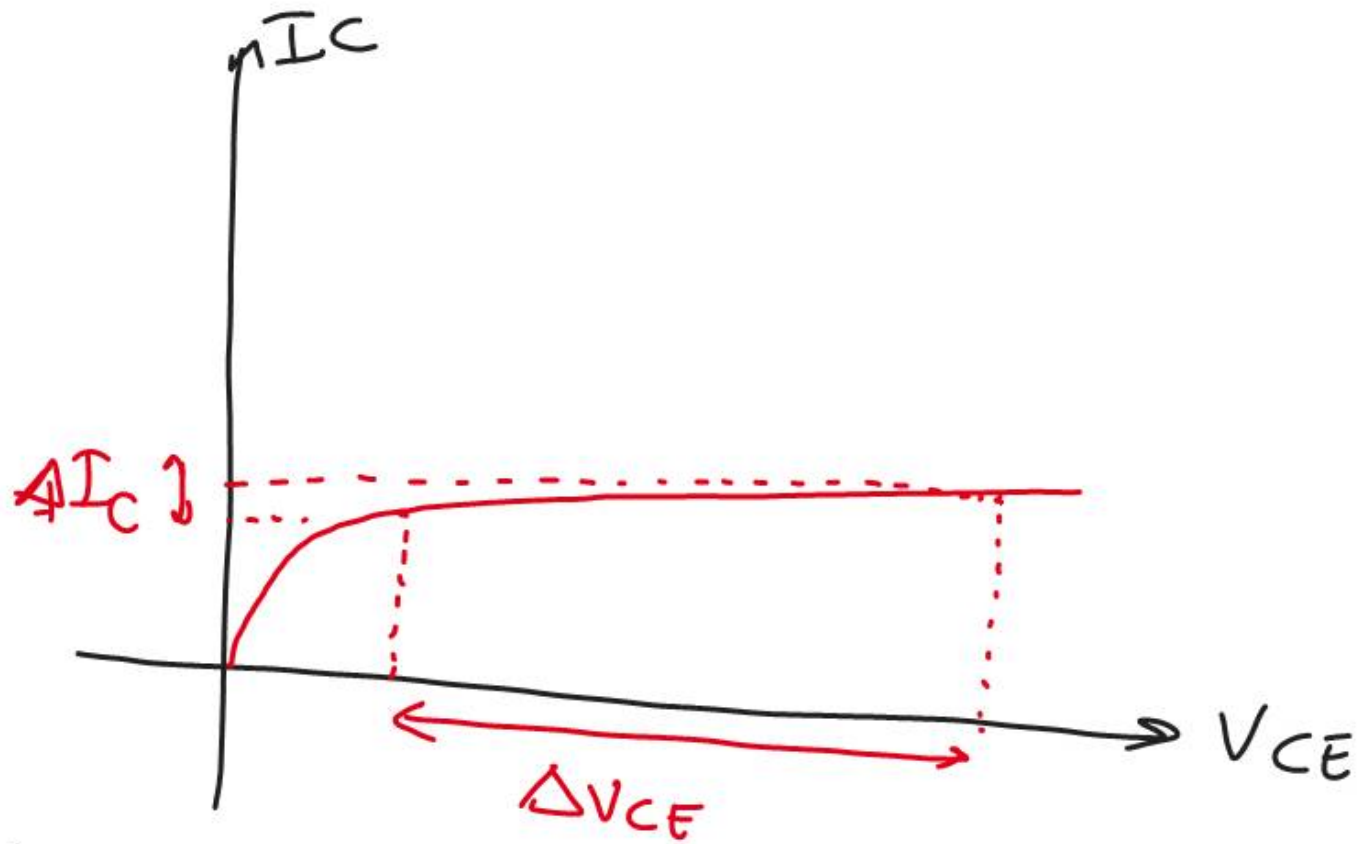


12.04.2011
©



Early's Effect:


$$\Delta V_{BE} \propto \Delta V_{CE}$$

⇒ When V_{CE} changes, so does V_{BE}

When V_{BE} changes, so does I_B

When I_B changes, so does I_C (βI_B)

Wilson's Current Mirror:

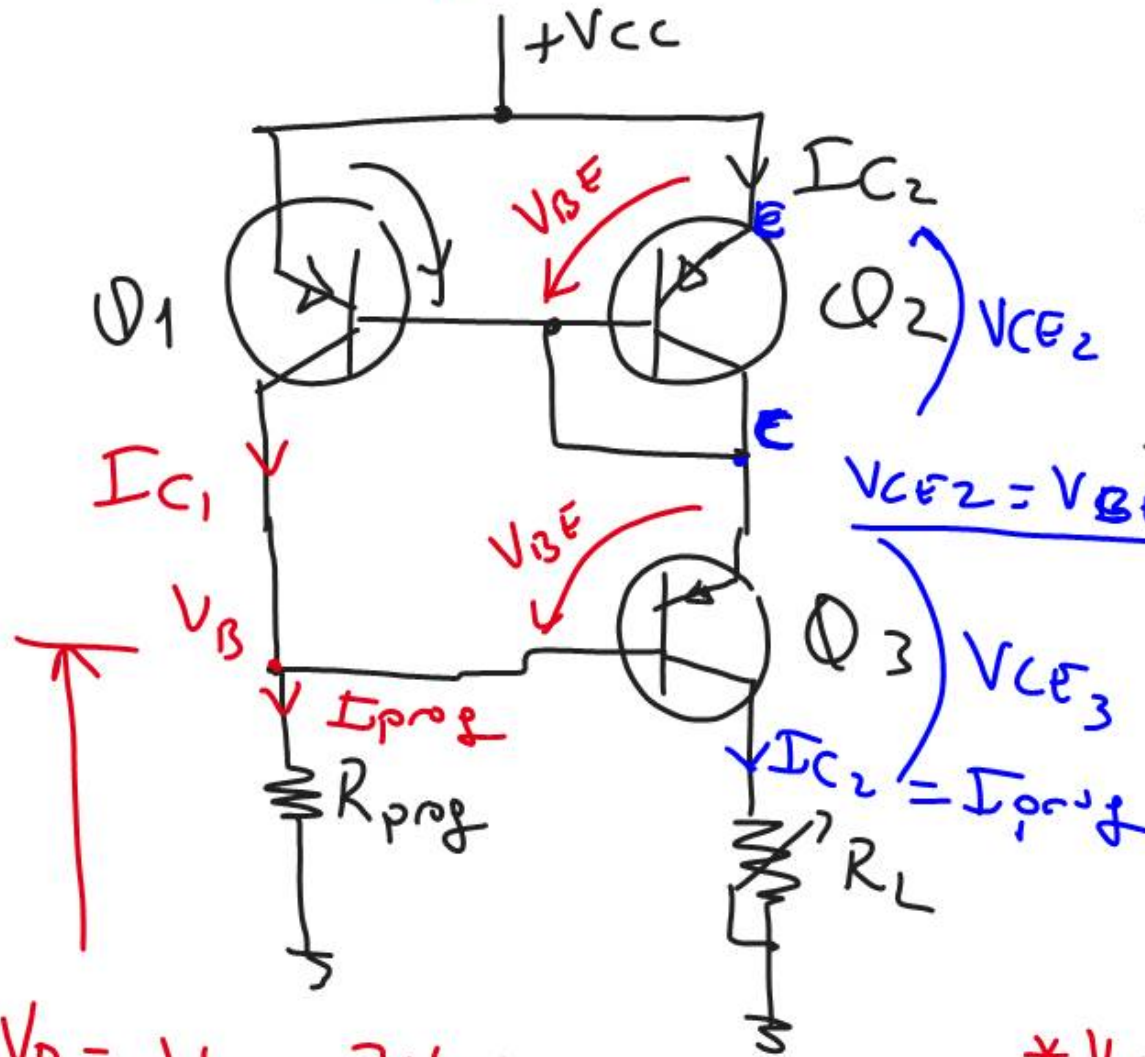

$$I_{C1} \equiv I_{prog}$$

$$V_{BE1} = V_{BE2} \text{ (matched)}$$

$$I_{C2} \equiv I_{C1} = I_{prog}$$

$$V_{CE2} = V_{BE2}$$

* Since V_{CE2} does not change

I_{C2} is not affected by $\Delta V_{CE2} = 0$
(no Early's effect on I_{C2})

* V_{CE3} is changing to provide the constant current I_{prog} .

However since I_{C3} is not determining the I_{prog} This will not be a problem for the mirror.

$$V_B = V_{CC} - 2V_{BE}$$


$$I_{prog} = \frac{V_{CC} - 2V_{BE}}{R_{prog}}$$

Field Effect Transistors (FETs)

Moore's Law?

FET

Unipolar devices

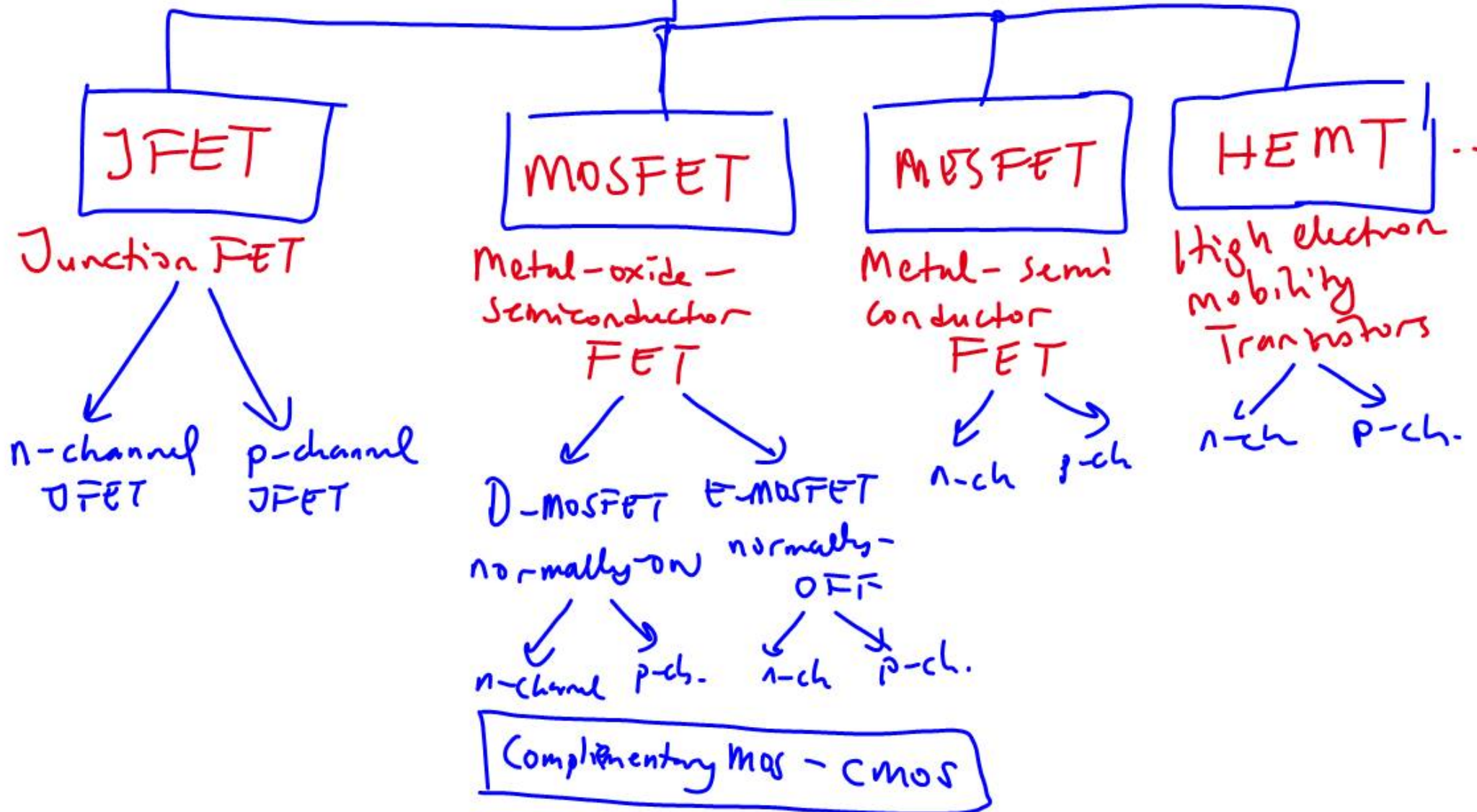

$$I = qn \cdot v \cdot A$$

↓

$$C \cdot \frac{1}{cm^3} \cdot \frac{cm}{s} \cdot cm^2$$

$$= \frac{C}{s} = \text{Ampere}$$

by controlling


- the cross-sectional area
(A) JFET, MESFET

- or the number of carriers
(n) MOSFET, HEMT, MESFET

- or the velocity of
carriers (v)
HEMT, JFET, MOSFET



The current can be controlled.

An n-channel JFET

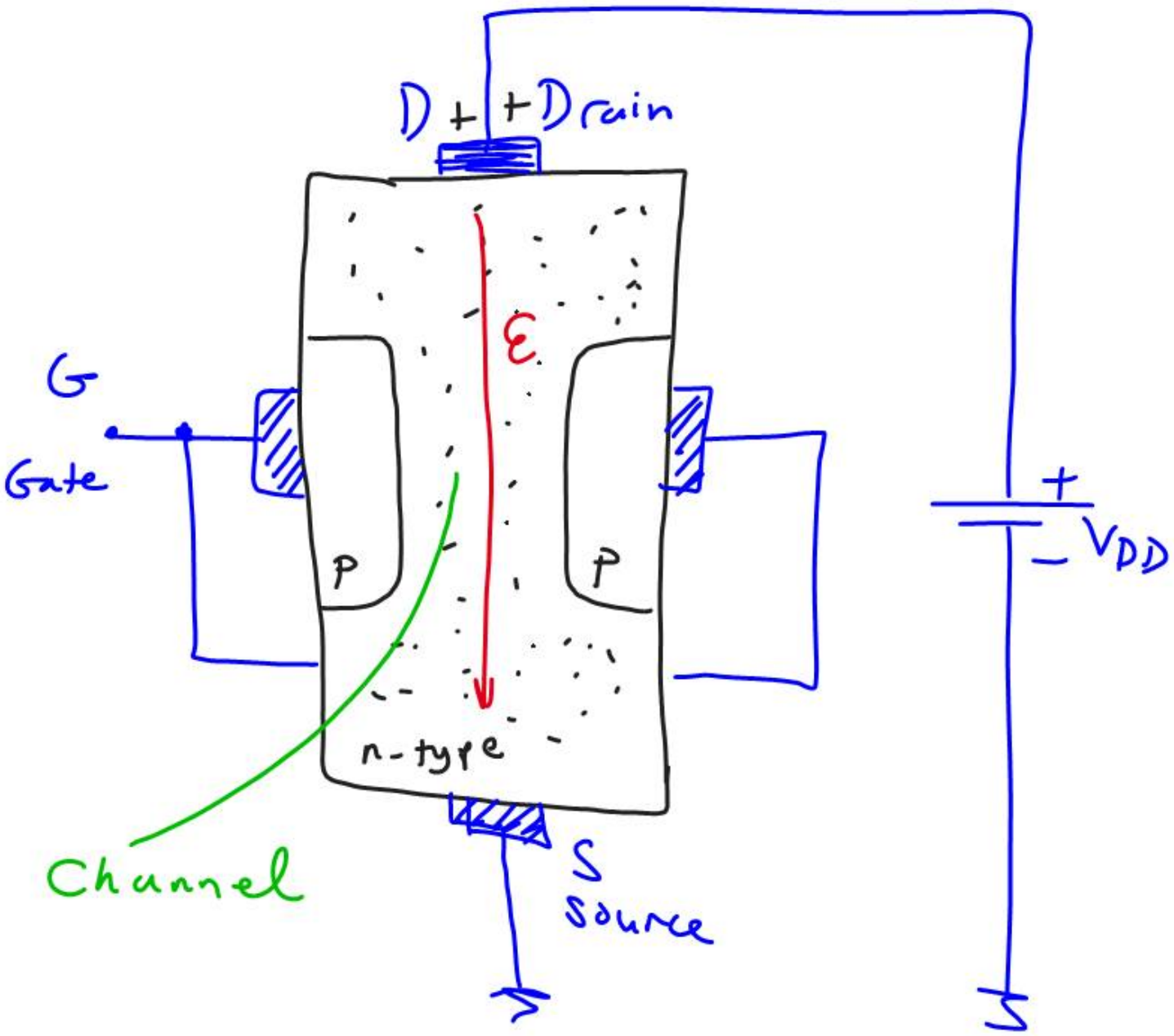

* Gate-to-source Junction is always REVERSE-BIASED.

RECITATION:

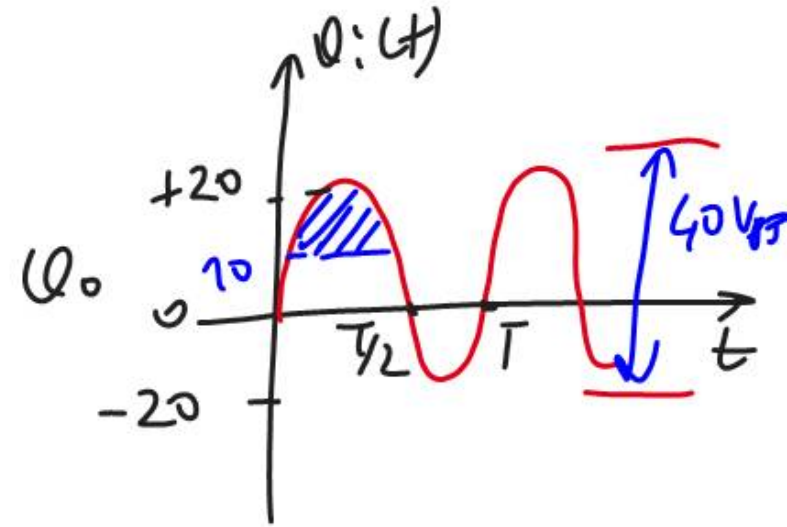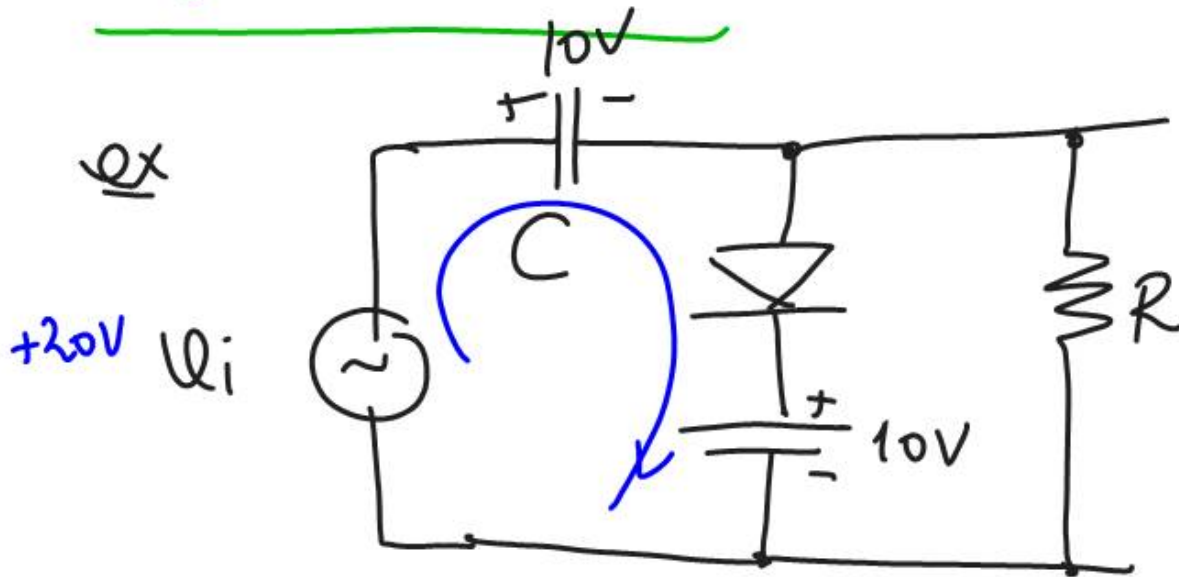


A clamper:

After the capacitor is charged the diode will never be forward biased.


$$u_i - u_c - 10V = 0$$

$$20 - u_c - 10 = 0$$


$$\underline{u_c = 10V}$$

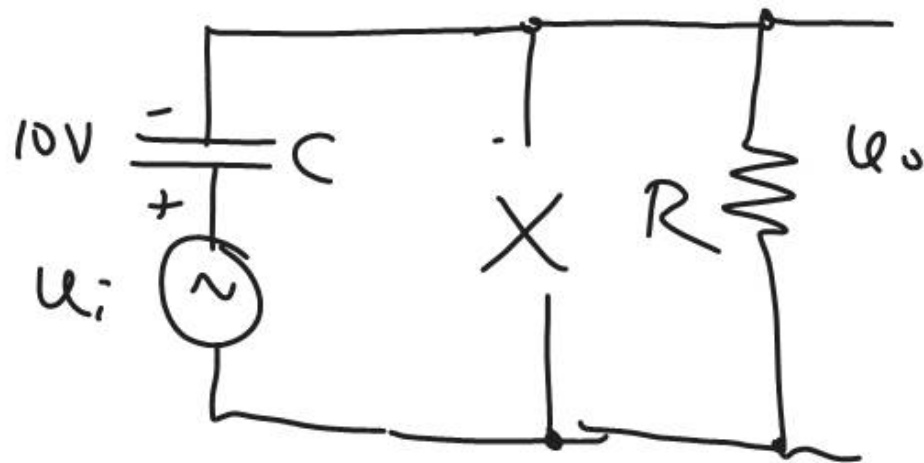

$$\underline{u_o = u_i - 10V}$$

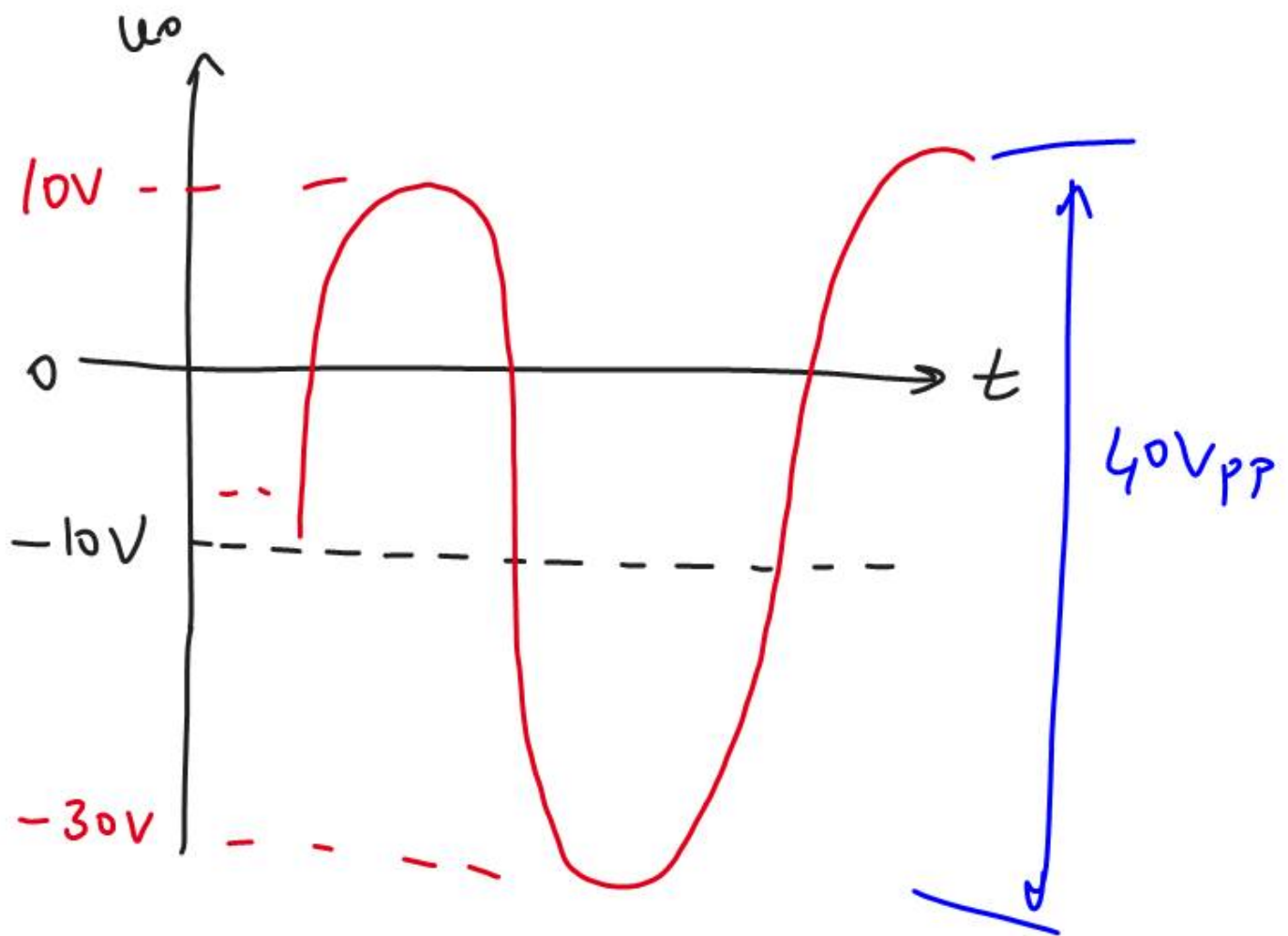

ex Cascode

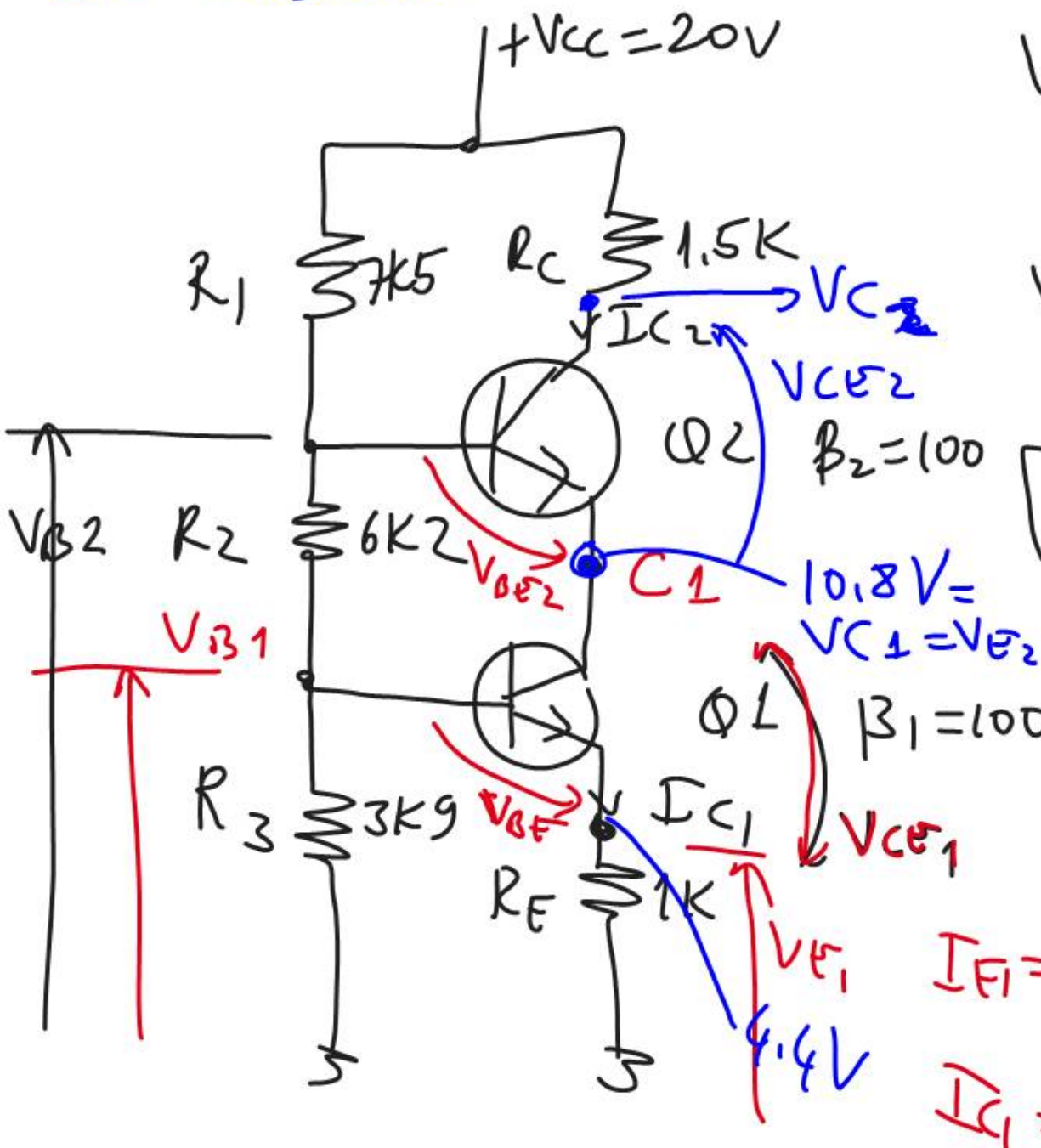

$$V_{B1} \equiv \frac{V_{cc}}{R_1 + R_2 + R_3} \cdot R_3$$

$$V_{B1} = \frac{20}{(7.5 + 6.2 + 3.9) \times 10^3} \times 3.9 \times 10^3$$

$$V_{B1} \equiv 4.4V$$

$$V_E = V_{B1} - V_{BE1} = 4.4 - 0.7 = 3.7V$$

$$V_E = 3.7V$$

$$I_{E1} = \frac{V_E}{R_E} = \frac{3.7}{1k} = 3.7mA$$

$$I_{C1} \approx 3.7mA$$

$$I_{E1} = \frac{V_{E1}}{R_E}$$

$$I_{C1} \approx I_{E1}$$

$$10.8V = V_{C1} = V_{E2}$$

$$\beta_2 = 100$$

$$\beta_1 = 100$$

$$V_{B2} \approx \frac{V_{CC}}{(7.5 + 6.2 + 3.9) \times 10^3} \times (6.2 + 3.9) \times 10^3$$

$$V_{B2} \approx 11.5 \text{ V}$$

$$V_{E2} = V_{C1} = V_{B2} - V_{BE2} \\ = 11.5 - 0.7$$

$$\underline{V_{C1} = V_{E2} = 10.8 \text{ V}}$$

$$V_{CE1} = V_{C1} - V_{E1} \\ = 10.8 - 4.4$$

$$\boxed{V_{CE1} = 6.4 \text{ V}}$$

$$I_{C2} \approx I_{E1} = 3.7 \text{ mA}$$

$$V_{C2} = V_{CC} - I_{C2} \cdot R_C$$

$$V_{C2} = 20 - 3.7 \times 10^{-3} \times 1.5 \times 10^3$$


$$V_{C2} = 20 - 5.6$$

$$\boxed{V_{C2} = 14.4 \text{ V}}$$

$$V_{CE2} = V_{C2} - V_{E2} \\ = 14.4 - 10.8$$

$$\boxed{V_{CE2} = 3.6 \text{ V}}$$

ex:

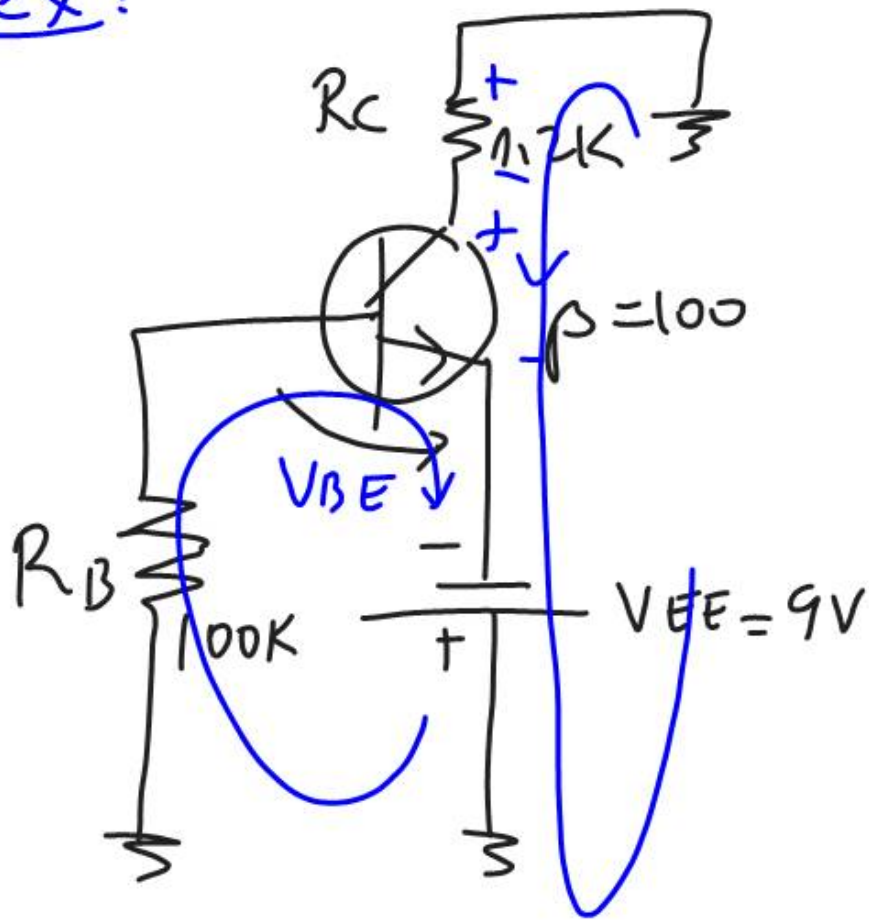

KVL input:

$$V_{EE} - R_B I_B - V_{BE} = 0$$

$$I_B = \frac{V_{EE} - V_{BE}}{R_B}$$

$$I_B = \frac{9 - 0.7}{10^5} = \frac{8.3}{10^5}$$

$$= 83 \times 10^{-6} \quad V_{CE} = V_{EE} - I_C R_C$$

$$I_C = \beta I_B$$

$$I_B = 83 \mu A$$

$$I_C = 83 \times 10^{-6} \times 10^2 = 8.3 \times 10^{-3} = \underline{8.3 \text{ mA}}$$

$$= 9 - \frac{8.3 \times 1.2}{10^{-3} \times 10^3}$$

$$V_{CE} < 0$$

XX
Not working!

Output KVL

$$0 - I_C R_C - V_{CE} + V_{CE} = 0$$