

Midterm Exam

April 13th, 2011

Wednesday 14:40 - 16:40

14.03.2011

©

1N4001 Diode Datasheet

log w. 2m, 2


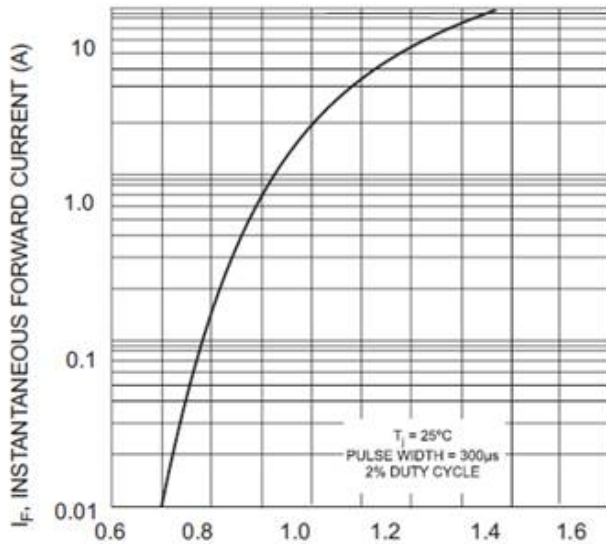



Fig. 2 Typical Forward Characteristics

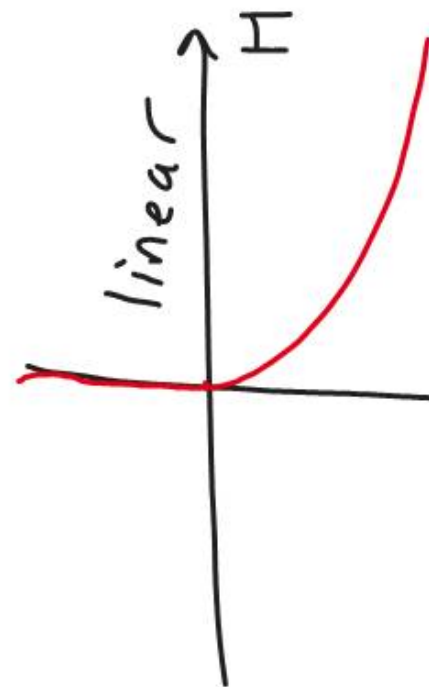

$$I = I_0 (e^{\frac{V}{V_T}} - 1)$$



$$\log I \approx \log I_0 + \log e^{\frac{V}{V_T}}$$
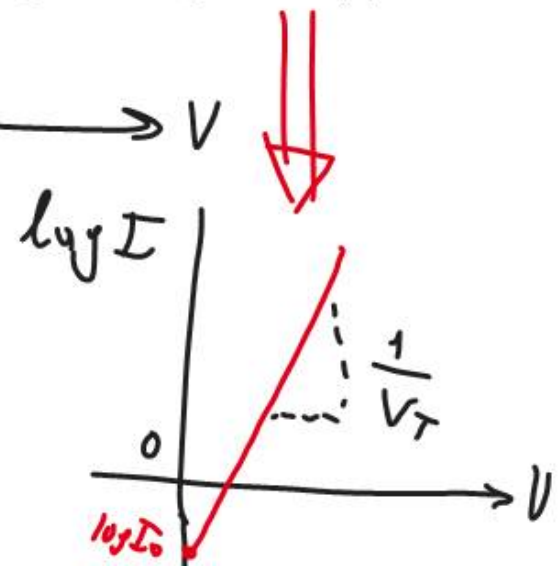
$$\log I \approx \log I_0 + \frac{V}{V_T}$$



# 1) Line Regulation with Zener

$R_L$  constant,  $V_i$  changing

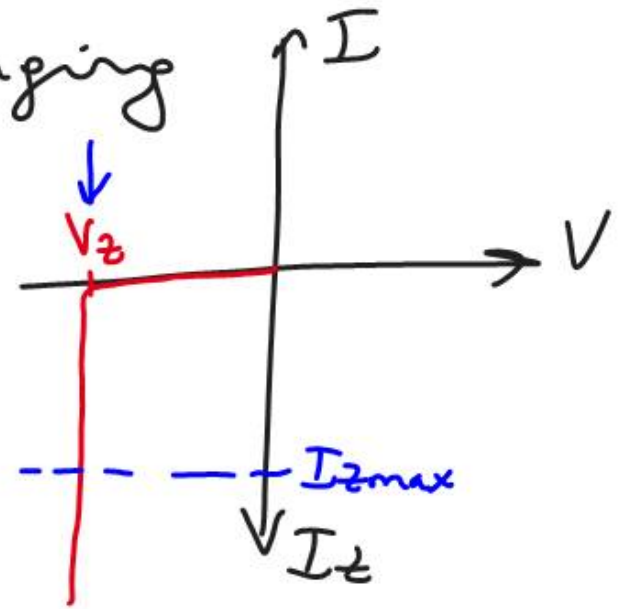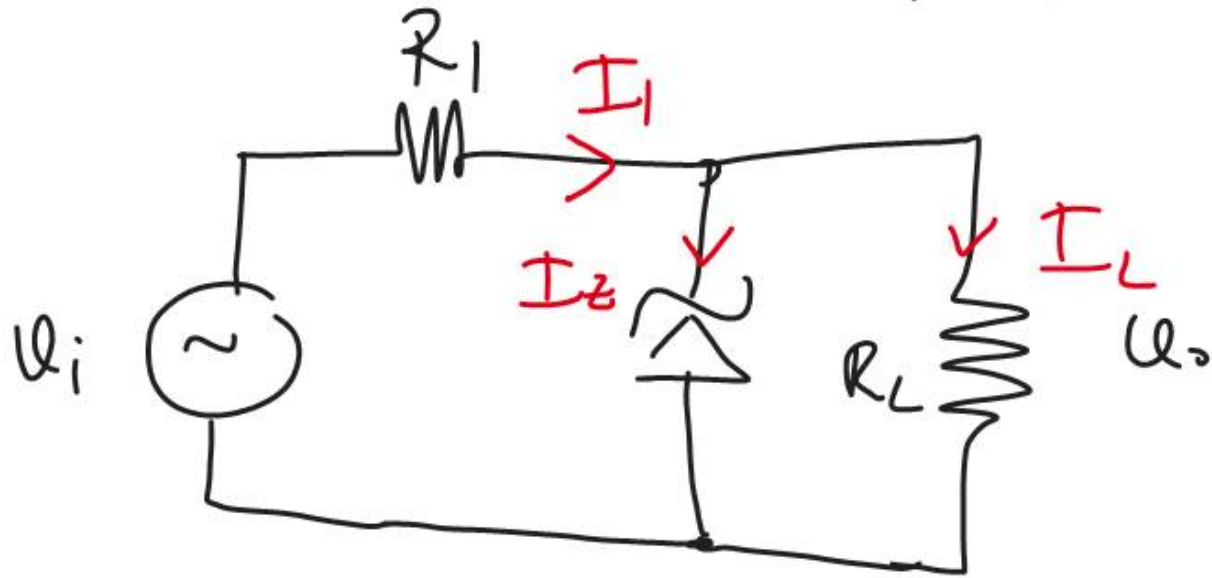

For the Zener to fire: The voltage across the Zener diode  $\geq V_Z$

$$\frac{U_i \cdot R_L}{R_1 + R_L} \geq V_Z$$

$\Rightarrow$  This gives the min value of the input signal.

$$U_{i \min} = V_Z - \frac{R_L + R_1}{R_L}$$


$$I_1 = I_z + I_L$$

$I_z$  should not exceed  $I_{zmax}$

$$I_{1max} = I_{zmax} + I_L$$

$$I_1 = \frac{V_i - V_z}{R_1}$$
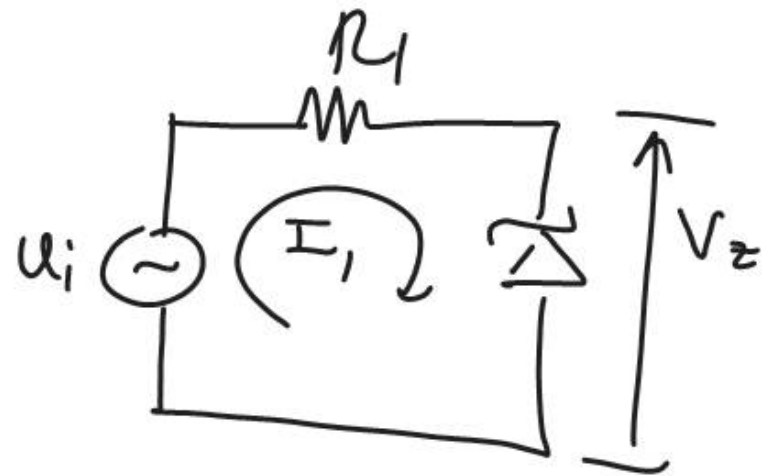
$$I_{1max} = \frac{V_{imax} - V_z}{R_1}$$




$$V_{imin} < u_i < V_{imax}$$

$$V_{imax} = I_{1max} \cdot R_1 + V_z$$
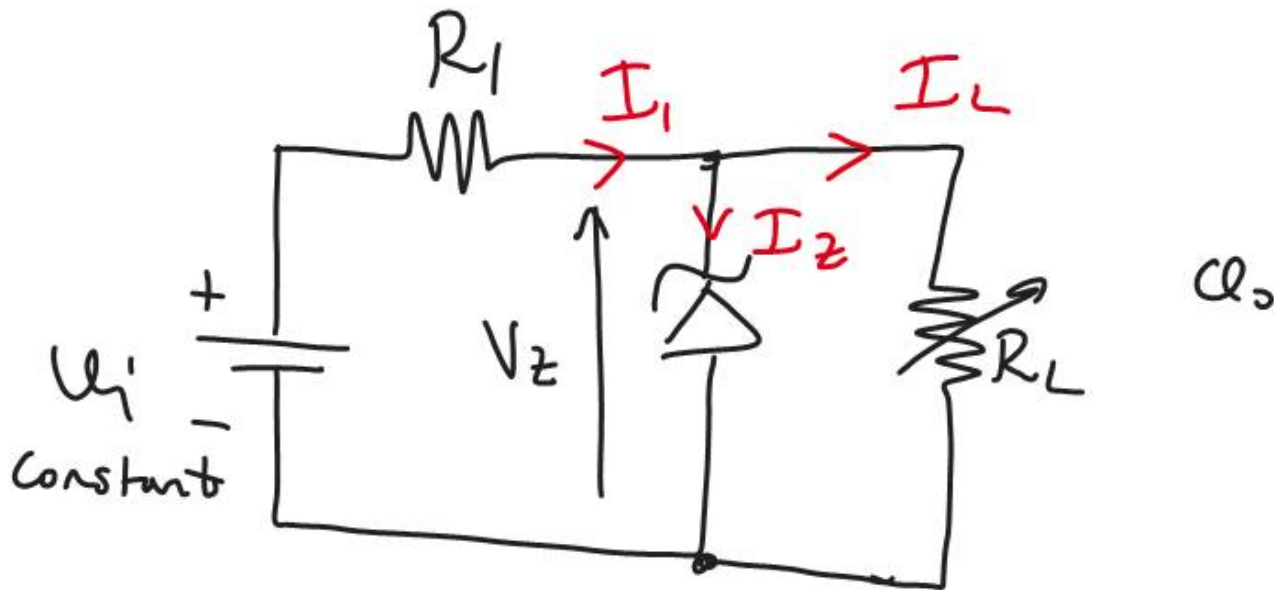
## ② Load Regulation

$V_i$  is constant,  $R_L \rightarrow$  changing



$$I_1 = I_z + I_L$$

as  $R_L \uparrow$   $I_L \downarrow$

$$V_o = V_z = I_L \cdot R_L$$

$$I_L = \frac{V_z}{R_L}$$

since  $\bar{I}_1 = \frac{V_i - V_z}{R_1} = \text{constant}$

$$I_1 = \bar{I}_1 = I_z + I_L$$

$I_z$  should not exceed  $I_{z\text{max}}$

$$\frac{V_1 - V_2}{R_1} = I_{Z_{max}} + I_{L_{min}}$$

$$I_{L_{min}} = \frac{V_1 - V_2}{R_1} - I_{Z_{max}} \Rightarrow R_{L_{max}} = \frac{V_2}{I_{L_{min}}}$$

When  $I_L$  increases  $\Rightarrow$  due to the decrease in  $R_L$

$$\frac{V_{in}}{R_1 + R_L} \cdot R_L \geq V_Z \quad \text{determines } R_{L_{min}}$$

$$V_{in} \cdot R_{L_{min}} = V_Z (R_1 + R_{L_{min}})$$

$$R_{L_{min}} (V_{in} - V_Z) = V_Z \cdot R_1$$

$$R_{L_{min}} = \frac{V_Z \cdot R_1}{V_1 - V_Z}$$

$$R_{L\min} \leq R_L \leq R_{L\max}$$

---