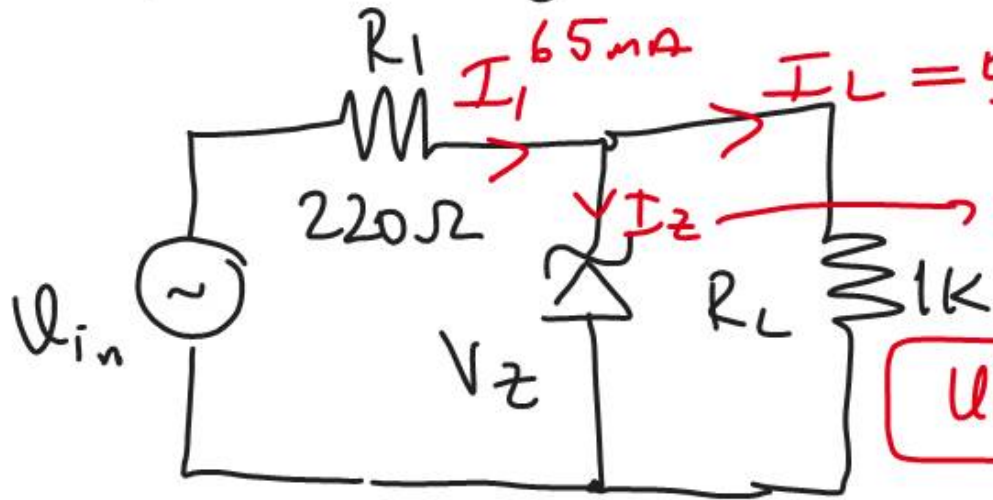


example: $V_z = 5V$
 $I_{zmax} = 60mA$ } are given

15.03.2011
 © CZJ

<Z>

① In the circuit given below determine V_{inmin} , V_{inmax}



$I_L = 5mA = \frac{V_z}{R_L} = \frac{5V}{1k} = \frac{5}{10^3} = 5 \times 10^{-3} A$

$I_{zmax} = 60mA$ given

$U_0 = 65 \times 10^{-3} \times 220 + 5 = 19.3V$

$U_{inmax} = I_{max} \cdot R_1 + V_z = 19.3V$

U_{inmin} :



$I_{1max} = I_{zmax} + I_L = 60mA + 5mA = 65mA$

$U_{inmin} = \frac{V_z}{R_L} (R_1 + R_L)$


$\frac{U_{in}}{R_1 + R_L} \cdot R_L \geq V_z$

$U_{inmin} = \frac{5}{1 \times 10^3} (1 \times 10^3 + 220)$

$U_{inmin} = 6.1V$

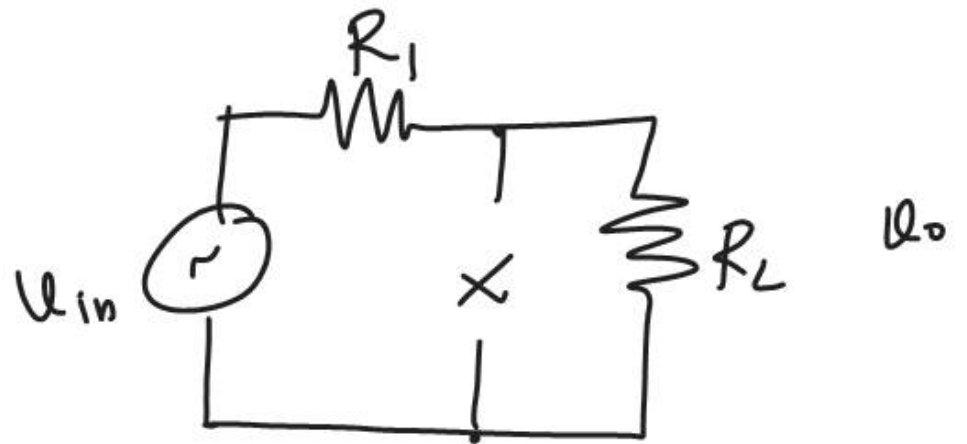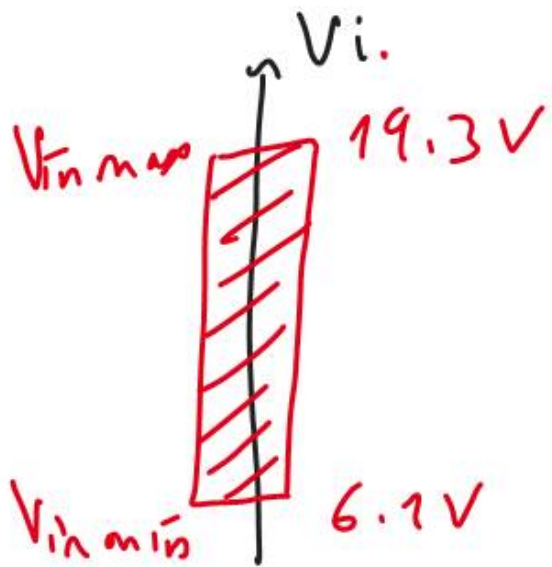

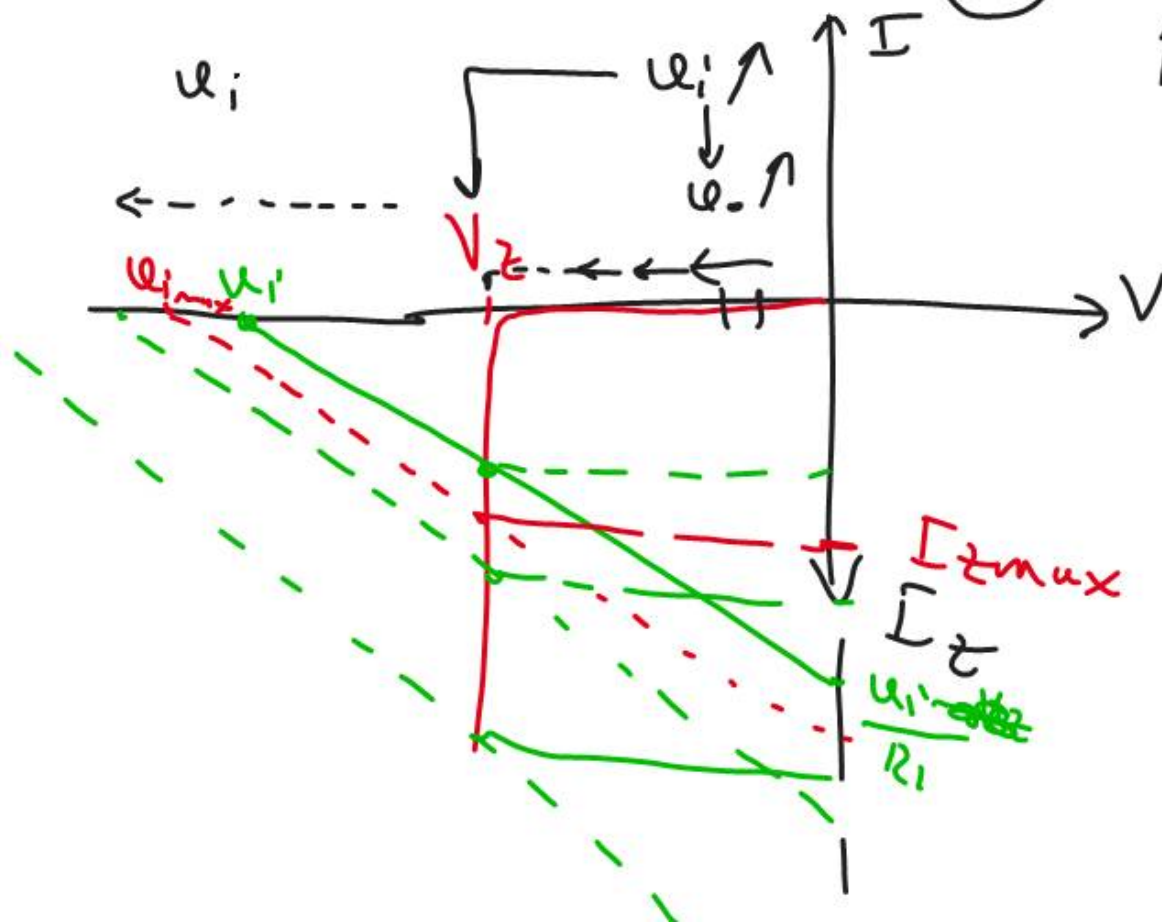
$$U_o = \frac{U_{in} \cdot R_L}{R_1 + R_L}$$



② Determine R_{Lmin} and R_{Lmax} if $V_{in} = 15V$ constant
 LOAD REGULATION

$R_1 = 100 \Omega$
 $I_{Zmax} = 60mA$

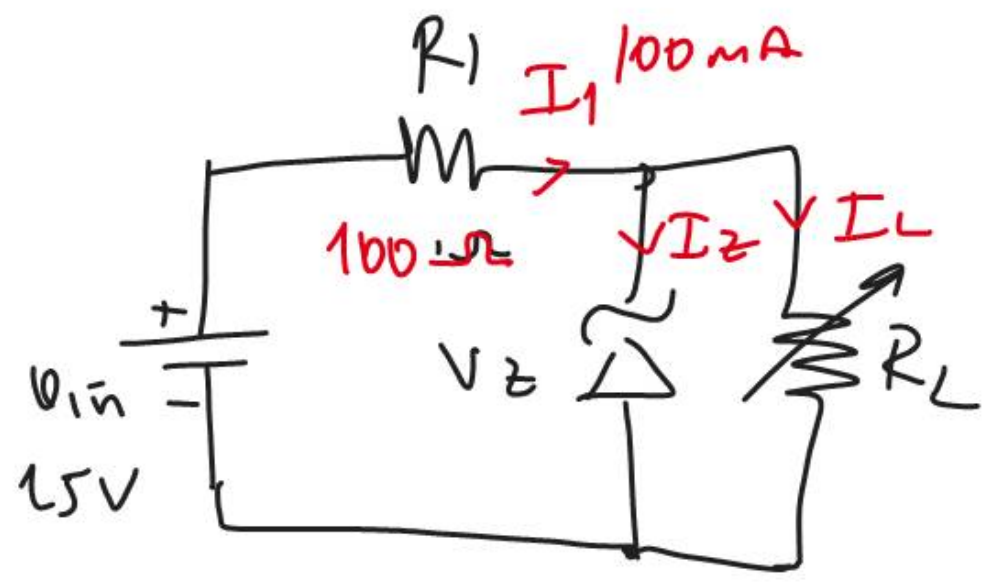

$V_o = V_z = 5V$ (in regulation)

$$I_L = \frac{V_z}{R_L}$$

$$I_1 = \frac{V_{in} - V_z}{R_1} = \frac{15 - 5}{100} = \frac{10}{100} = 0.1 = 100mA$$

$I_{Zmax} = 60mA$ $I_1 = 100mA = 60mA + I_L$

$I_{Lmin} = 40mA$ $R_{Lmax} = \frac{V_z}{I_{Lmin}} = \frac{5V}{40 \times 10^{-3}} = \underline{\underline{125 \Omega}}$

$R_{L \min}$:

$$\frac{V_{in}}{R_1 + R_L} \cdot R_L \geq V_Z$$



$$\frac{15V}{R_1 + R_L} R_L = V_Z$$

$$R_L \cdot 15 = V_Z \cdot R_1 + V_Z \cdot R_L$$


$$R_L (15 - V_Z) = V_Z \cdot R_1$$

$$R_L (15 - 5) = 5 \cdot 100$$

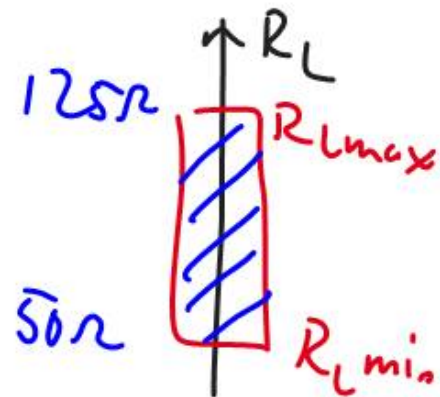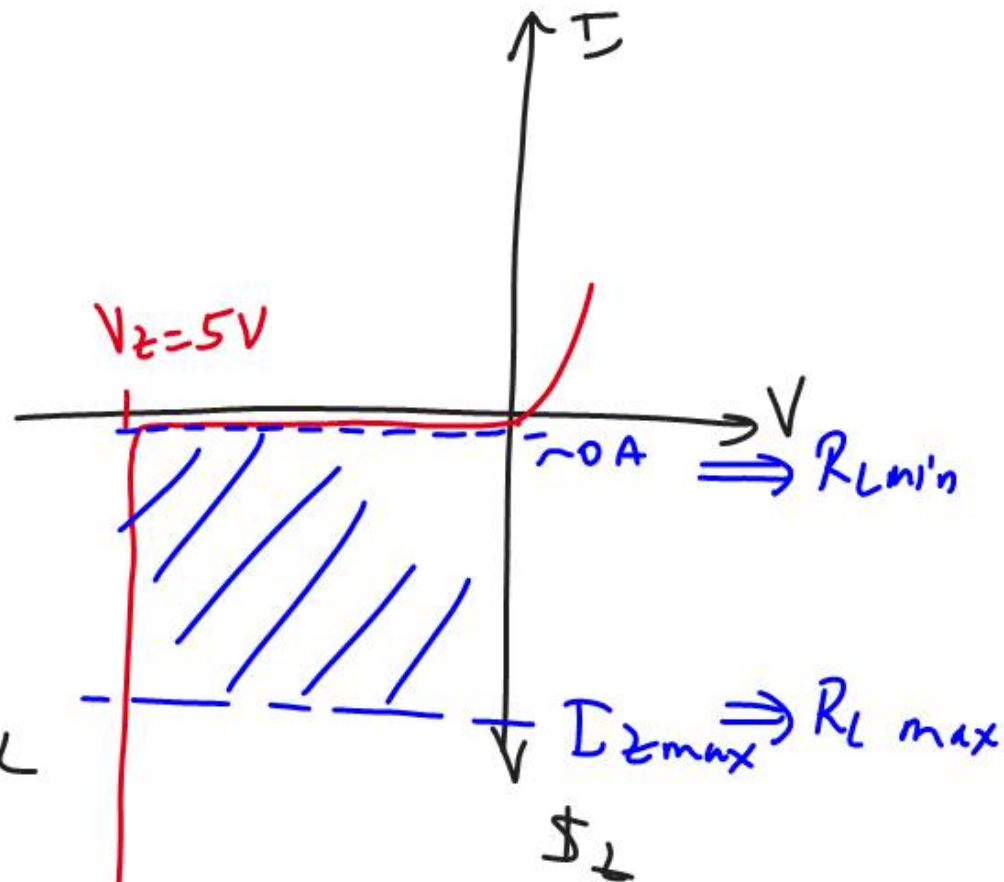
$$R_{L \min} = \frac{5 \times 100}{10} = \underline{50 \Omega}$$



ex:

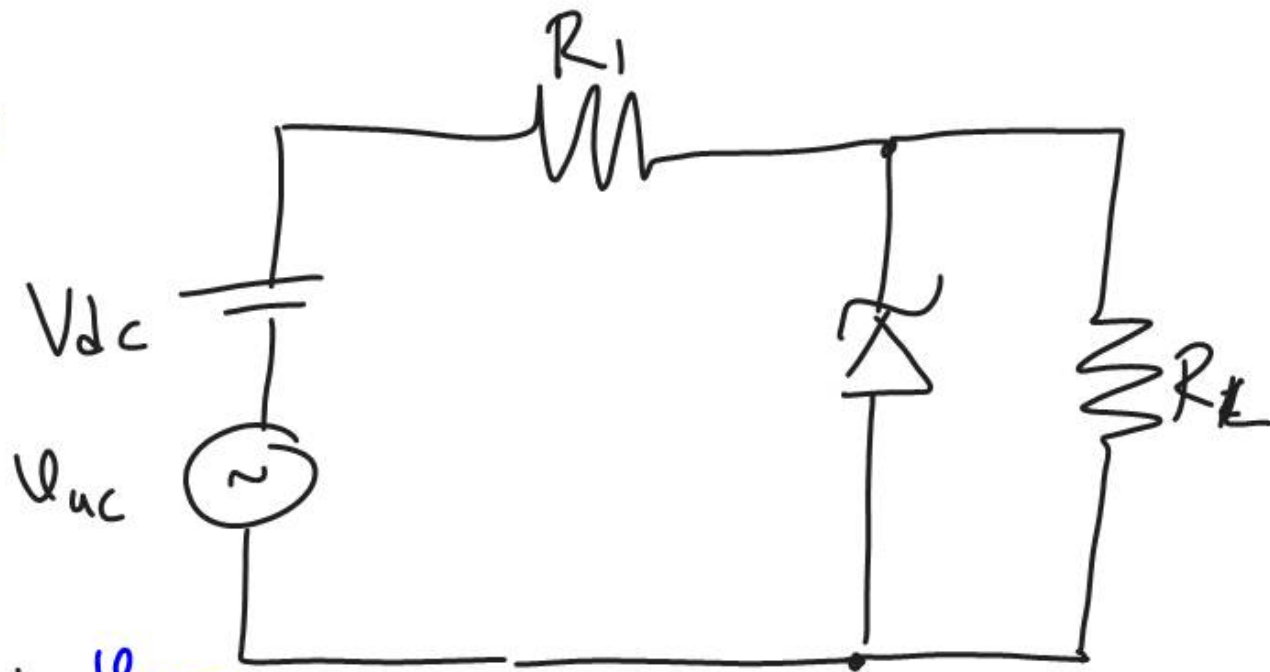

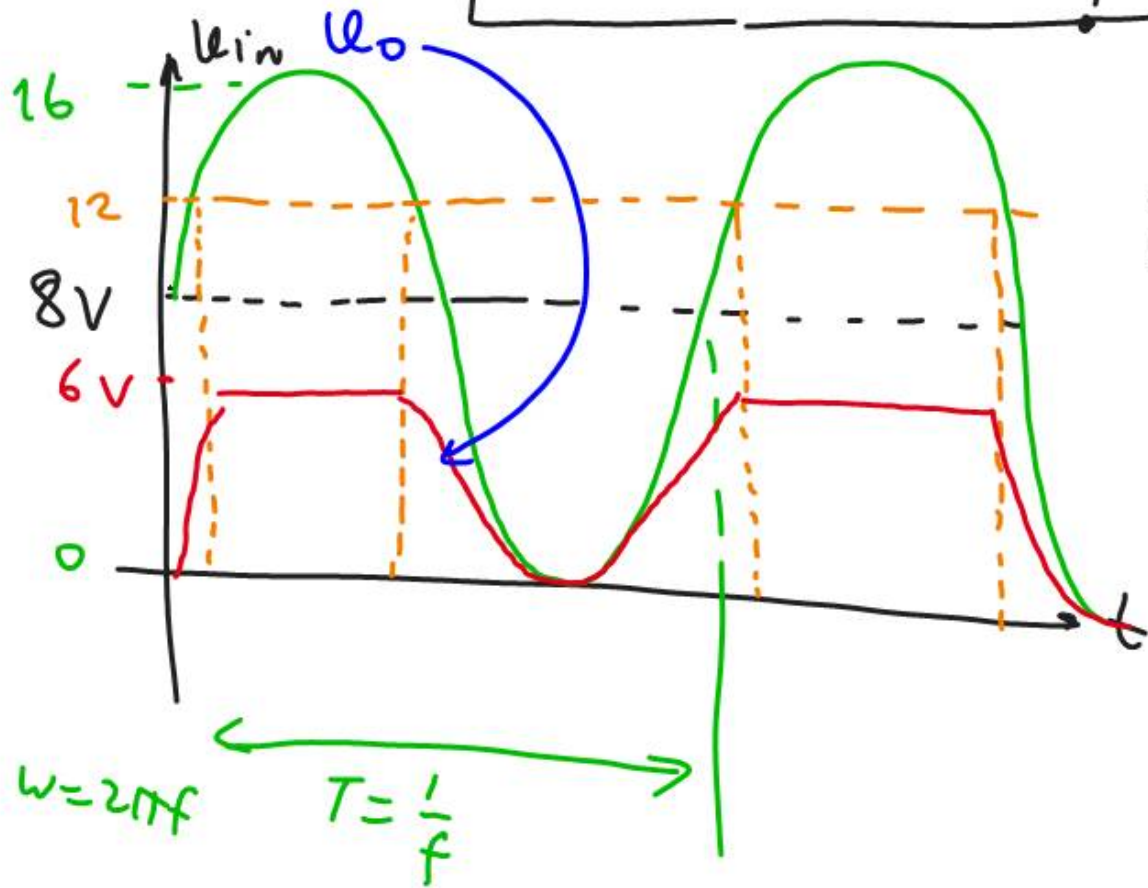$V_z = 6V$
 $R_1 = R_L$
 $U_{in} = 8.0V(1 + \sin \omega t)$
 $U_o = ?$




$$\frac{U_{in}}{R_1 + R_L} \geq V_z$$

$$\frac{U_{in}}{2} \geq V_z$$

$$U_{in} \geq 2V_z$$

$$U_{in} = 12V \Rightarrow U_o = V_z$$

When $U_{in} < 12V$

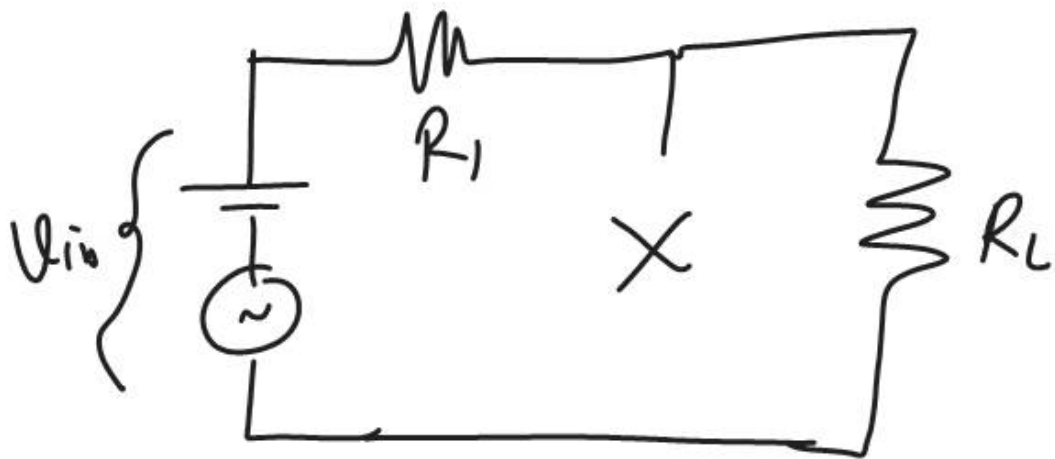


U_o


$$U_o = \frac{U_{in}}{R_1 + R_L} \cdot R_L$$

$$U_o = \frac{U_{in}}{2}$$

A Voltage Regulator:

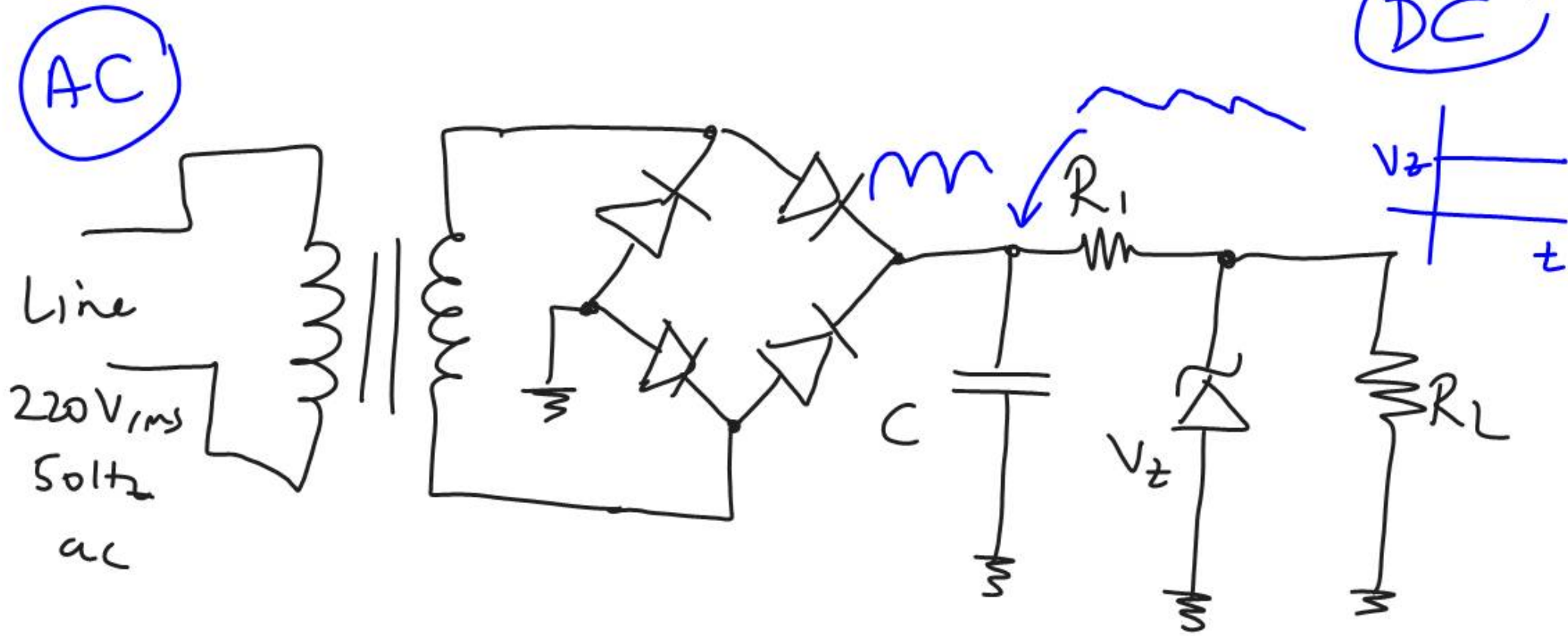


Integrated Circuit Regulators (IC)

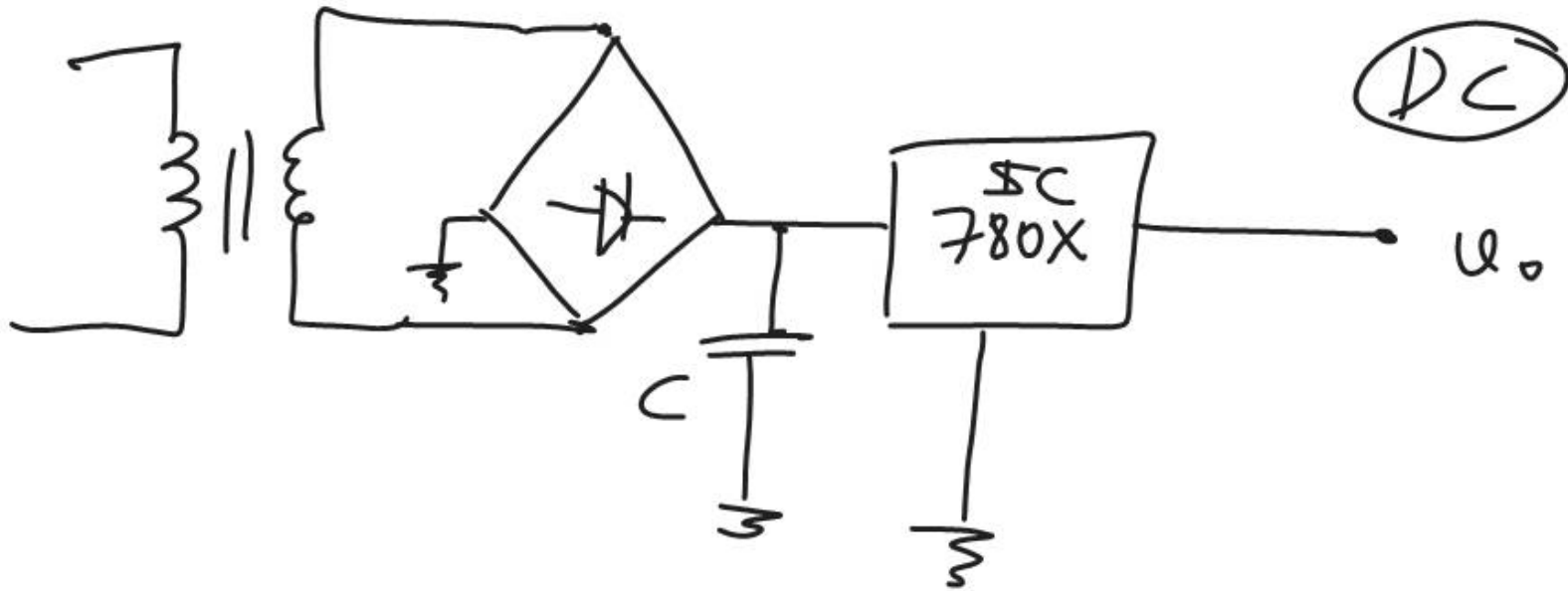

7805 \rightarrow 5V

7807 \rightarrow 7V


790X \rightarrow -XV.

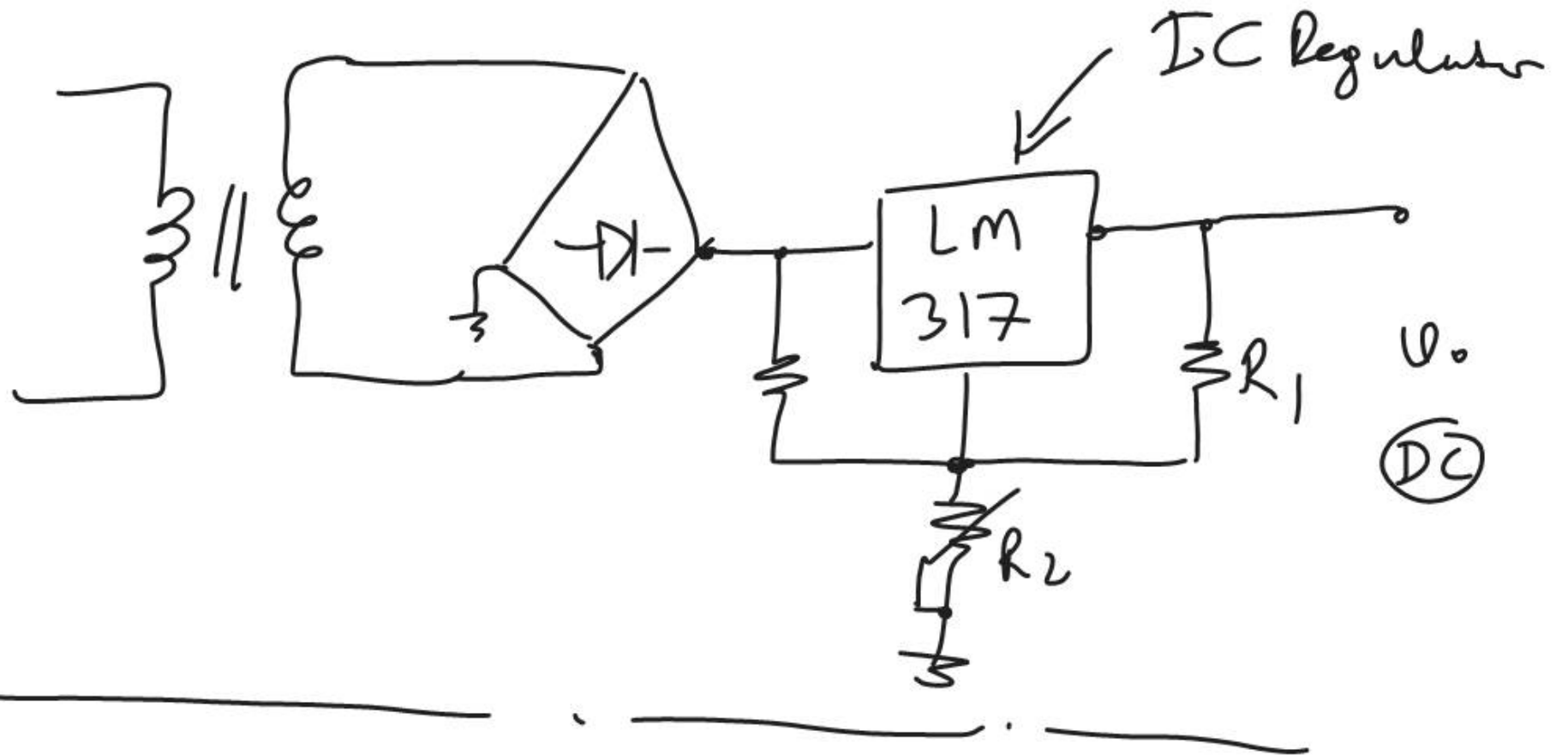

→ SWITCHING REGULATORS

OTHER DIODES

- Light Emitting Diode (LED)

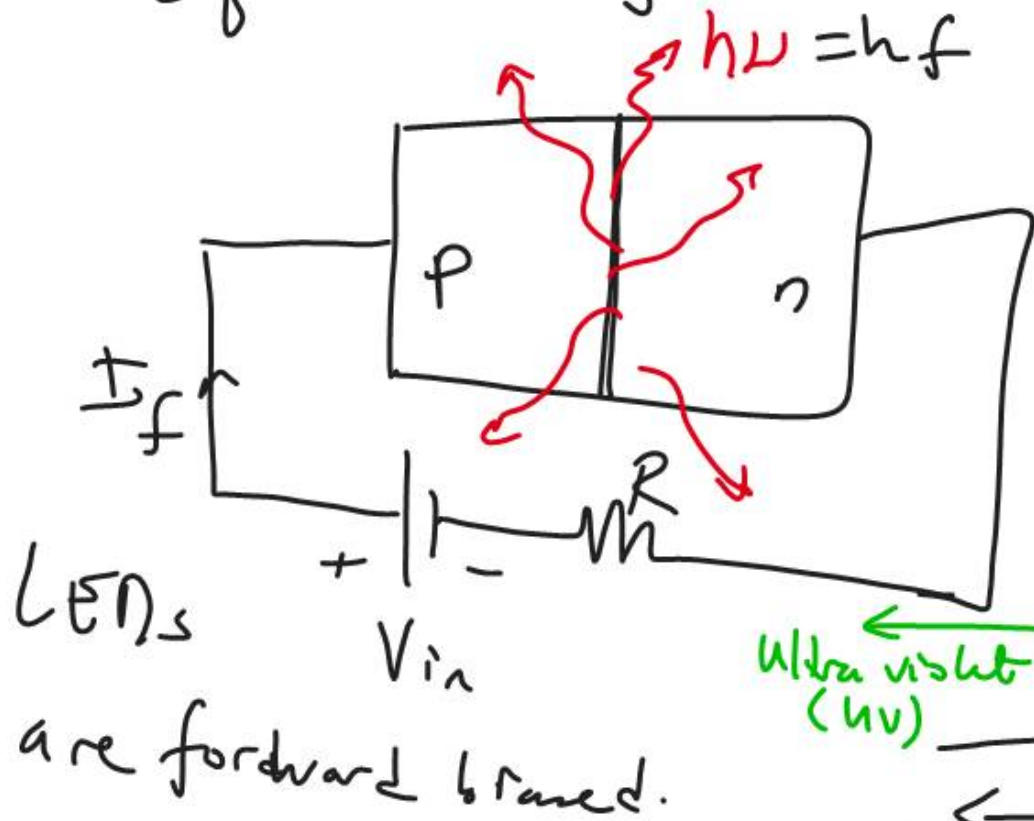


$$\lambda = \frac{c}{f}$$

$3 \times 10^8 \text{ m/s}$
speed of light

$$\lambda \cdot f = c \text{ (m/s)}$$

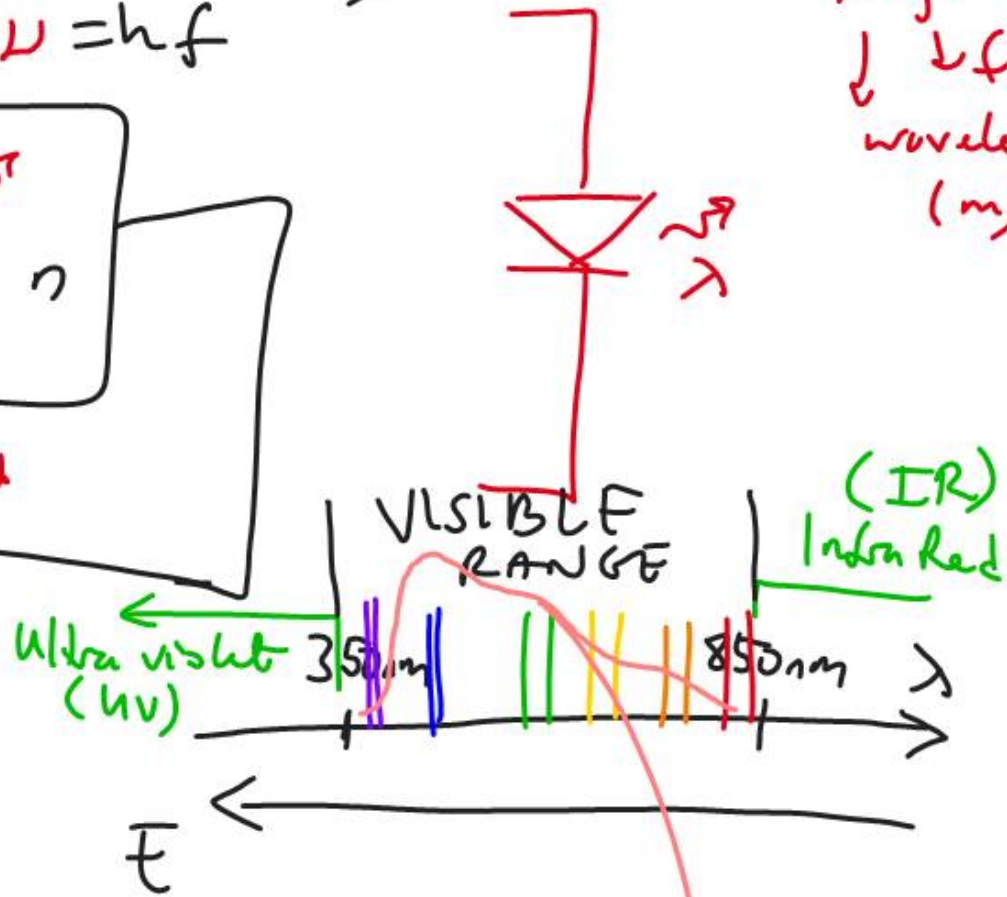↓ ↓ frequency ($\frac{1}{s}$)
wavelength (m)




$$E = hf = h \cdot \frac{c}{\lambda}$$


GaAs LED → will emit RED light

GaN LED → " " BLUE "


AlGaAs - GaAs LEDs → RED, yellow, amber

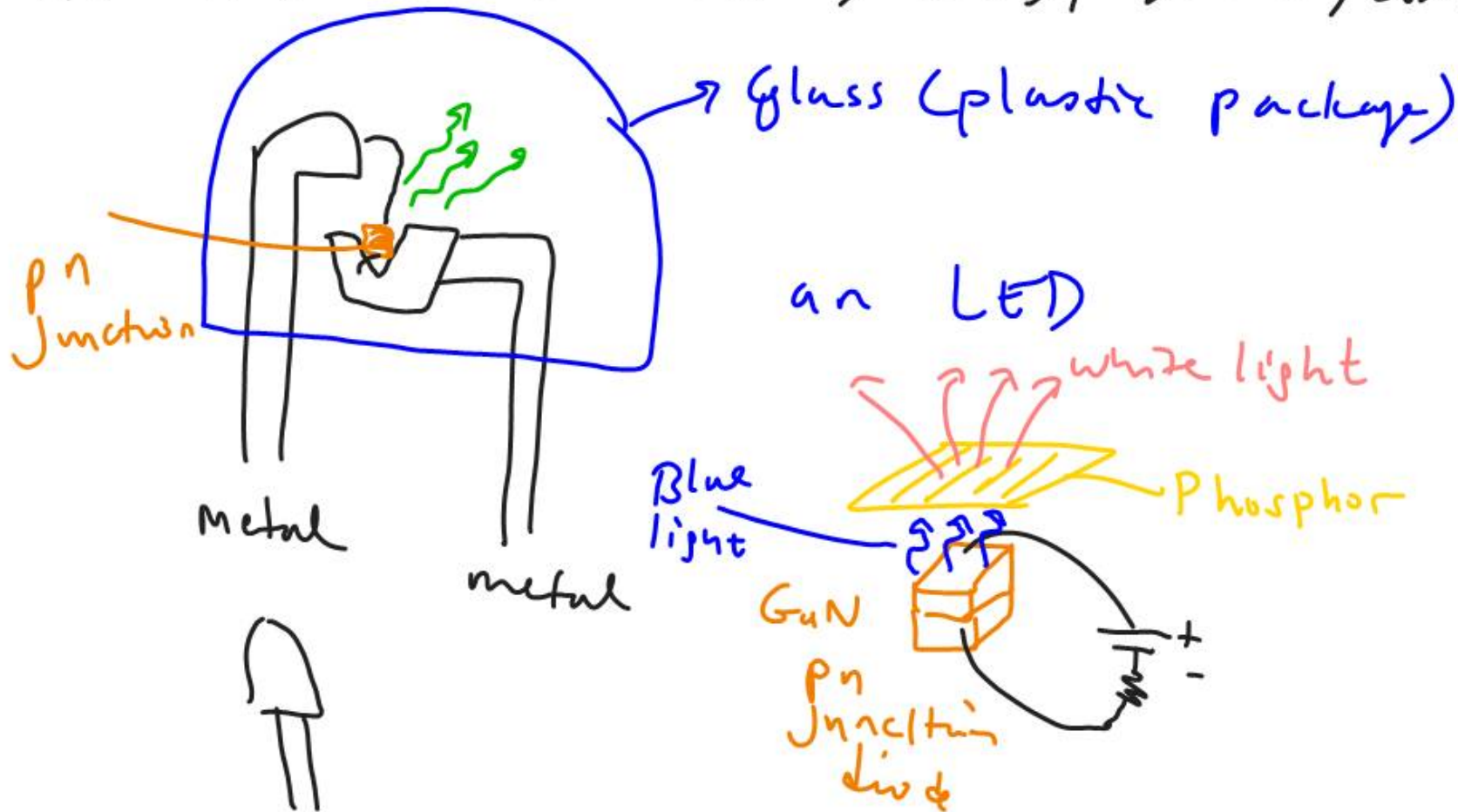

A PHOTODIODE

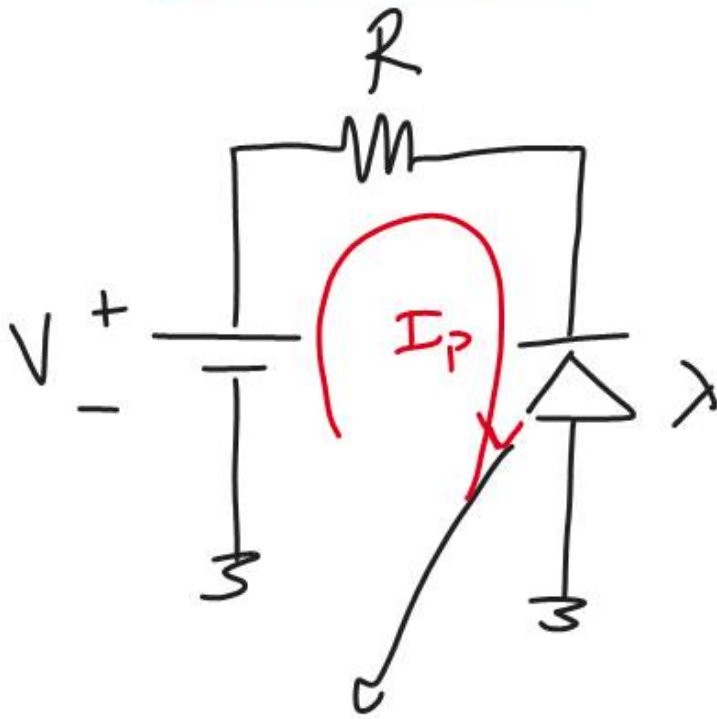

Photodiodes are always
Reverse-biased

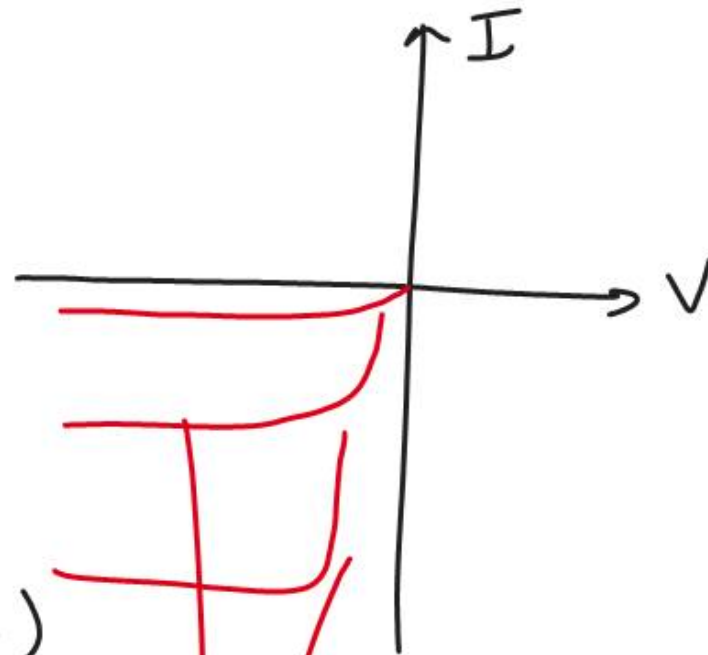

a photodiode
generates current (I_p)
when a proper photon
falls on it.

Light energy
increases

