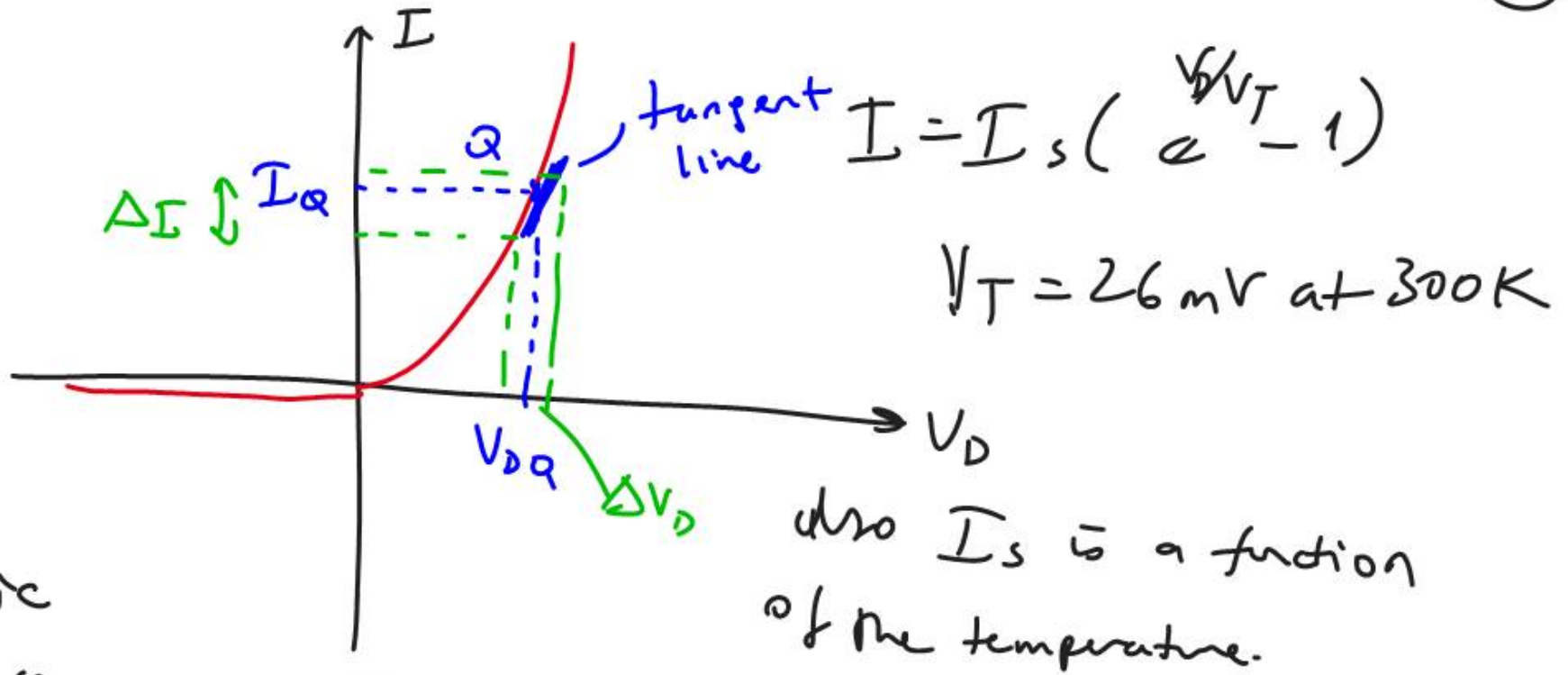


DIODE EQUATION

22.02.2011
©



Dynamic
Resistance
of a diode: r_d

Q = quiescent

Slope of the tangent $\equiv \left. \frac{\Delta I}{\Delta V_D} \right|_Q = \frac{dI}{dV_D}$


$$\frac{dI}{dV_D} = \frac{d}{dV_D} \left[I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \right] = \frac{I_S}{V_T} e^{\frac{V_D}{V_T}} = \frac{1}{V_T} \left(I_S e^{\frac{V_D}{V_T}} \right)$$

$$\frac{dI}{dV_D} \approx \frac{I}{V_T} \quad \rightarrow \quad \approx I$$


$$r_d = \frac{dV_D}{dI} \approx \frac{V_T}{I}$$

$$r_d \approx \frac{V_T}{I}$$


A pn Junction diode

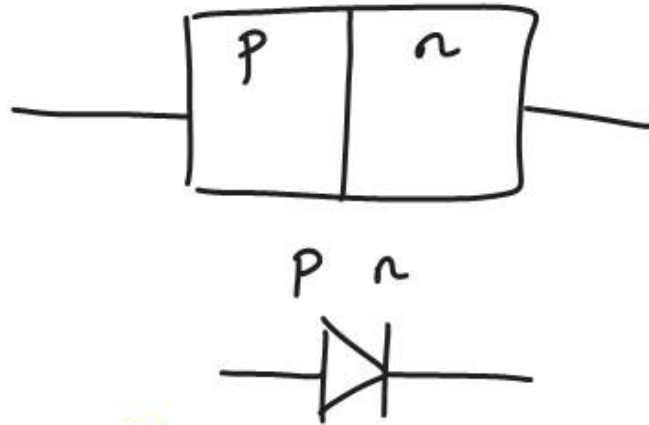

historical diode tube

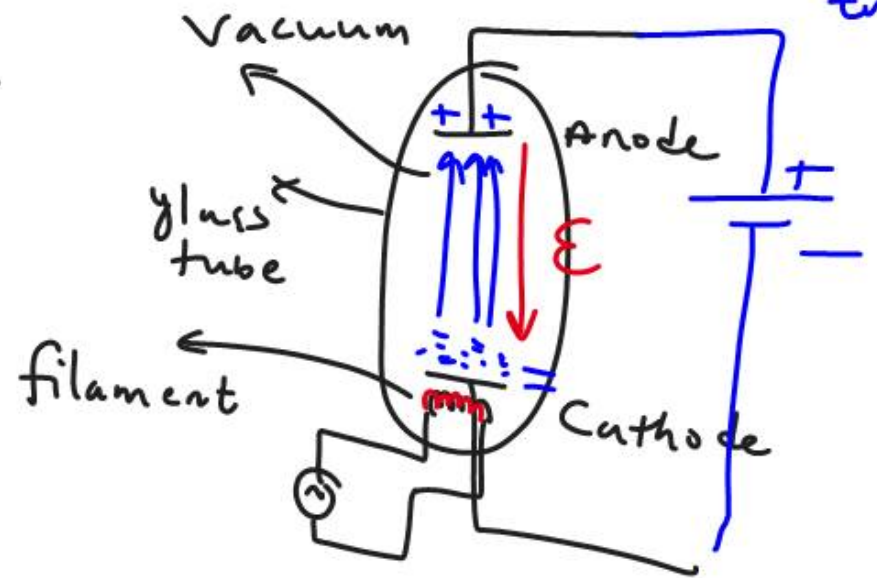



A diode circuit:

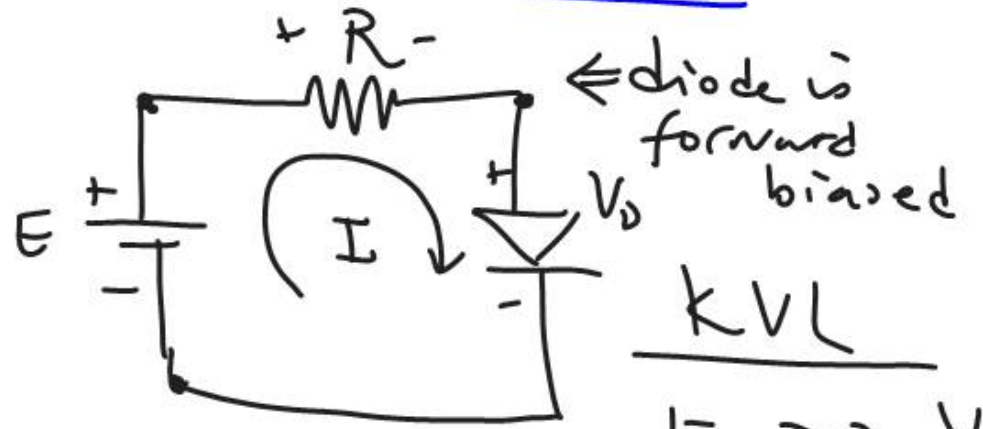

KVL

$$E - I \cdot R - V_D = 0$$


DIODE BIAS

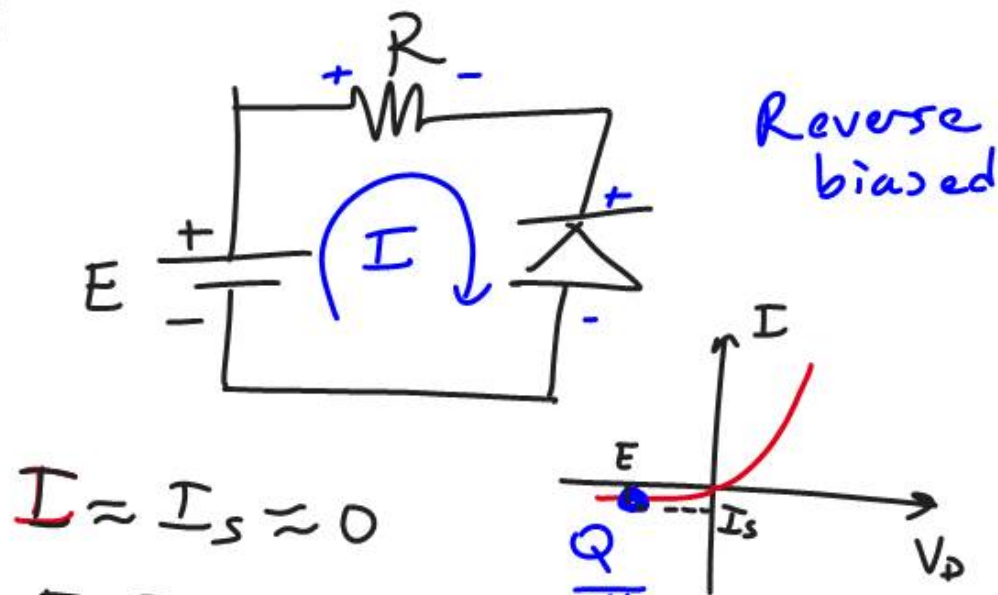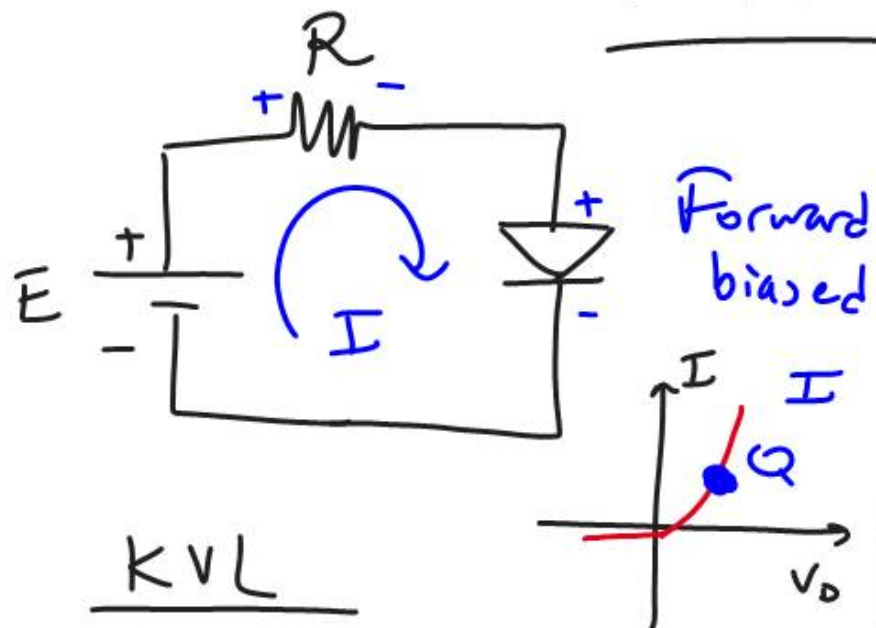

$$I \approx I_S \approx 0$$

$$E - I \cdot R - V_D = 0$$

$$V_D \approx E$$

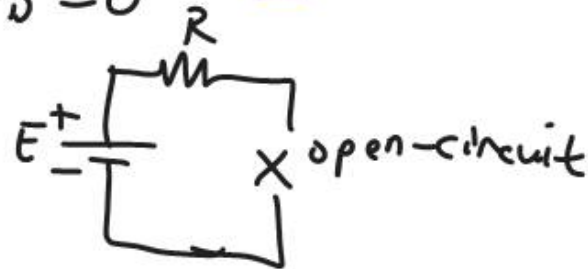

KVL


$$E - I \cdot R - V_D = 0$$

2 unknowns: I, V_D

We need another equation.

- ① The curve (The diode characteristic) \Rightarrow Graphical solution
- ② Use the diode equation ($I = I_S e^{V_D/V_T - 1}$)
- ③ Approx. Take $V_D = 0.7V$ for Si

① Graphical Solution

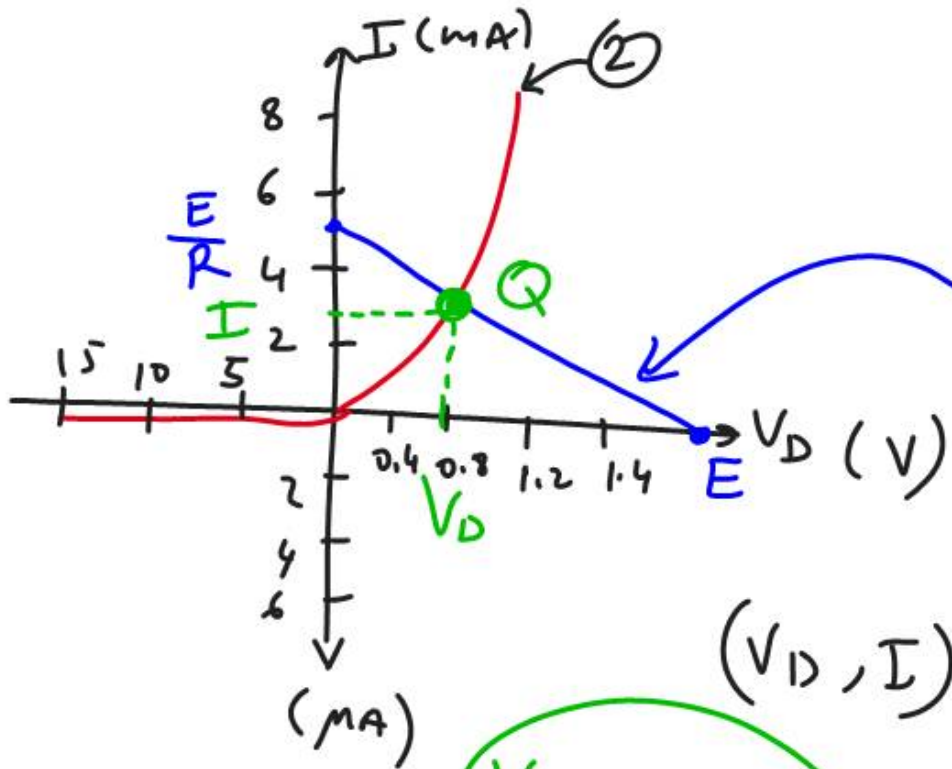

KVL:
 $E - I \cdot R - V_D = 0 \quad (1)$
 Line equation $y = ax + b$
 $\downarrow \quad \downarrow$
LOAD LINE $I \quad V_D$

$I = 0 \quad V_D = E$
 $V_D = 0 \quad I = \frac{E}{R}$

$(V_D, I) \Rightarrow (0, \frac{E}{R}), (E, 0)$

$V_D \approx 0.8V$
 $I \approx 3mA$

② DIODE EQUATION SOLUTION

Our objective is
to find I , V_D

$$E - I \cdot R - V_D = 0 \quad \text{①}$$

$$I = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \quad \text{②}$$

→ This is NOT a linear equation!

2 unknowns, 2 equations ✓

$$I = \frac{E - V_D}{R} \quad \text{substitute this into ②}$$

$$\frac{E - V_D}{R} = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

$$V_T = 26 \text{ mV}$$

$$I_S = 1 \mu\text{A}$$

$$E = 1.5 \text{ V}$$


$$R = 500 \Omega$$

③ Approximation

⑥ $V_D \approx 0.7V$ (Si) $V_D \approx 0.3V$ (for Ge), $V_D \approx 1.2V$ (for GaAs)


⑦ $E - I \cdot R - V_D = 0$
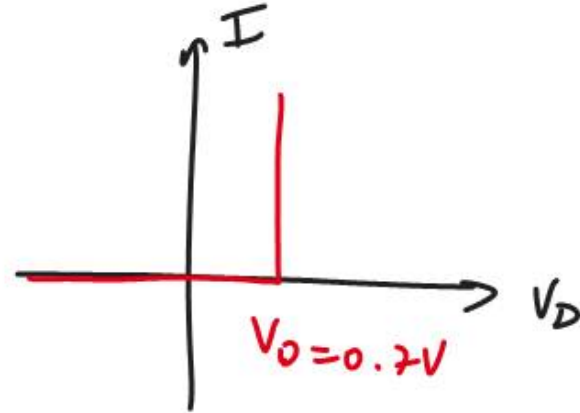
$$\boxed{I = \frac{E - V_D}{R}}, \quad V_D = 0.7V.$$




④ Very big approximation
 $V_D \approx 0V.$

$$I = \frac{E}{R}$$

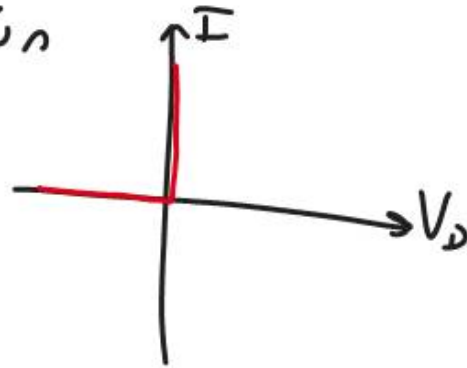

ex

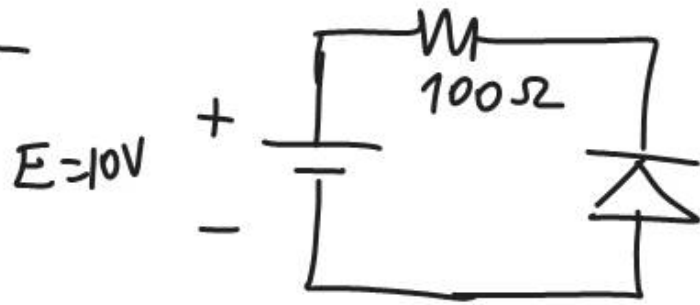


$$V_D = ? \approx 10V$$

$$I = ? \approx 0$$

Diode is reverse biased.

ex

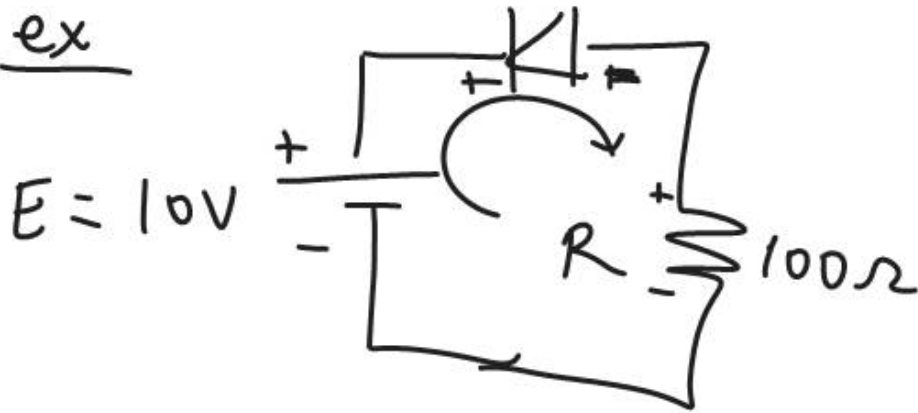

$$V_D = ?$$


$$V_D = E = 10V$$

Reverse biased

$$I = ?$$

$$I = 0$$

ex

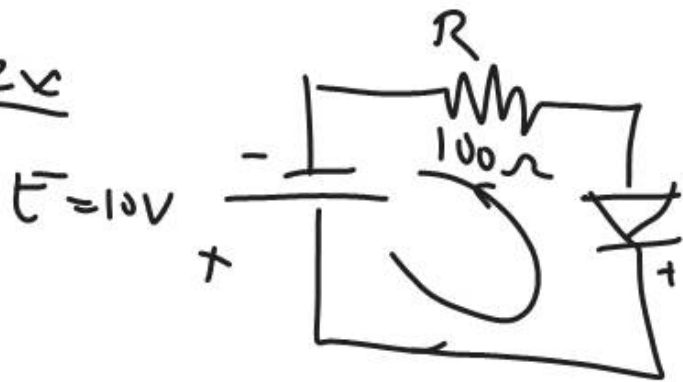

$$V_D = ?$$


$$V_D = E = 10V$$

$$I = ?$$

$$I = 0$$

Reverse biased

ex

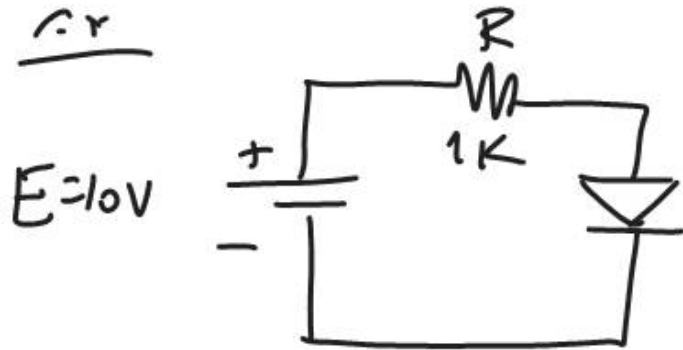

$V_D = ?$
 $I = ?$

Forward biased.


$V_D \approx 0.7V$

$I = \frac{E - V_D}{R} = \frac{10 - 0.7}{10^3} = \underline{9.3mA}$

Assume $V_D \approx 0.7V$
 when forward biased

$1k \Omega = 1000 \Omega = 10^3 \Omega$


ex

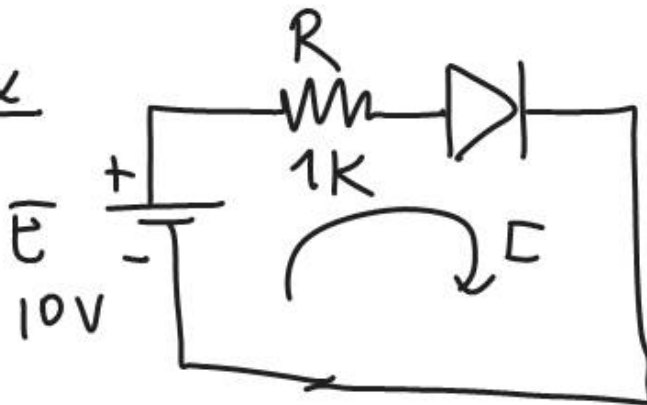


$I = ?$ $E - V_D - IR = 0$

$V_D = ?$ $I = 0$ $V_D = E = 10V$

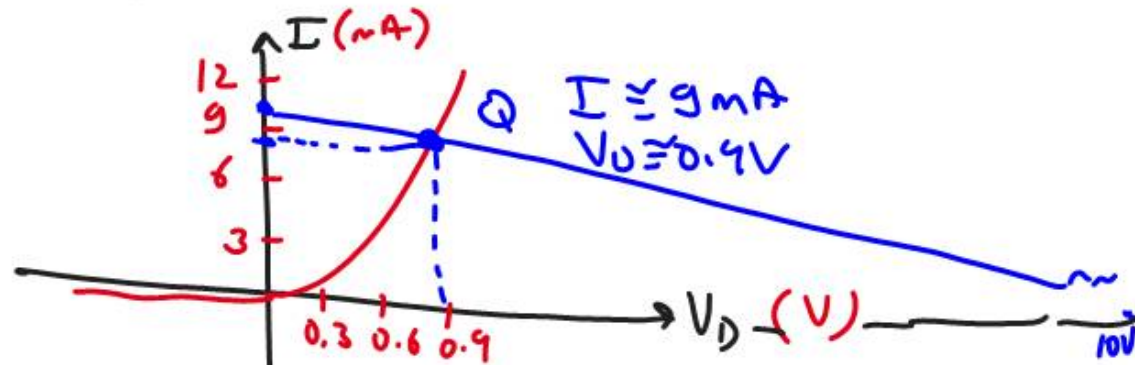$V_D = 0$ $I = \frac{E}{R} = \frac{10}{10^3} = 10mA$



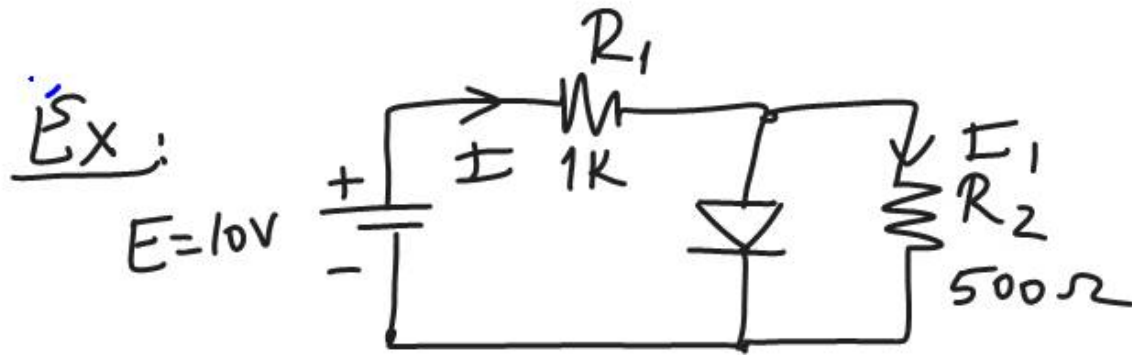

$$I = ? , I_1 = ?$$

$$V_D = ? \text{ (si)}$$

$$V_D \approx 0.7V$$



KVL

$$E - I \cdot R_1 - V_D = 0$$

$$I = \frac{E - V_D}{R_1} = \frac{10 - 0.7}{10^3} = 9.3 \text{ mA}$$

$$I_1 = \frac{V_D}{R_2} = \frac{0.7V}{500\Omega}$$

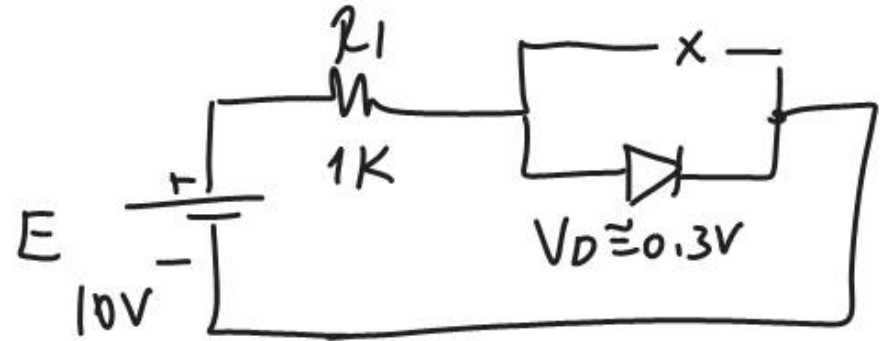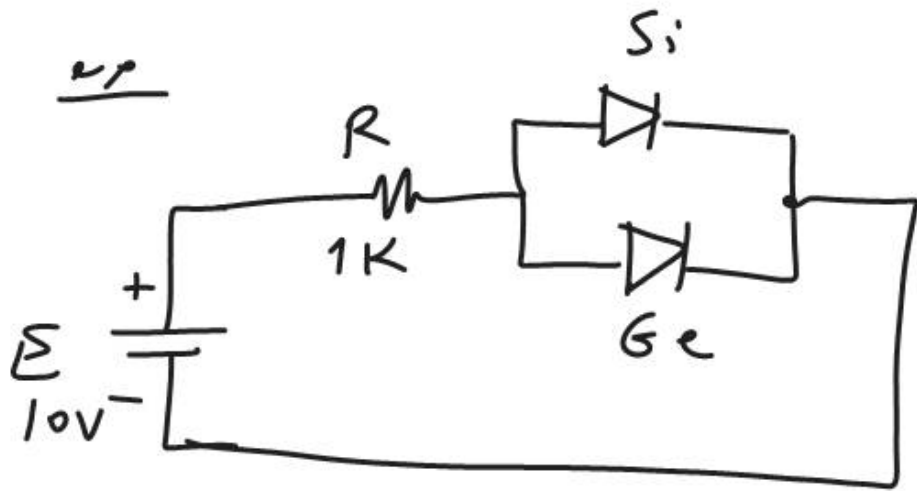
$$I_1 = \frac{1.4}{1000} = 1.4 \text{ mA}$$





$$I = \frac{E - 0.3V}{R}$$

$$\approx \frac{10 - 0.3}{103} \approx 9.2 \text{ mA}$$


$$V_D \approx 0.3V$$

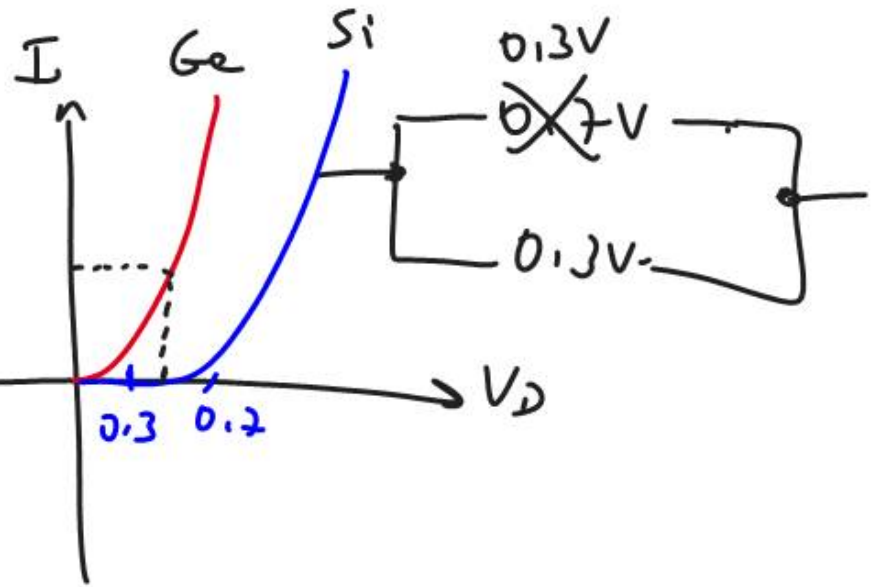

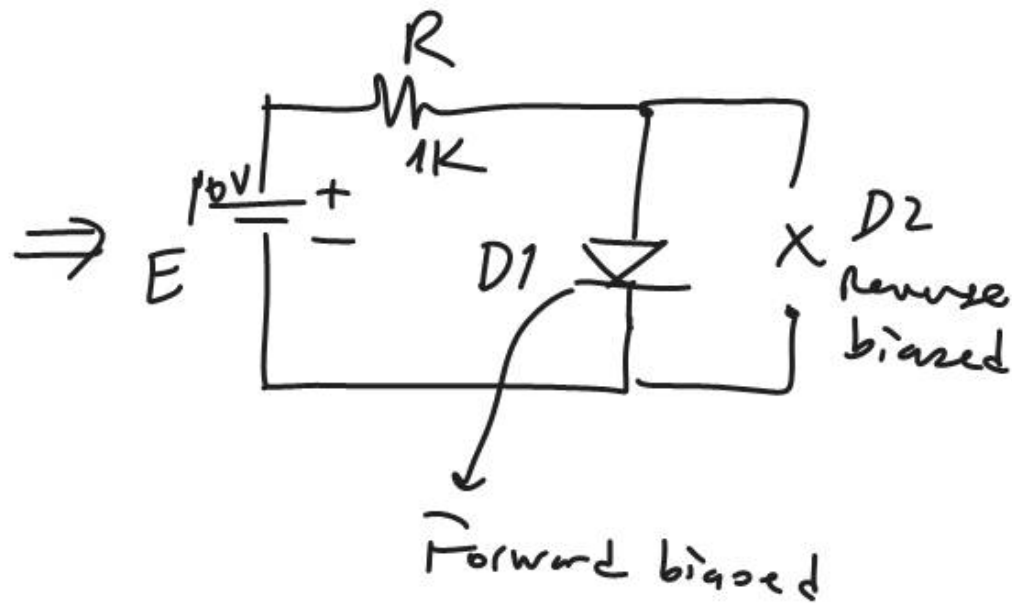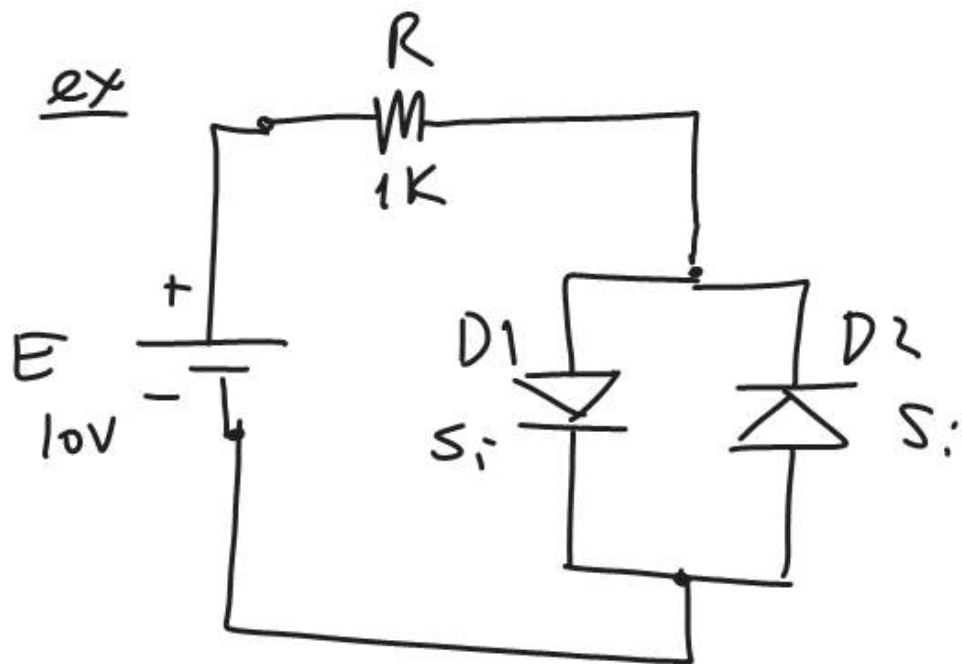


$$I = \frac{E - V_D}{R} = \frac{10 - 0.7}{10^3} = 9.3 \text{ mA}$$

$$V_D \approx 0.7 \text{ V}$$

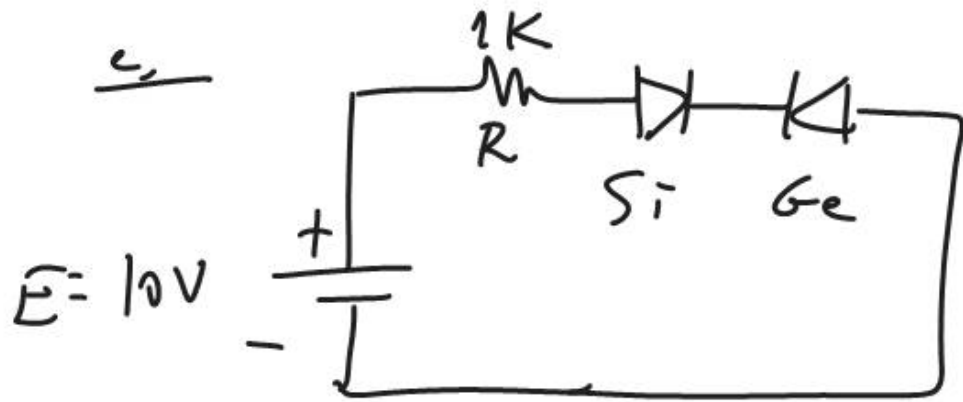

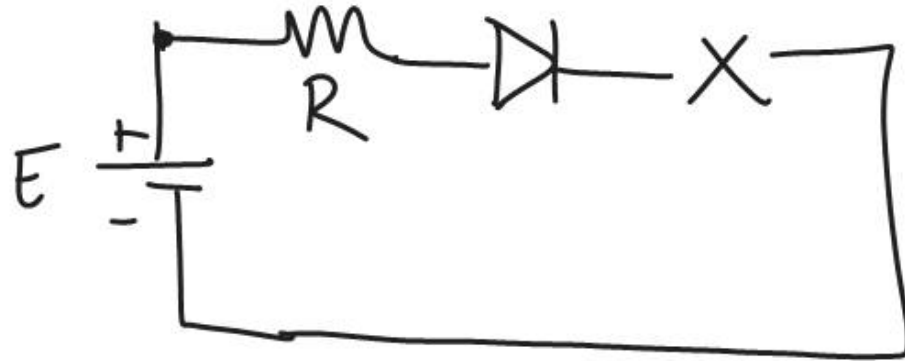Si is forward biased
Ge is reverse biased






$$I = 0$$

$$V_D = ?$$

$$V_D = V_{D1} + V_{D2} \cong E \cong 10V$$

CLIPPERS & CLAMPERS


CLIPPERS

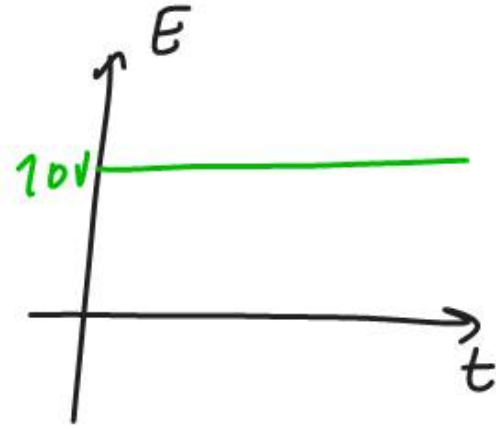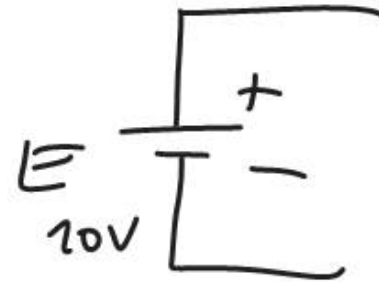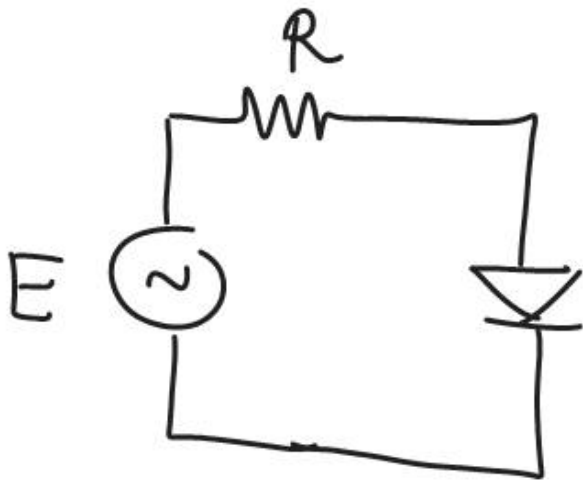

Direct Current (DC)
Voltage

$$E = V_m \sin \omega t = V_m \sin 2\pi f t$$

$T = \text{period (second)}$

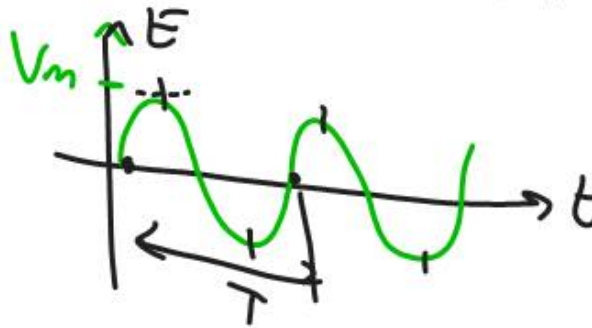

$$f = \frac{1}{T} \quad (\text{1/second} = \text{cycles} = \text{Hz})$$

