

Number: \_\_\_\_\_

Name: \_\_\_\_\_

ECE 246  
FINAL EXAM


07.06.2012

Exam is closed-book/notebook. You can use exA-3 full of your handwritten notes (photocopy is not allowed). No mobile device will be used. You can use a calculator. There are 4 questions. Please print your name on every page. Also fill in the answer boxes given. Solve every question in the space given. No answer on the question pages. Exam duration 2.5 hours. Use the universal characteristics given for FET calculations.

Question ①

For the circuit given below calculate

- a)  $I_{C2}$
- b)  $V_{CE2}$ .

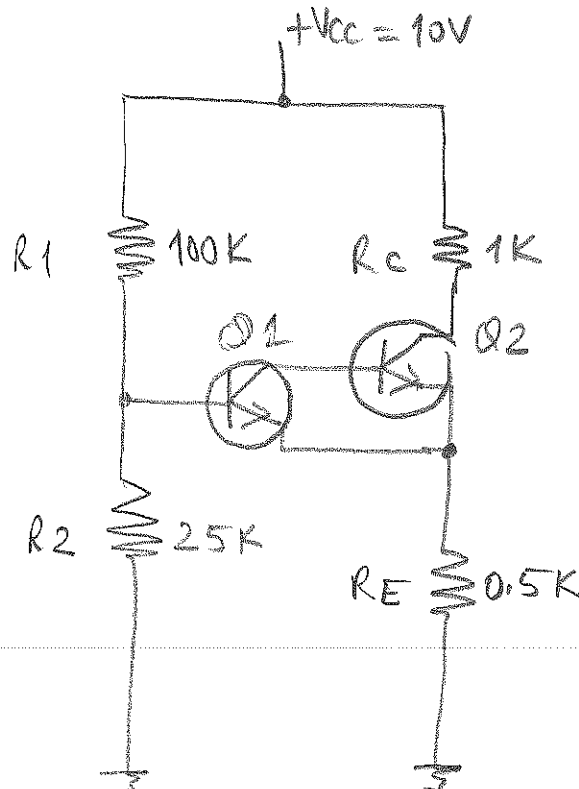


Q1 and Q2 are identical transistors.  
 $V_{BE1} = V_{BE2} = 0.6V$   
 $\beta_1 = \beta_2 = 20$   
 $T = 300K$

Answer (1):

$I_{C2}$	$V_{CE2}$

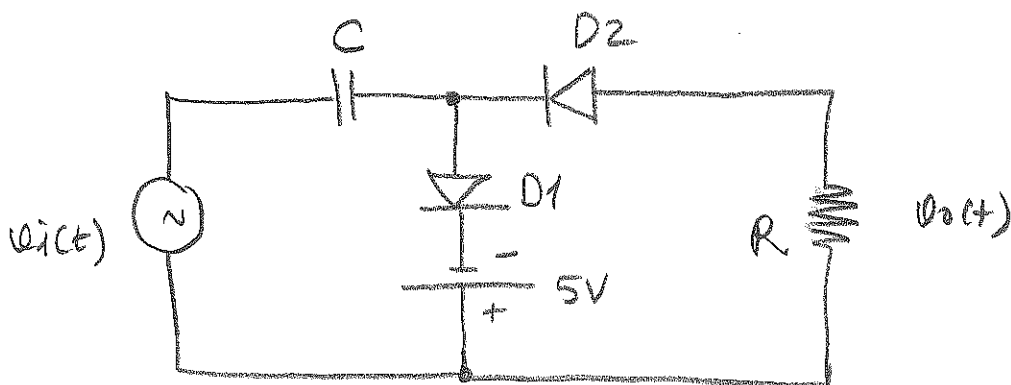Question (2)

For the circuit given below sketch the output signal.




$$v_i(t) = 10 \sin 200\pi t$$

$$R = 10K$$

$$C = 100nF$$

Diodes are ideal.


Answer (2)

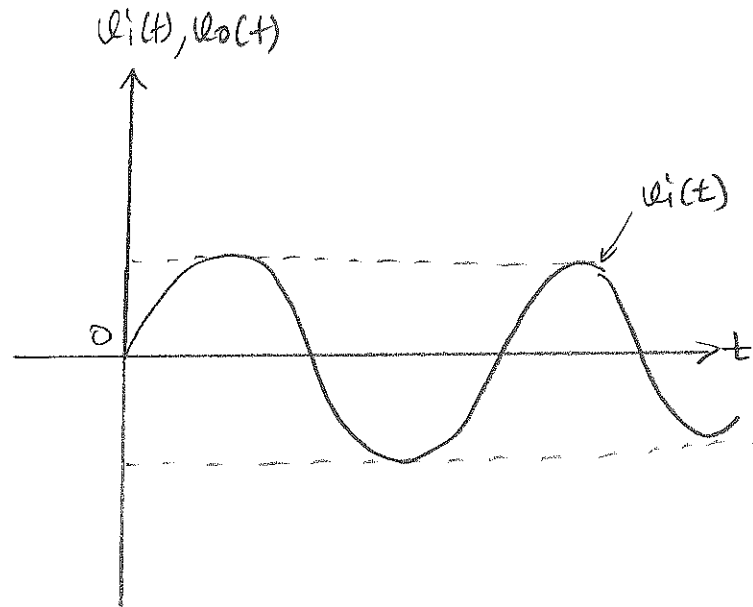

Question (3) For the amplifier circuit given below, calculate

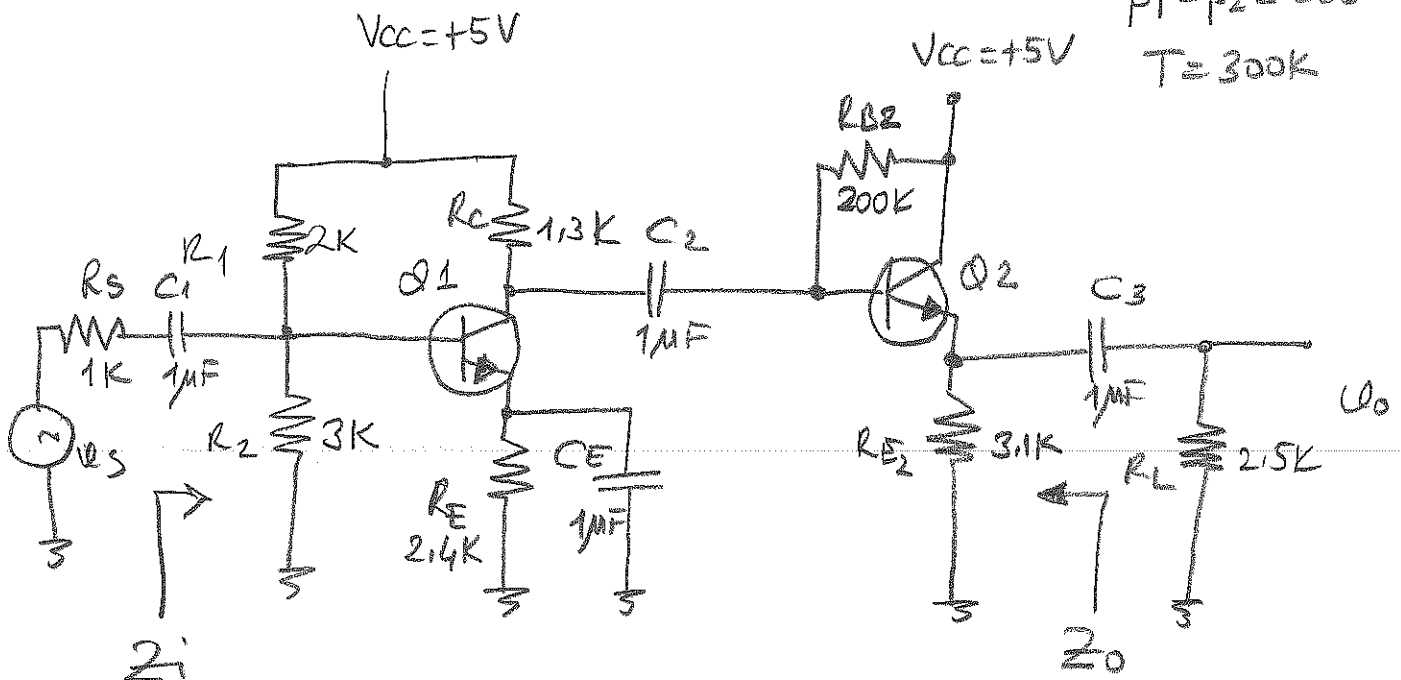- a) The overall voltage gain  $A_{VT} = \frac{v_o}{v_s}$   
 b)  $Z_i$  and  $Z_o$ .

$V_{BE1} = V_{BE2} = 0.6V$   
 $\beta_1 = \beta_2 = 200$   
 $T = 300K$



Answer ③

Answer (3) - continued

Fill the table:


$I_{E1}$	$I_{E2}$	$r_{e1}$	$r_{e2}$	$A_{v1}$	$A_{v2}$	$A_{v3}$	$A_{vT}$	$Z_i$	$Z_o$

Answer (3) - continued

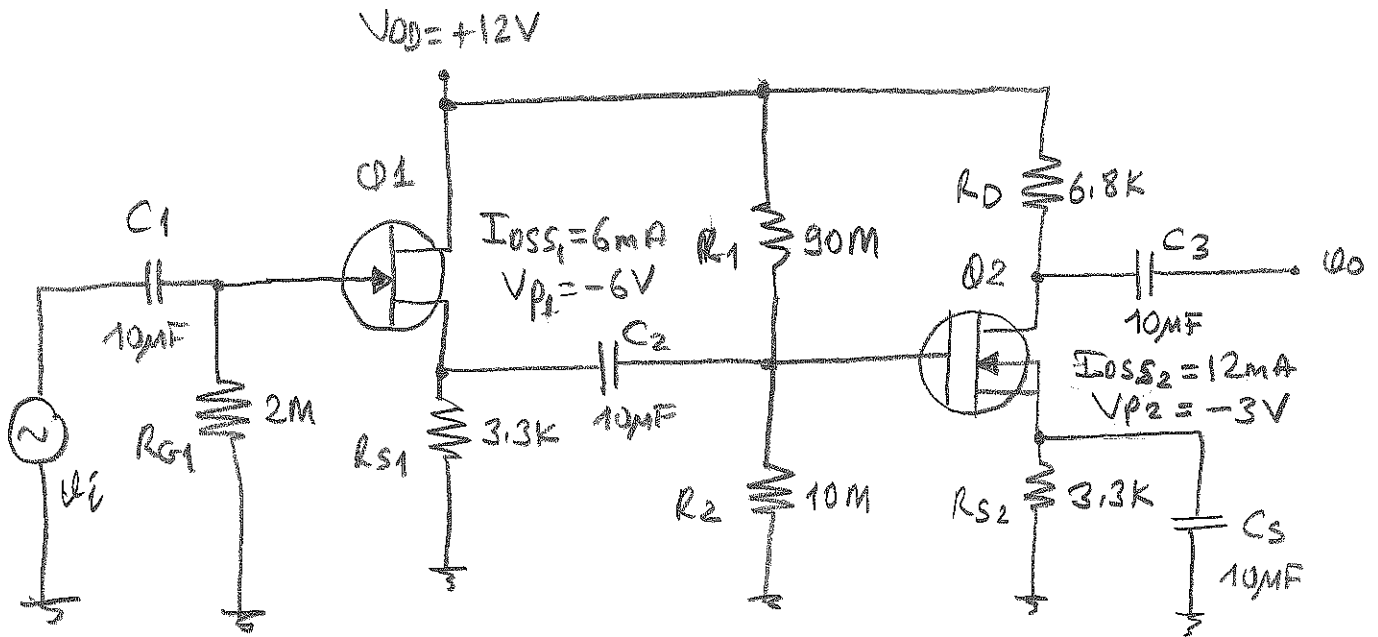Question (4)

For the circuit given below, calculate the

overall gain  $A_{vT} = \frac{V_o}{V_i}$ .




Answer ④

Answer (4) - continued


Fill the table:

$V_{GSQ1}$	$V_{GSQ2}$	$g_{m1}$	$g_{m2}$	$A_{U1}$	$A_{U2}$	$A_{UT}$



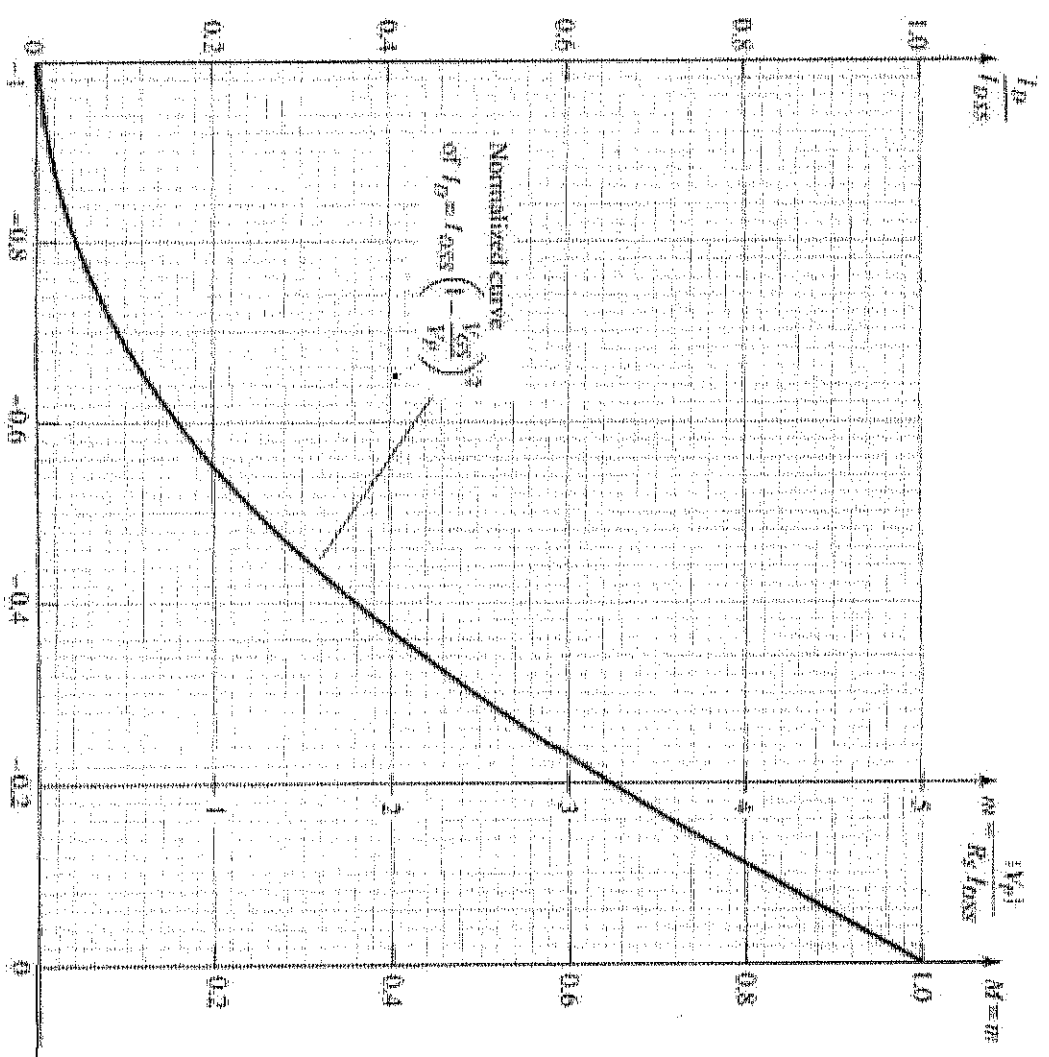

3 (40p)

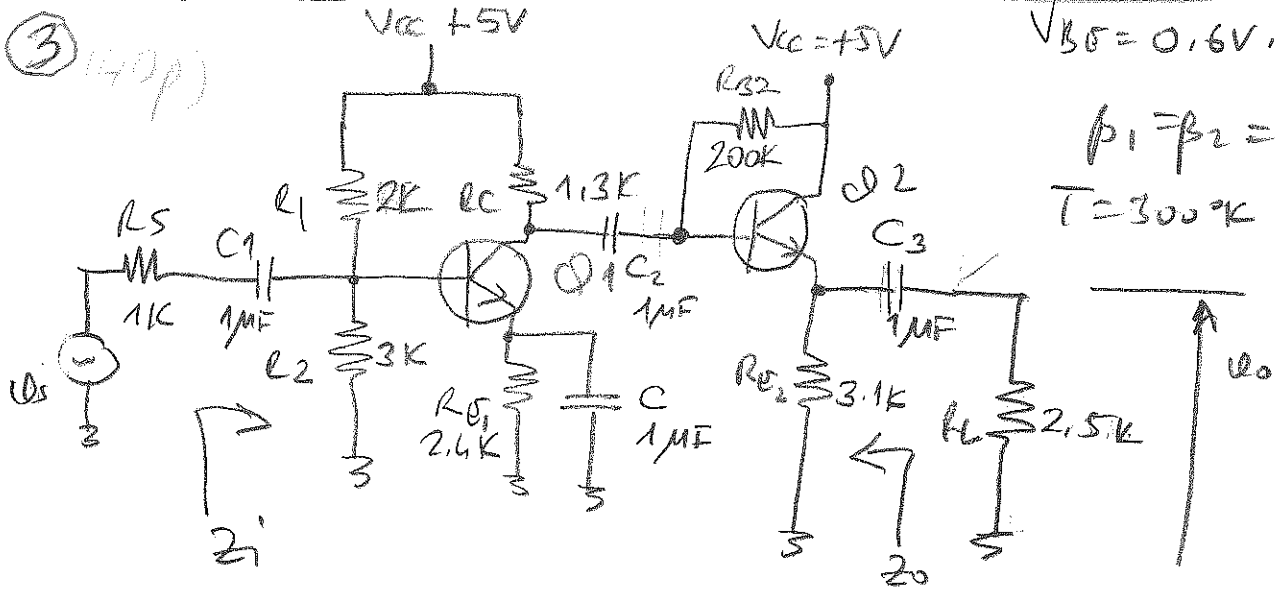

$V_{BE} = 0.6V$

$\beta_1 = \beta_2 = 200$

$T = 300^{\circ}K$

- For the amplifier circuit given above, calculate
- The overall voltage gain  $A_{VT} = \frac{V_o}{V_s}$
  - Calculate  $Z_i$  and  $Z_o$ .

SOLUTION

a) The DC analysis: for Q1

$$V_{B1} = \frac{V_{CC} \cdot R_2}{R_1 + R_2} = \frac{5 \times 3 \times 10^3}{(2+3) \times 10^3} = \frac{15}{5} = 3V$$

$$V_{E1} = V_{B1} - V_{BE} = 3 - 0.6 = 2.4V$$

$$I_{E1} = \frac{V_{E1}}{R_{E1}} = \frac{2.4}{2.4 \times 10^3} = 1mA$$

$$r_{e1} = \frac{V_T}{I_{E1}} = \frac{26 \times 10^{-3}}{10^{-2}} = 2.6\Omega$$

for Q2

$$V_{CC} - I_{B2} R_B - V_{BE} - I_{E2} R_{E2} = 0$$

$$I_{B2} = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_{E2}}$$

$$I_{B2} = \frac{5 - 0.6}{200 \times 10^3 + 201 \times 3.1 \times 10^3}$$

$$I_{B2} = \frac{4.4}{823 \times 10^3}$$

$$I_{B2} = 5.3 \times 10^{-6} A$$


$$I_{E2} = (\beta + 1) \times I_{B2}$$

$$I_{E2} = 201 \times 5.3 \times 10^{-6}$$

$$I_{E2} = 1.07 mA$$

$$r_{e2} = \frac{26mV}{1.07 \times 10^{-3}} = 24\Omega$$

# AC ANALYSIS

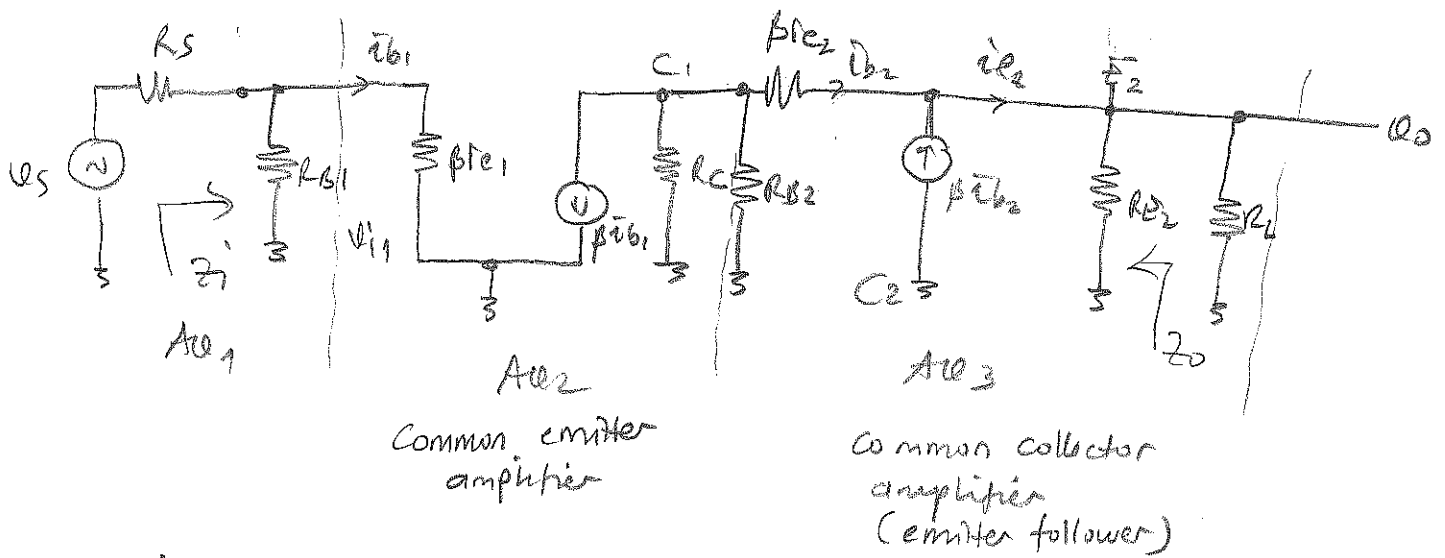

$$A_{0T} = A_{01} \cdot A_{02} \cdot A_{03}$$

$$A_{01} = \frac{v_{i1}}{v_s} = \frac{Z_i}{R_s + Z_i}$$

$$v_{i2} - v_o = i_{b2} \cdot \beta r_{e2} \Rightarrow i_{b2} = \frac{v_{i2} - v_o}{\beta r_{e2}}$$

$$v_o = i_{e2} \cdot (R_{E2} // R_L)$$

$$v_o = (\beta + 1) i_{b2} (R_{E2} // R_L)$$

$$v_o = (\beta + 1) \left( \frac{v_{i2} - v_o}{\beta r_{e2}} \right) \cdot (R_{E2} // R_L)$$

$$v_o = (\beta + 1) v_{i2} \left( \frac{R_{E2} // R_L}{\beta r_{e2}} \right) - (\beta + 1) v_o \left( \frac{R_{E2} // R_L}{\beta r_{e2}} \right)$$

$$\beta + 1 \approx \beta', \quad \beta = 200$$

$$v_o \approx v_{i2} (R_{E2} // R_L) - v_o (R_{E2} // R_L)$$

$$v_o (1 + R_{E2} // R_L) = v_{i2} (R_{E2} // R_L)$$

$$\frac{v_o}{v_{i2}} \approx A_{03} \approx \frac{R_{E2} // R_L}{1 + R_{E2} // R_L}$$

Emitter Follower

$$A_{03} = \frac{3.1 \times 10^3 \times 2.5 \times 10^3}{(3.1 + 2.5) \times 10^3} = \frac{1.38 \times 10^3}{1 + 1.38 \times 10^3}$$

$$A_{03} \approx 1$$

$$A_{0T} = 0.5 \times (-50) \times 1$$

$$A_{0T} \approx -25$$

$$A_{02} = - \frac{R_c'}{r_{e1}} \quad \text{Common emitter}$$

$$R_c' = R_c // R_{B2} \approx \frac{1.3 \times 10^3 \times 200 \times 10^3}{(1.3 + 200) \times 10^3} = 1.3 \text{ k}\Omega$$

$$Z_i = R_{B1} // \beta r_{e1}$$

$$R_{B1} = R_1 // R_2$$

$$Z_i = \frac{\left( \frac{2 \text{ k}\Omega \times 3 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} \right) (201 \times 26)}{\left( \frac{2 \text{ k}\Omega \times 3 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} \right) + 201 \times 26}$$

$$Z_i = \frac{1.2 \times 10^3 \times 5.2 \times 10^3}{(1.2 + 5.2) \times 10^3} = \frac{6.24 \times 10^3}{6.4 \times 10^3}$$

$$Z_i \approx 975 \Omega$$

$$A_{01} = \frac{975 \Omega}{103 + 975} \approx 0.5$$


$$A_{02} = - \frac{1.3 \times 10^3}{26}$$

$$A_{02} \approx -50$$

(2)

$$b) Z_i = R_{B1} \parallel \beta r_{e1} = 975 \Omega$$

$$Z_o =$$

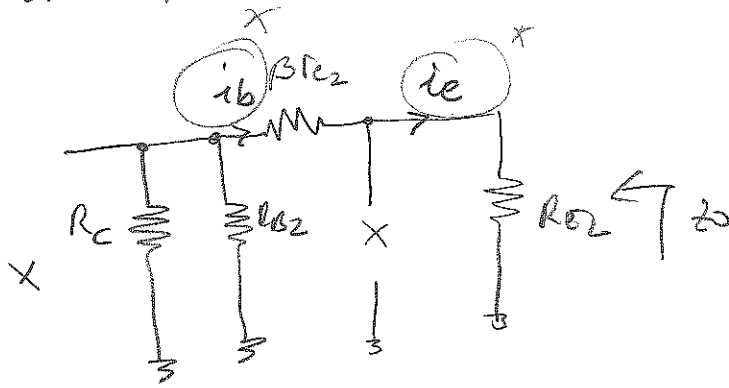

$$Z_o = R_{o2} \parallel \left( \frac{\beta r_{e2} + R_C \parallel R_{B2}}{\beta} \right)$$

$$Z_o = R_{o2} \parallel \left( r_{e2} + \frac{R_C \parallel R_{B2}}{\beta} \right)$$

$$R_C \parallel R_{B2} = 1.3K$$

$$Z_o = R_{o2} \parallel \left( 26 + \frac{1.3 \times 10^3}{200} \right)$$

$$Z_o = R_{o2} \parallel (26 + 6.5)$$


$$Z_o = R_{o2} \parallel 32.5$$

$$Z_o = \frac{3.1 \times 10^3 \times 32.5}{(3.1 \times 10^3 + 32.5)}$$

$$Z_o \approx 32.5 \Omega$$

$I_{E1}$	$I_{E2}$	$r_{e1}$	$r_{e2}$	$A_{v1}$	$A_{v2}$	$A_{v3}$	$A_{vT}$	$Z_i$	$Z_o$
1mA	1.07mA	26 $\Omega$	24 $\Omega$	0.5	-50	1	-25	975 $\Omega$	32.5 $\Omega$

2  
15p

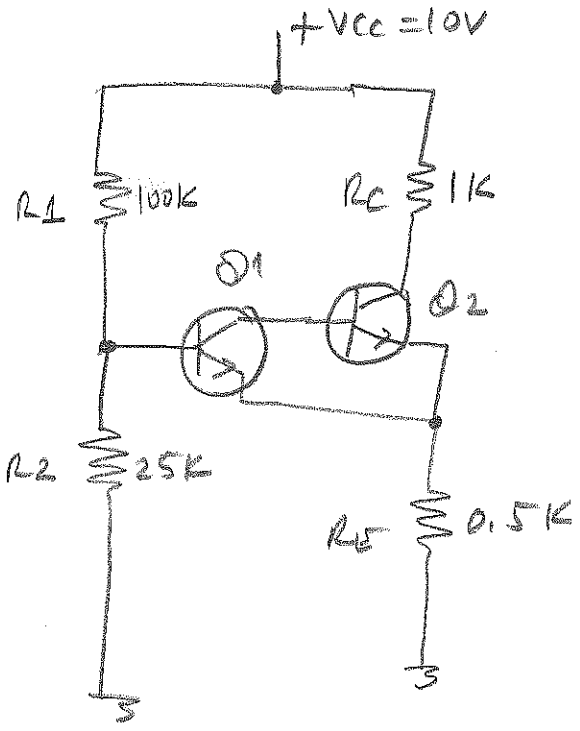

Q1 and Q2 are identical transistors,  
 $V_{BE1} = V_{BE2} = 0.6V$ ,  
 $\beta_1 = \beta_2 = 20$

- a) Calculate  $I_{C2}$
- b) Calculate  $V_{CE2}$ .

Sol

$$I_E = \frac{V_{B1} - V_{BE}}{R_E}$$

$$V_{B1} = \frac{V_{CC}}{R_1 + R_2} \cdot R_2 = \frac{10}{125 \times 10^3} \cdot 25 \times 10^3$$

$$V_{B1} = \frac{10}{5} = 2V$$

$$V_E = V_{B1} - V_{BE} = 2 - 0.6 = 1.4V$$

$$I_E = \frac{V_E}{R_E} = \frac{1.4V}{0.5 \times 10^3} = 2.8mA$$

a)  $I_E = I_{E1} + I_{E2}$

$$\left. \begin{aligned} I_{C2} &= \beta \cdot I_{B2} \\ I_{B2} &= \beta \cdot I_{B1} \end{aligned} \right\} I_{C2} = \beta^2 \cdot I_{B1}$$

$$I_E = (\beta + 1) I_{B1} + (\beta + 1)^2 I_{B1}$$

$$I_{B1} = \frac{I_E}{(\beta + 1) + (\beta + 1)^2} = \frac{I_E}{(\beta + 1)(\beta + 2)} = \frac{2.8 \times 10^{-3}}{21.22}$$

$$I_{B1} = 6.06 \times 10^{-6} A$$

$$I_{C2} = \beta^2 \cdot I_{B1} = (20)^2 \cdot 6.06 \times 10^{-6}$$

$$I_{C2} = 2.4 \times 10^{-3} A$$

4

output level

b)  $V_{CC} - I_{C2}R_C - V_{CE2} - I_{E2}R_E = 0$

$V_{CE2} = V_{CC} - I_{C2}R_C - I_{E2}R_E$

(12)


$V_{CE2} = 10 - 2.4 \times 10^{-3} \times 10^3 - 2.8 \times 10^{-3} \times 0.5 \times 10^3$

$V_{CE2} = 10 - 2.4 - 1.4$

$V_{CE2} = 6.2V$

$I_{C2}$	$V_{CE2}$
2.4 mA	6.2V

(1) 15p

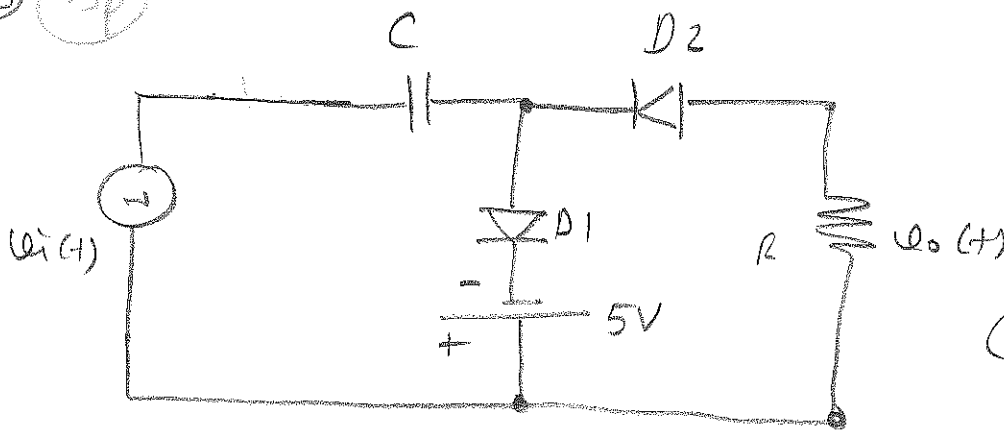


Sketch the output signal  $u_o(t)$   
(Diodes are ideal)

$u_i(t) = 10 \sin 200\pi t$ ,  $R = 10k$ ,  $C = 100nF$

SOL First lets charge the capacitor:

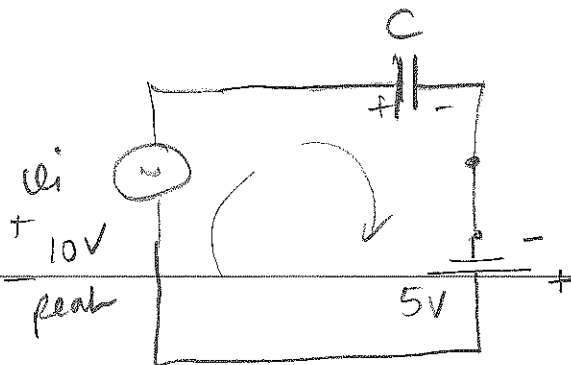When  $u_i > -5V$  the capacitor charges (D1 is forward biased)



$u_i = u_C + 5V$

$u_C = u_i + 5$


in the end of charging period

$u_C = 15V$


$u_C$  is charged to this voltage.

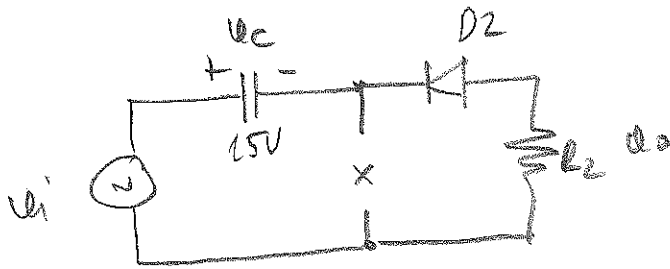(5)


After the capacitor is charged to this voltage,  $D_1$  becomes reverse biased and will never be forward biased again.



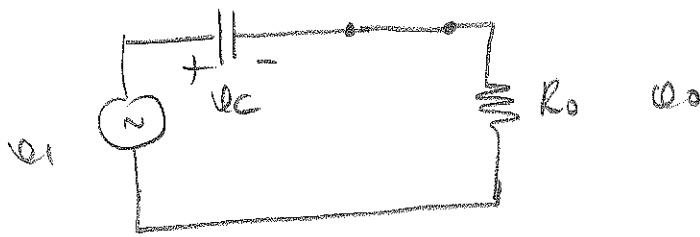$D_2$  will always be forward biased after that point



$$v_o = v_i - v_c$$

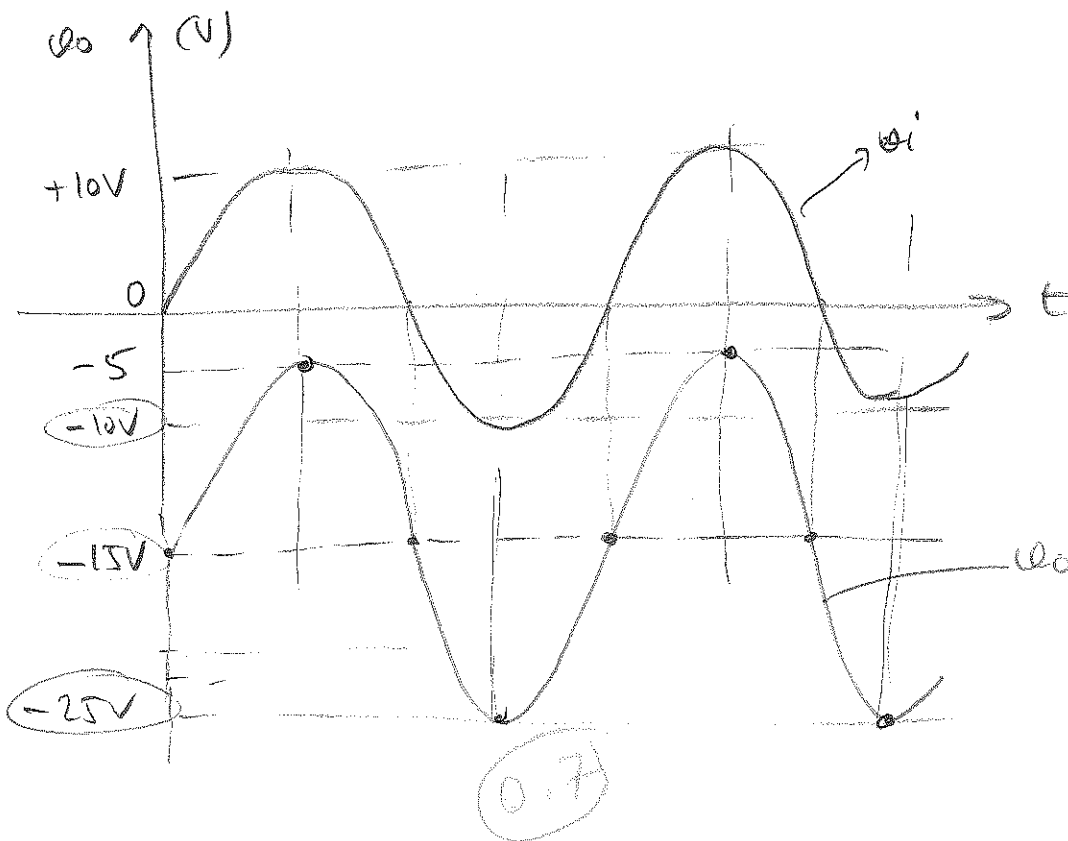


④ For the circuit given below calculate

(30p)


The overall voltage gain

$$A_{vT} = \frac{V_o}{V_i}$$

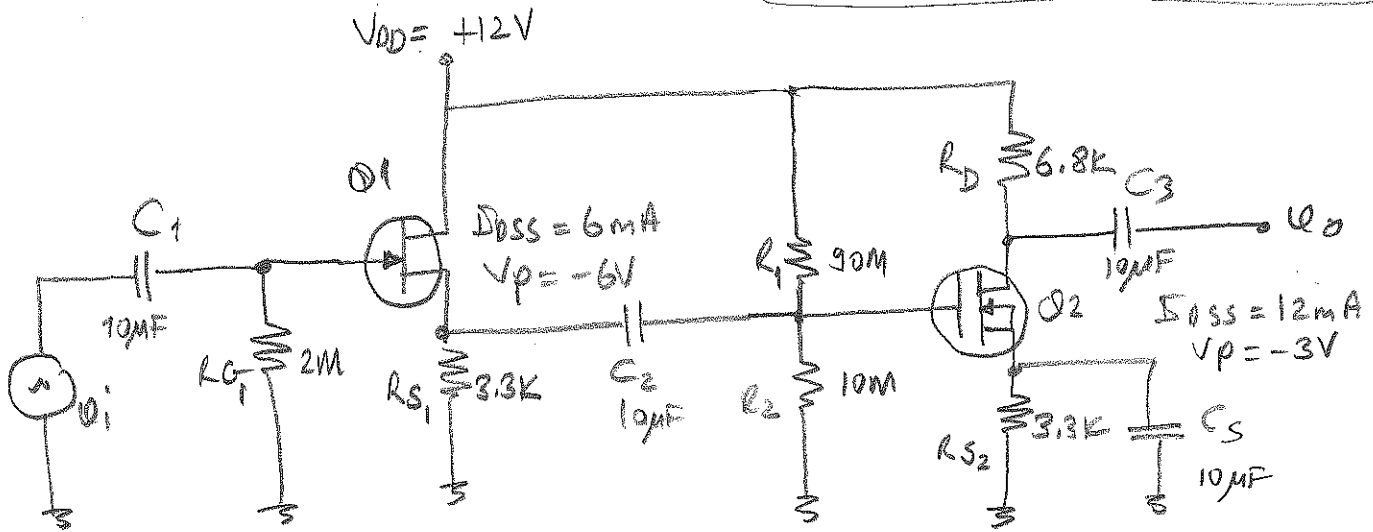

DC analysis to find the gm's:

Q1:

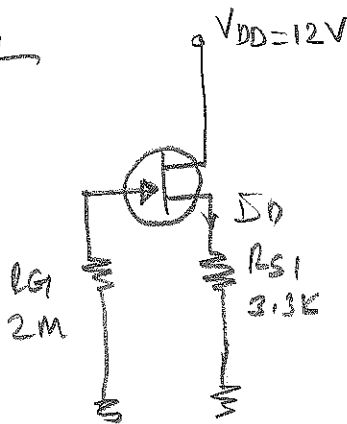

Input KVL

$$V_G - V_{GS} - V_S = 0$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = 0 - V_S$$

$$V_{GS} = -I_D R_S$$

Using the JFET characteristic curve

$$V_{GS} = -I_D \times 3.3 \times 10^3 \quad \text{Load line}$$

1st point

$$V_{GS} = 0$$

$$I_D = 0$$

2nd point

$$V_{GS} = -6V$$

$$I_D = \frac{6}{3.3 \times 10^3} = 1.8 \text{ mA}$$

$$V_{GS1} = -3.5V$$

$$g_{m1} = \frac{2 I_{DSS} (1 - \frac{V_{GS}}{V_p})}{|V_p|}$$

$$g_{m1} = \frac{2 \times 6 \times 10^{-3}}{6} (1 - \frac{3.5}{6})$$

$$g_{m1} = 0.84 \text{ ms}$$

Q2

$$V_{GS} = V_G - V_S$$

$$V_G = \frac{V_{DD}}{R_1 + R_2}$$

$$V_G = \frac{12}{100 \times 10^3} \cdot 10 \times 10^6$$

$$V_G = 1.2V$$

$$V_{GS} = 1.2 - I_D \cdot R_S$$

$$V_{GS} = 1.2 - I_D \times 3.3 \times 10^3$$

Load line

$$V_{GS} = 0 \quad I_D = \frac{1.2}{3.3 \times 10^3} = 3.63 \times 10^{-4} \text{ A}$$

$$V_{GS} = -2.4V \quad I_D = \frac{-3.6}{3.3 \times 10^3} \approx 1.1 \text{ mA}$$

$$V_{GS2Q} = -2.4V$$

$$g_{m2} = \frac{2 I_{DSS} (1 - \frac{V_{GS}}{V_p})}{|V_p|}$$

⑦



$$g_{m2} = \frac{2 \times 10^{-3}}{3} \left(1 - \frac{2.1}{3}\right)$$

$$= 8 \times 10^{-3} \times 0.3$$

$$g_{m2} = 2.4 \text{ mS}$$

1st circuit is a common-drain circuit

$$A_{v1} = \frac{g_{m1} R_{S'}}{1 + g_{m1} R_{S'}}$$

$$R_{S'} = R_S // (R_1 // R_2)$$

$$R_{S'} = 3.3 \text{ k} // (10 \text{ M} // 90 \text{ M}) \approx \underline{\underline{3 \text{ k}}}$$

$$A_{v1} = \frac{0.84 \times 10^{-3} \times 3 \times 10^3}{1 + 0.84 \times 10^{-3} \times 3 \times 10^3} = \frac{2.52}{1 + 2.52} = \frac{2.52}{3.52} = \underline{\underline{0.72}}$$

2nd circuit is a common source circuit

$$A_{v2} = -g_{m2} R_D$$

$$A_{v2} = -2.4 \times 10^{-3} \times 6.8 \times 10^3$$

$$A_{v2} = -16.3$$

Overall gain  $A_{vT} = A_{v1} \times A_{v2}$

$$A_{vT} = 0.72 \times (-16.3)$$

$$A_{vT} \approx -11.7$$

$V_{GS01}$	$V_{GS02}$	$g_{m1}$	$g_{m2}$	$A_{v1}$	$A_{v2}$	$A_{vT}$
-3.5V	-2.1V	0.84 mS	2.4 mS	0.72	-16.3	-11.7

