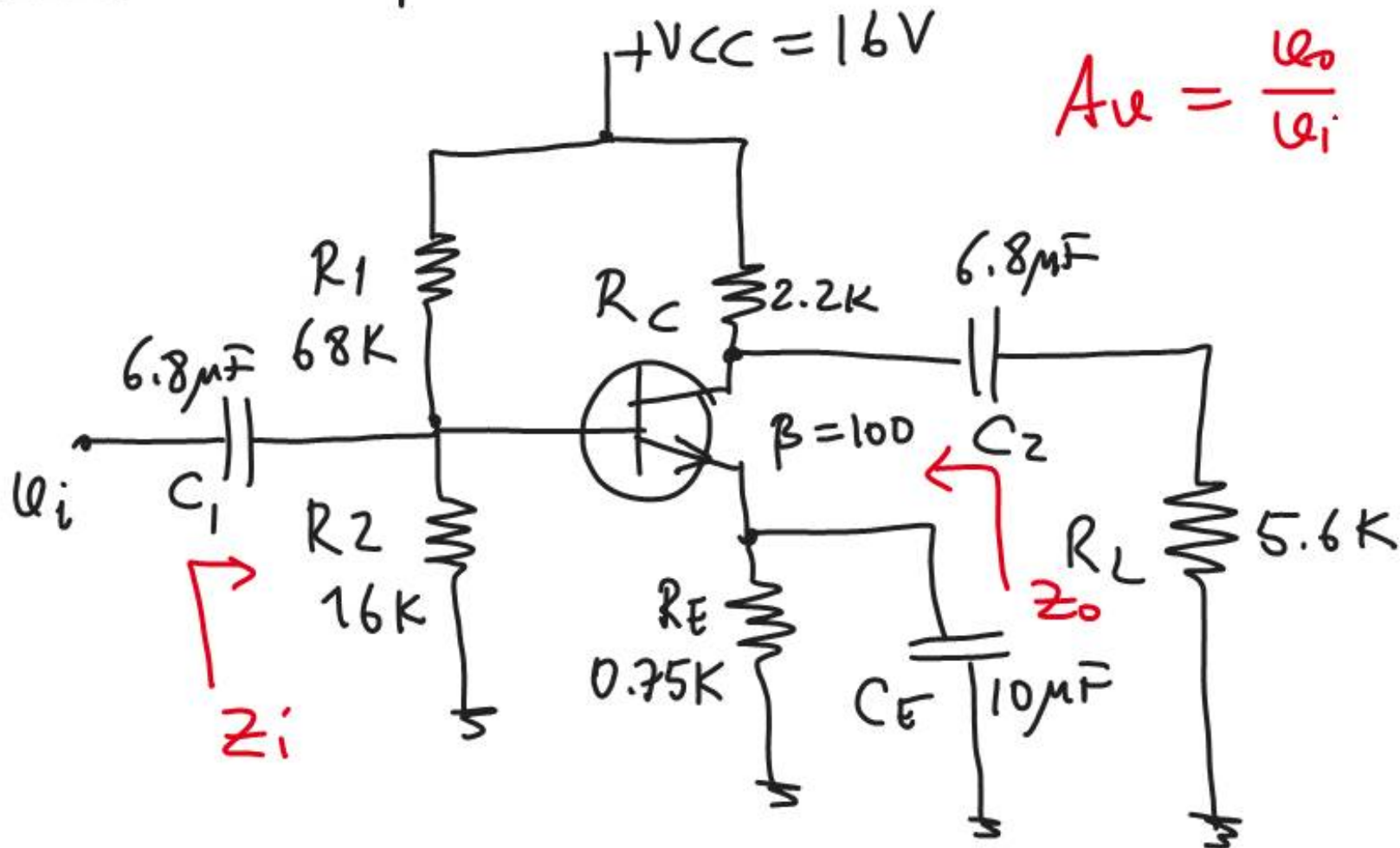


22.05.2012


©

Last lecture this year.

Ex: Chapter 5 Problem 40



DC

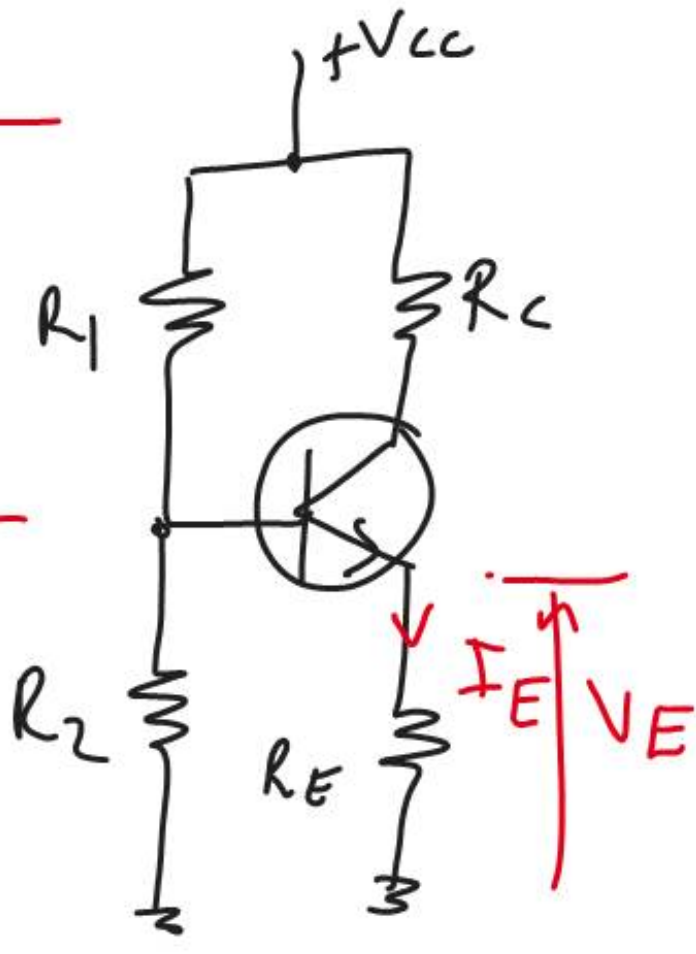

$$V_B \approx \frac{V_{CC}}{R_1 + R_2} = \frac{16}{(68 + 16) \times 10^3} \times 16 \times 10^3$$
$$\approx 3V$$

$$V_E = V_B - V_{BE} = 3 - 0.7 = 2.3V$$


$$I_E = \frac{V_E}{R_E} = \frac{2.3}{0.75 \times 10^3} \approx 3 \times 10^{-3} A$$

$$r_e = \frac{V_T}{I_E} = \frac{26 \times 10^{-3}}{3 \times 10^{-3}} \approx 9 \Omega$$



AC Analysis

$$A_v = ?$$

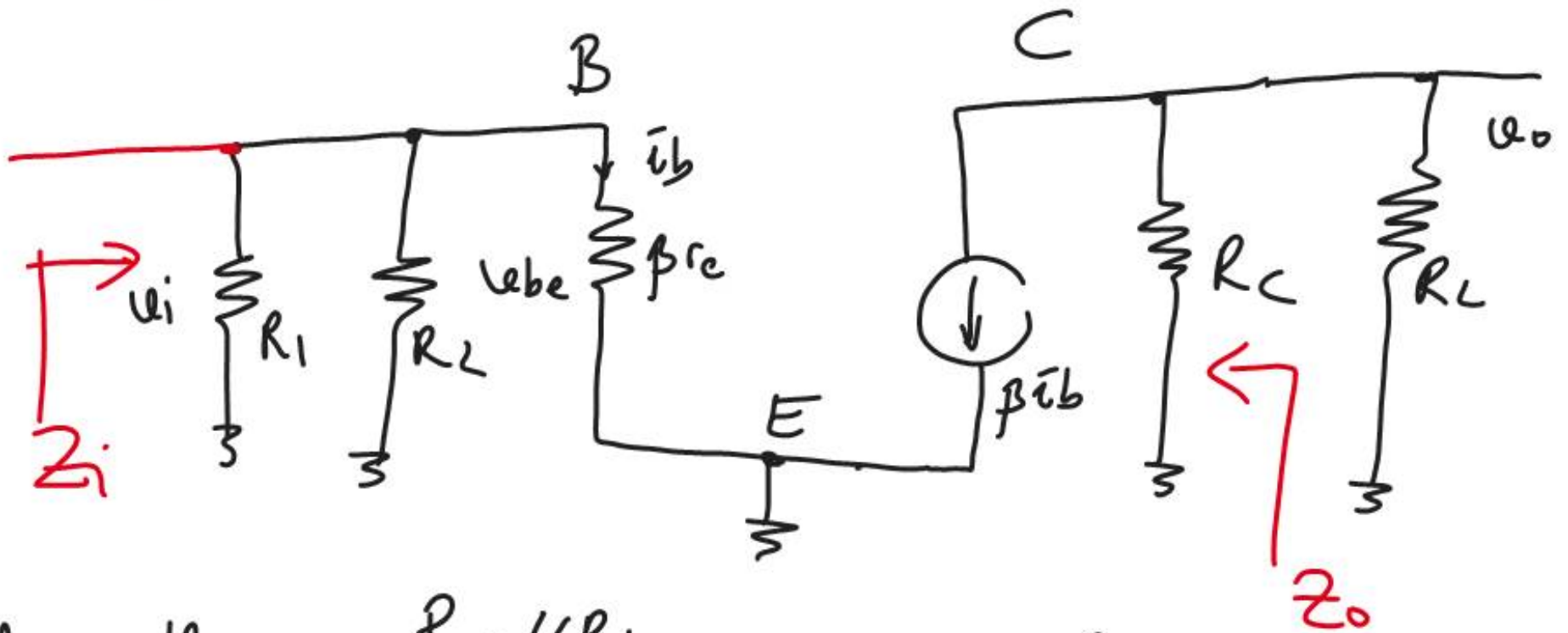


$$A_v = \frac{v_o}{v_i} = - \frac{R_C \parallel R_L}{r_e}$$

$$Z_o \approx R_C$$

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

Ex Chapter 5 Problem 43

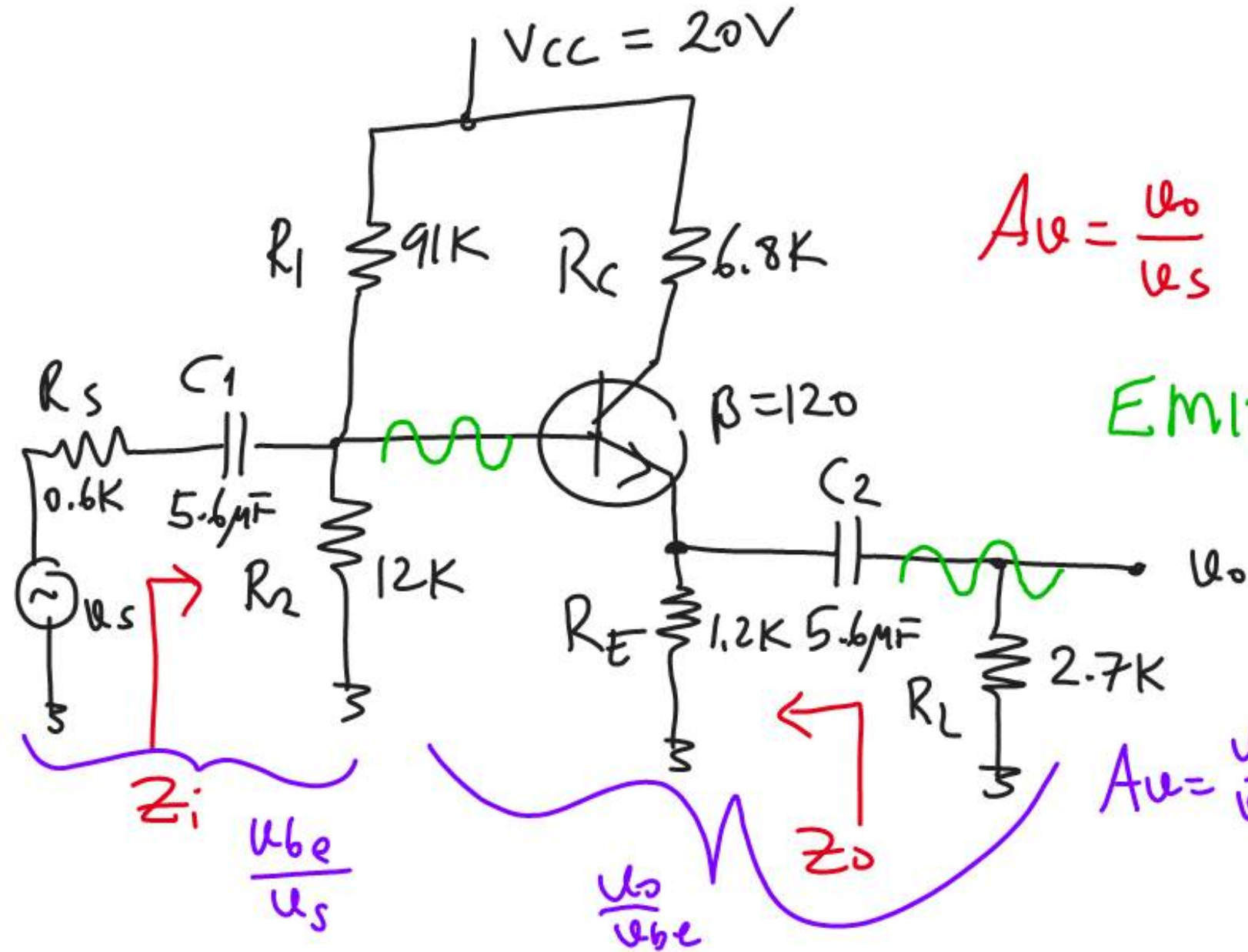


$$A_v = \frac{v_o}{v_s} ?$$

EMITTER Follower

$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_{be}} \cdot \frac{v_{be}}{v_s} = \left(\frac{R_E \parallel R_L}{R_E \parallel R_L + R_i} \right) \left(\frac{Z_i}{Z_i + R_S} \right)$$

DC Analysis

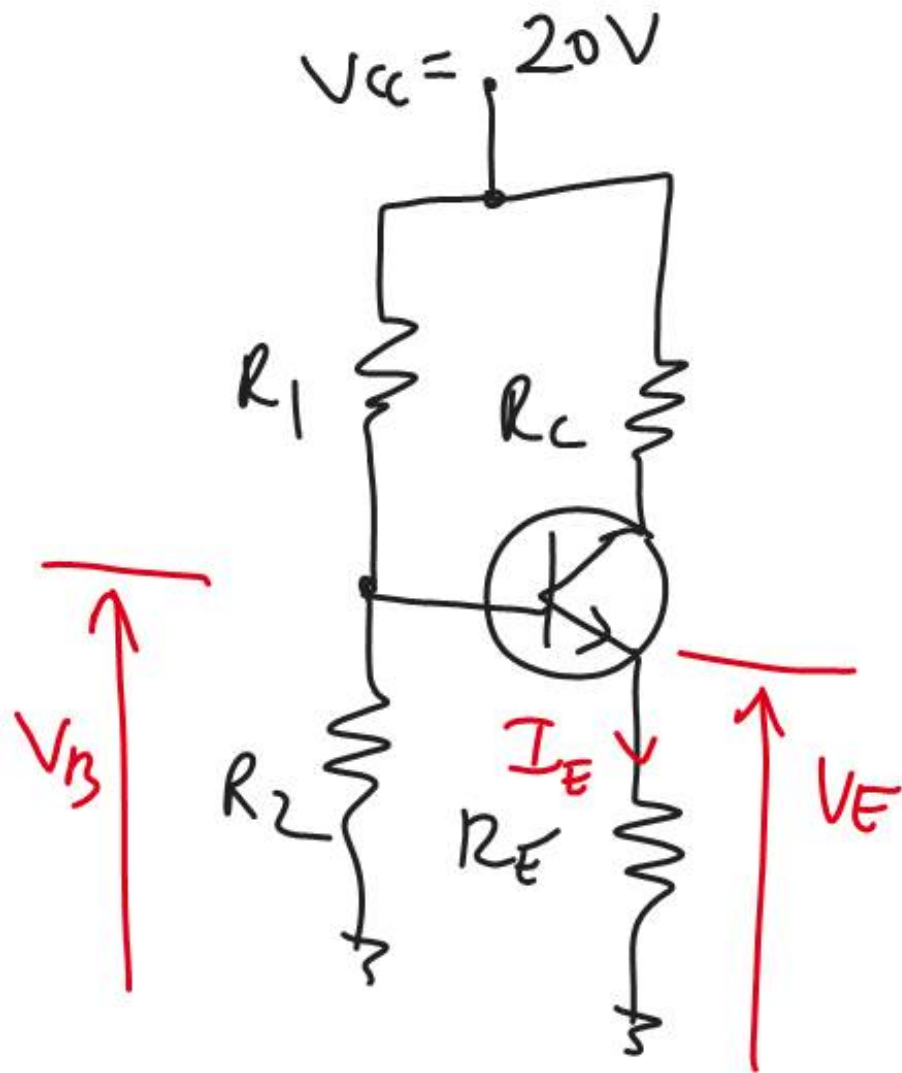

$$V_B = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{20}{91 + 12} \cdot 12$$

$$V_B \approx 2.3V$$



$$V_E = V_B - 0.7 = 2.3 - 0.7$$

$$V_E = 1.6V$$

$$I_E = \frac{V_E}{R_E} = \frac{1.6}{1.2 \times 10^3} = 1.3 \times 10^{-3} A$$

$$r_e = \frac{V_T}{I_E} = \frac{26 \times 10^{-3}}{1.3 \times 10^{-3}} = \underline{20 \Omega}$$


AC Analysis

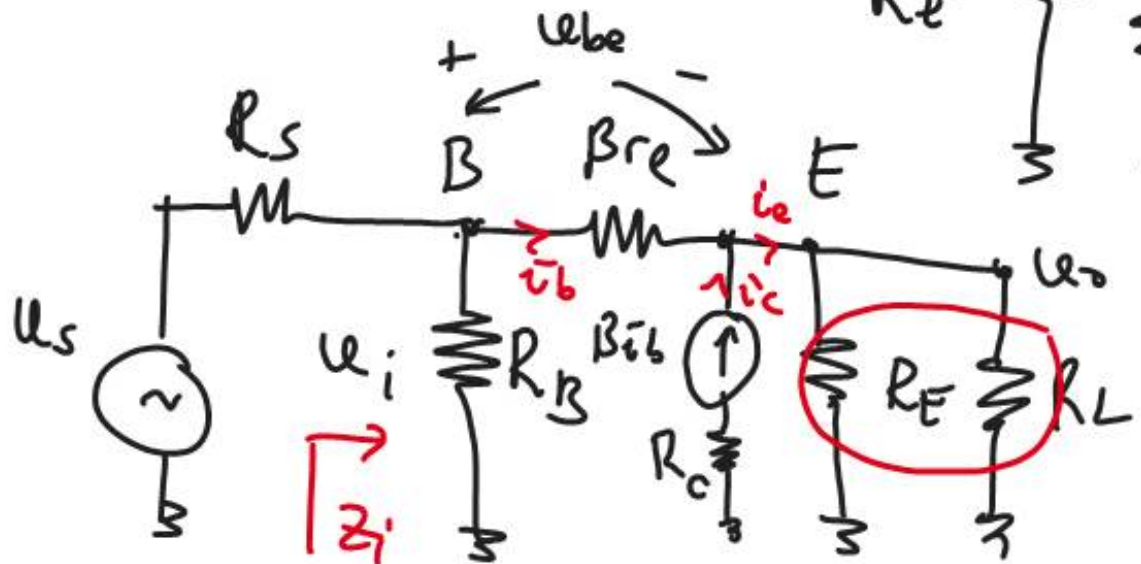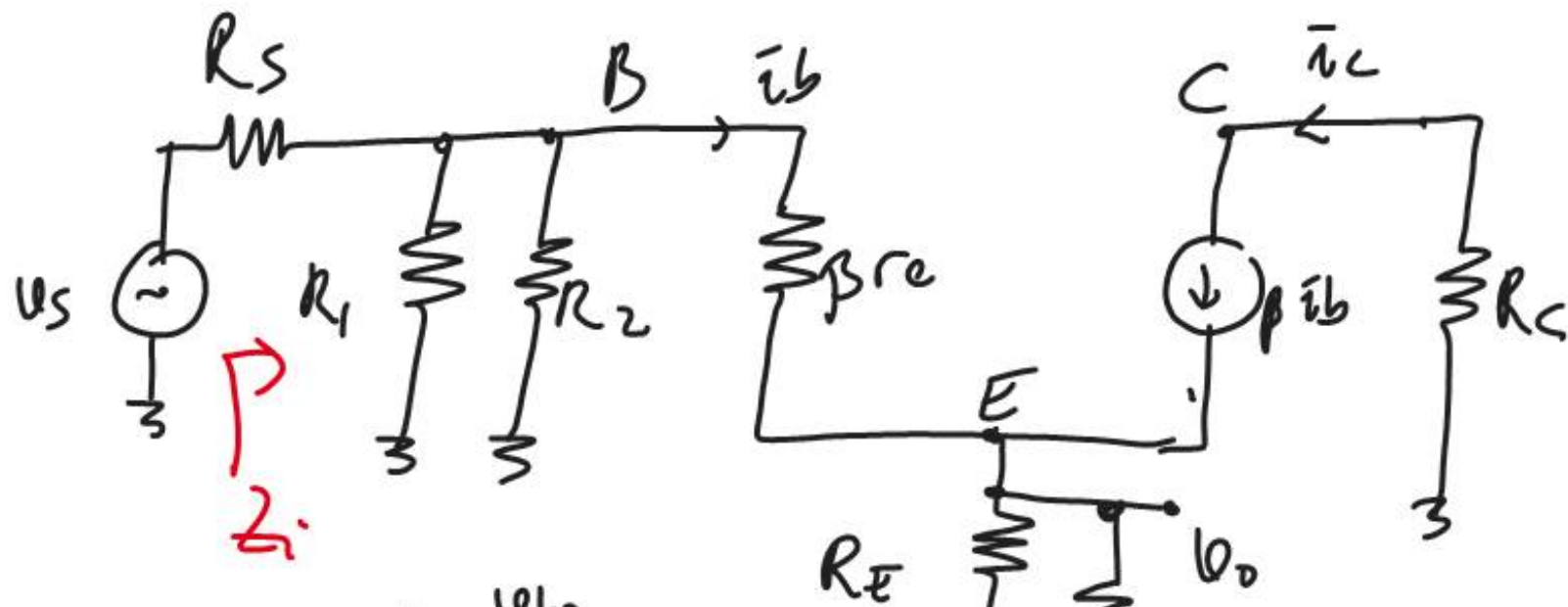

$$u_o = i_e \cdot (R_L \parallel R_E)$$

$$= (\beta + 1) i_b \cdot (R_L \parallel R_E)$$
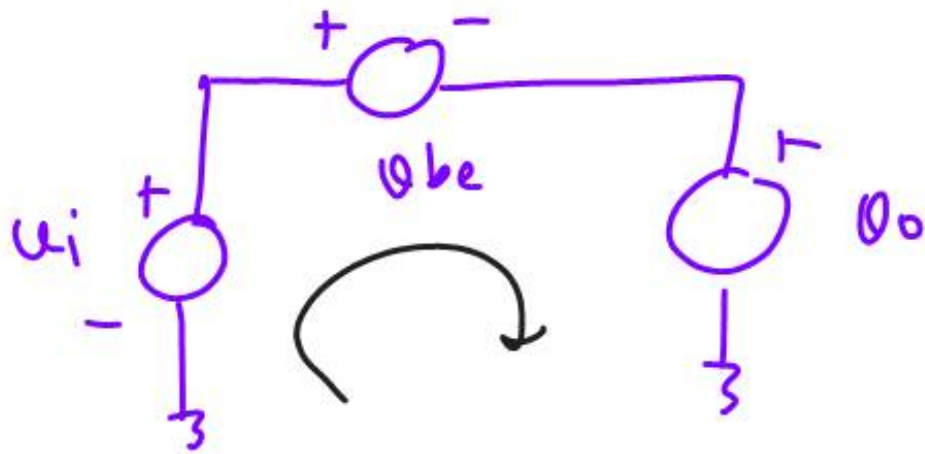
$$u_o = (\beta + 1) \frac{u_{be}}{\beta r_e} \cdot (R_L \parallel R_E)$$



$$u_i - u_b - u_o = 0$$

$$u_{be} = u_i - u_o$$

$$u_o = \frac{(\cancel{\beta})}{\cancel{\beta} \cdot r_e} (R_E // R_L) \cdot u_{be}$$

$$u_o \approx \left(\frac{R_E // R_L}{r_e} \right) \cdot u_{be}$$

$$u_o = \left(\frac{R_E // R_L}{r_e} \right) (u_i - u_o)$$

$$u_o + \left(\frac{R_E // R_L}{r_e} \right) u_o = \left(\frac{R_E // R_L}{r_e} \right) u_i$$

$$u_o \left[1 + \frac{R_E // R_L}{r_e} \right] = \left(\frac{R_E // R_L}{r_e} \right) u_i$$

$$\frac{u_o}{u_i} = \frac{\frac{R_E // R_L}{r_e}}{1 + \frac{R_E // R_L}{r_e}}$$

$$\frac{u_o}{u_i} = \frac{\frac{R_E // R_L}{r_e}}{\cancel{r_e} + \frac{R_E // R_L}{\cancel{r_e}}}$$

$$\frac{u_o}{u_i} = \frac{(R_E // R_L)}{r_e + (R_E // R_L)}$$


$$\frac{v_i}{v_s} = \frac{z_i}{z_i + R_s}$$

$$A_{vT} = \frac{v_o}{v_s} = \frac{(R_E // R_L)}{r_e + (R_E // R_L)} \cdot \frac{z_i}{z_i + R_s}$$

Overall Gain



$$z_i =$$


$$z_i \equiv$$

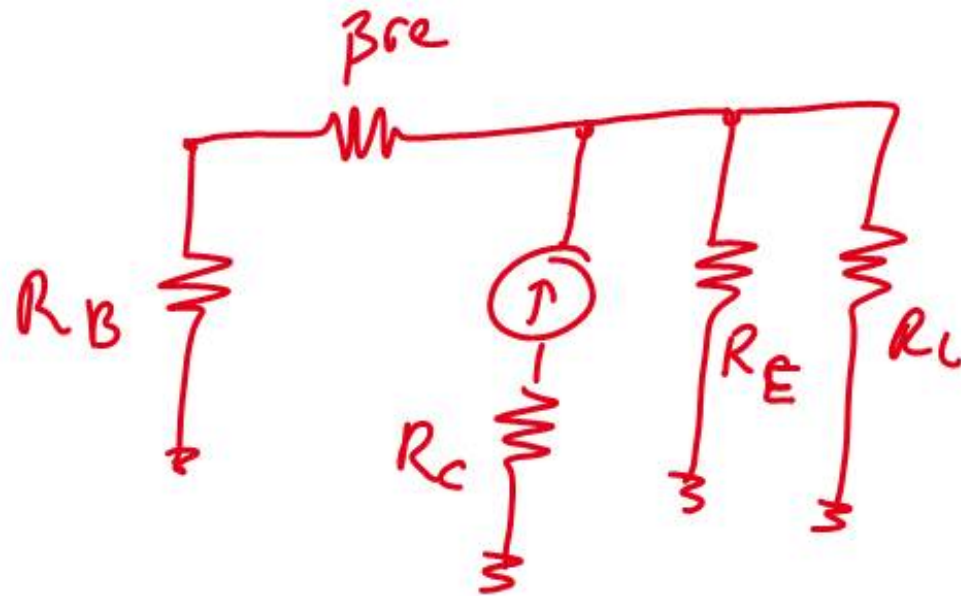


$$z_i \equiv R_B // [\beta r_e + (R_E // R_L)]$$

$$R_B = R_1 // R_2$$

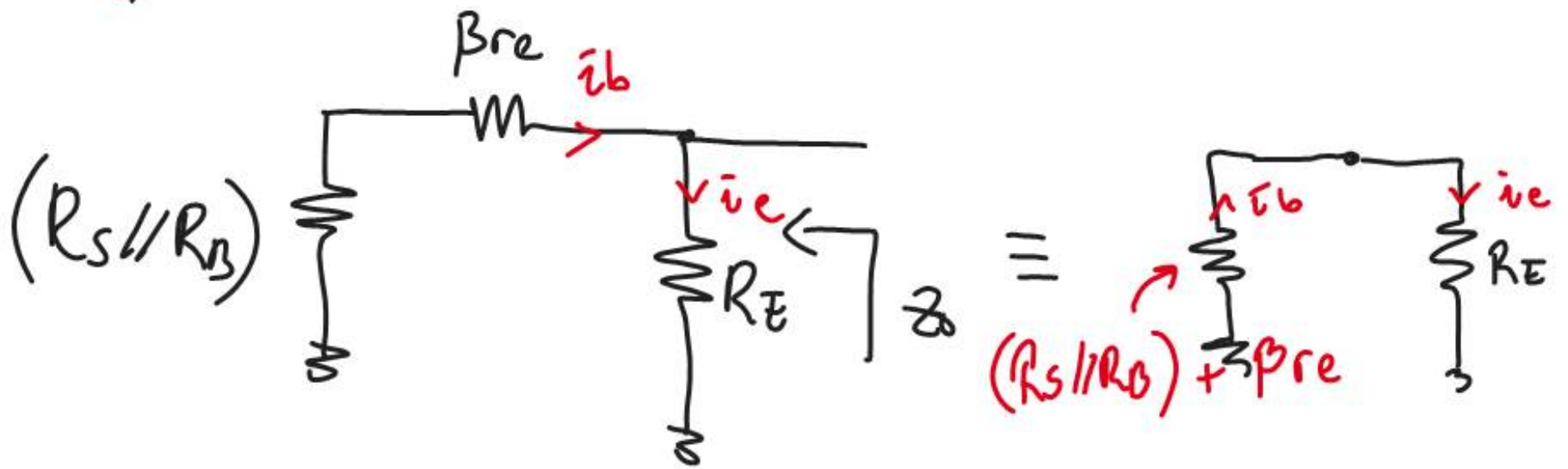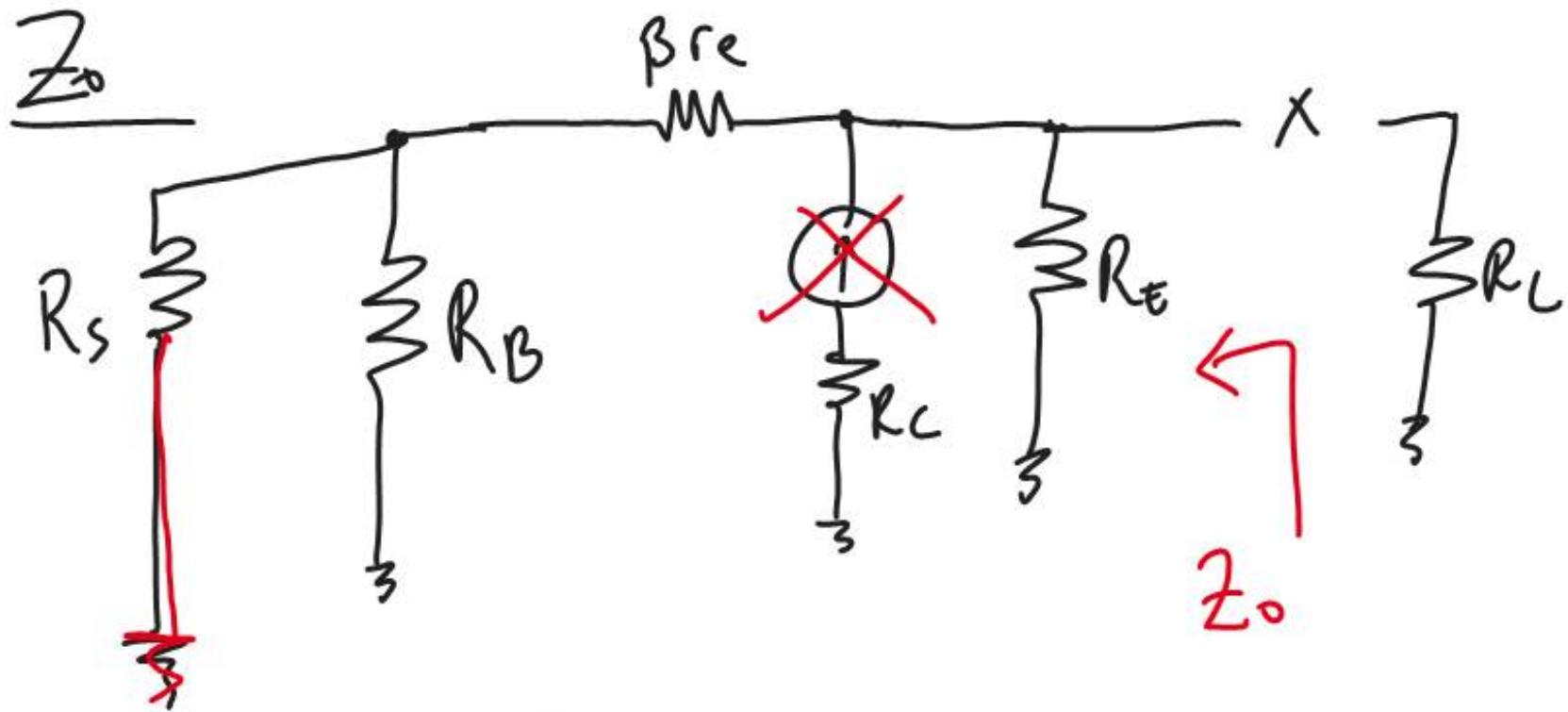

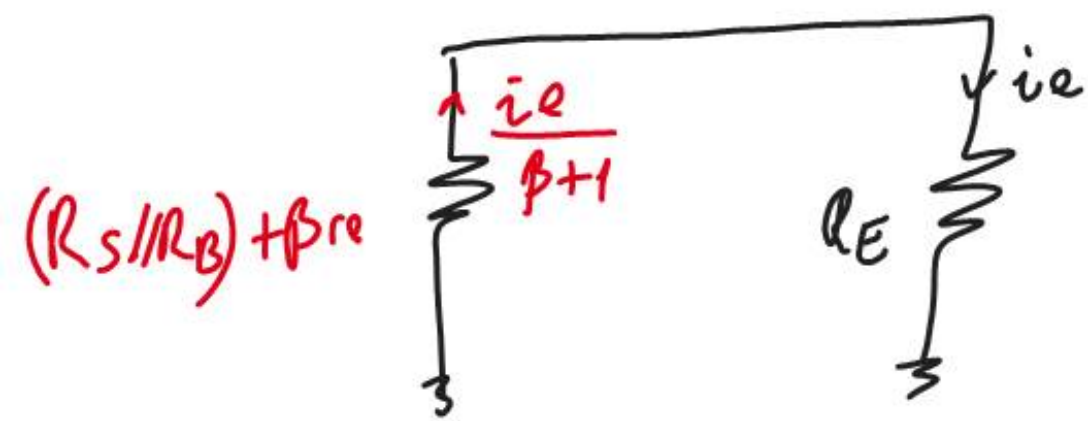
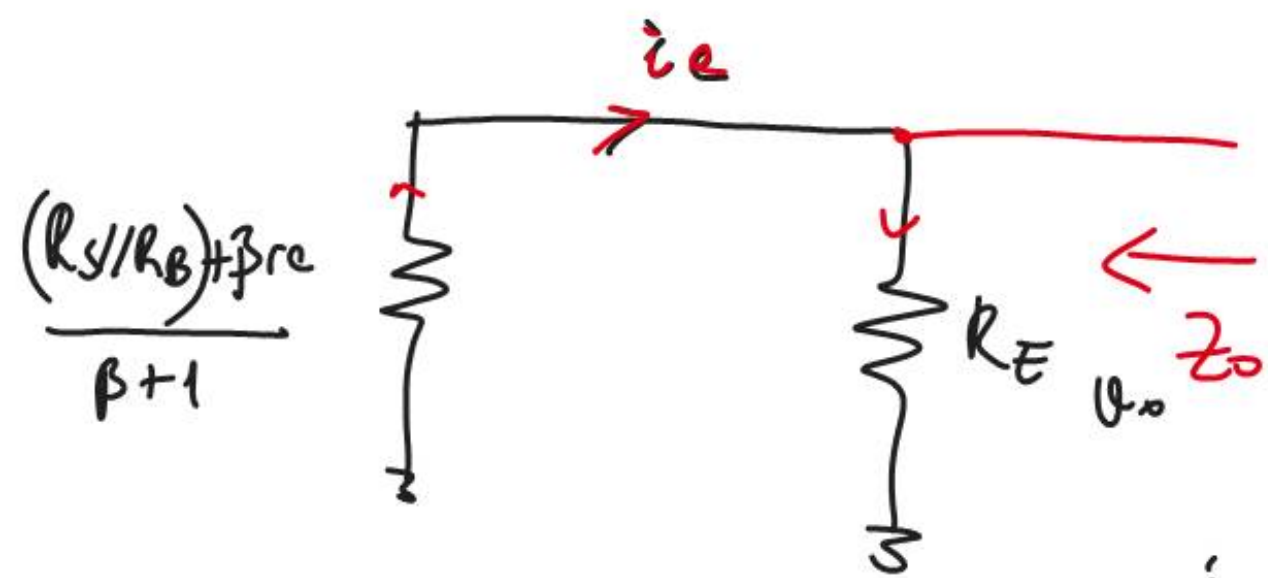
$$Z_o = R_E \parallel \left[\frac{(R_s/R_B) + \beta r_e}{\beta + 1} \right]$$




$$Z_o = \frac{v_o}{i_o}$$

$$i_o = i_e$$

Ex: Chapter 8 Problem 54, 55, 56

CASCADE
AMPLIFIER

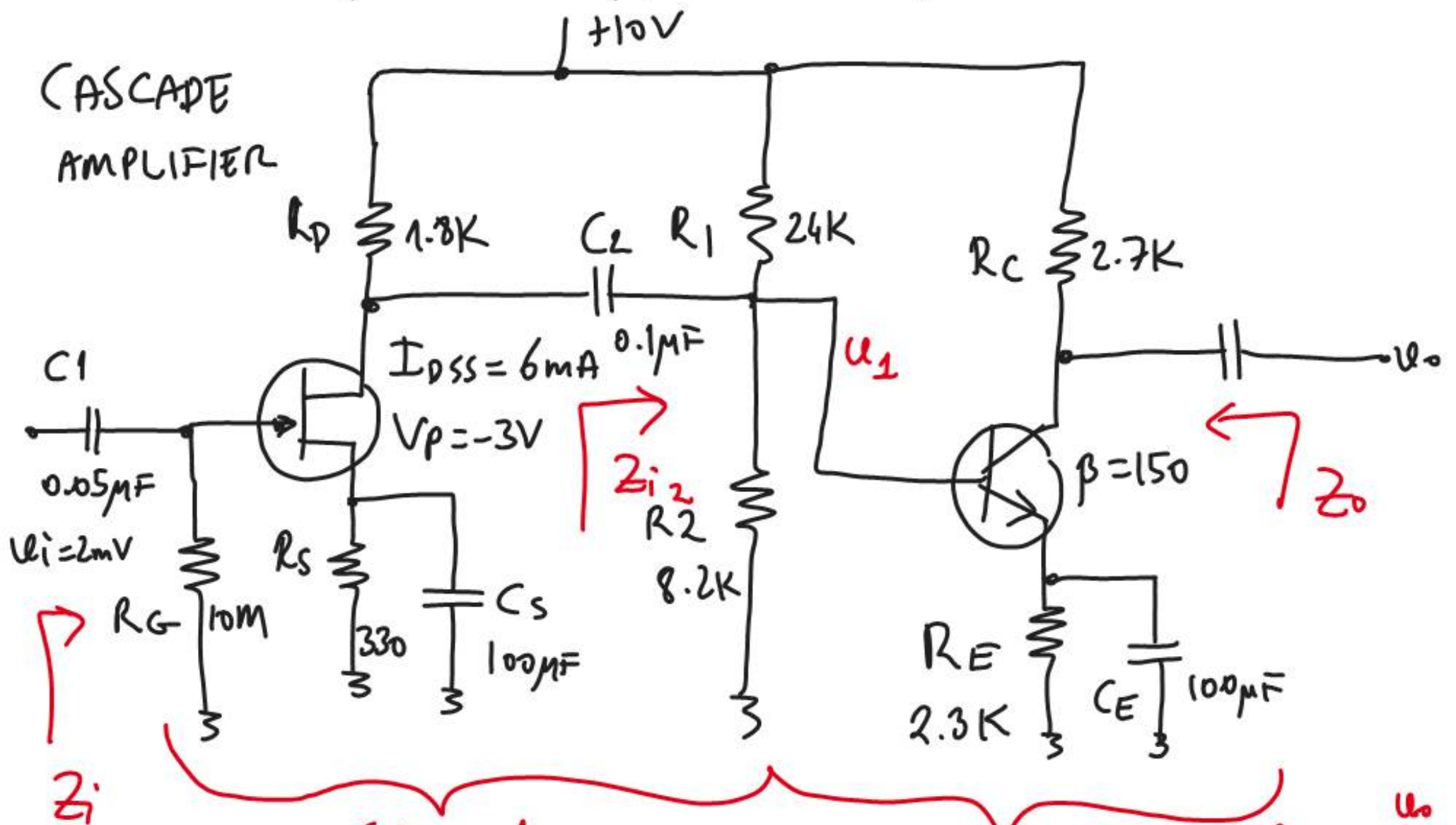

Stage - 1
JFET AMPLIFIER


$$A_{u1} = \frac{u_1}{u_i} = -g_m R_D' \quad R_D' = R_D // Z_{i2}$$

Stage - 2
BJT Amplifier

$$A_{u2} = \frac{u_o}{u_1} = -\frac{R_C}{r_e}$$

$$A_{vT} = A_{v1} \cdot A_{v2} = (-g_m R_D') \left(-\frac{R_C}{r_e}\right) = \frac{g_m}{r_e} \cdot R_D' \cdot R_C$$

DC Analysis

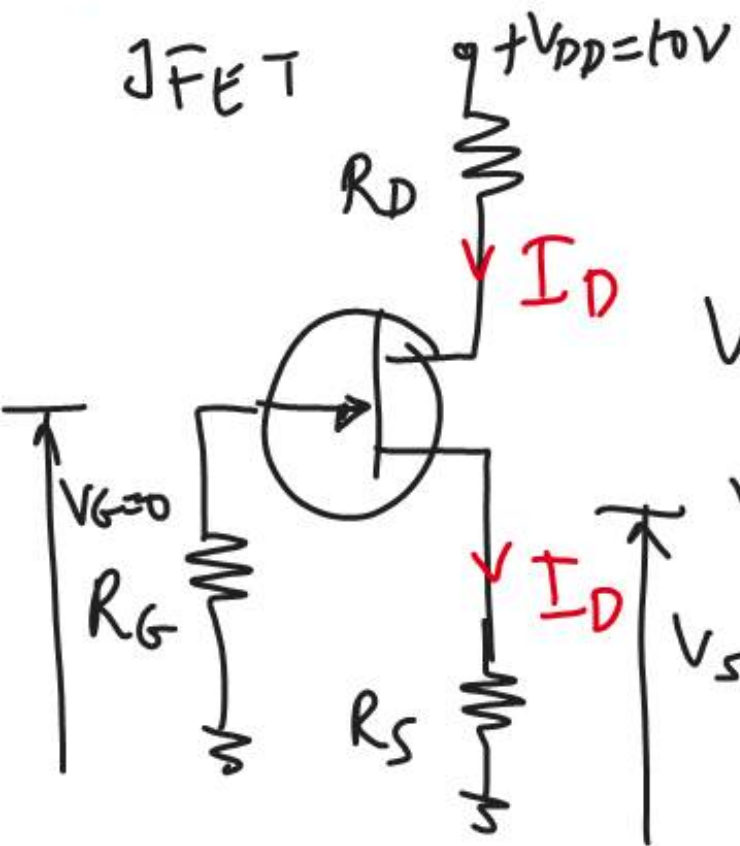


$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$


$$V_{GS} = V_G - V_S$$

$$V_{GS} = 0 - I_D \cdot R_S$$

$$V_{GS} = -I_D \cdot R_S$$

Load line

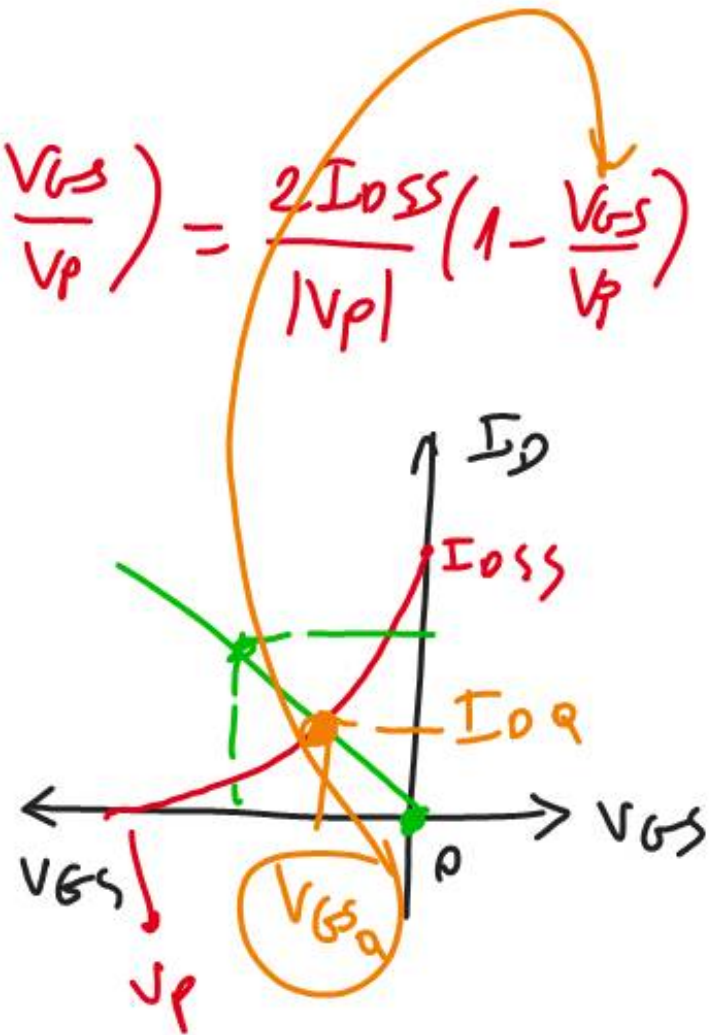

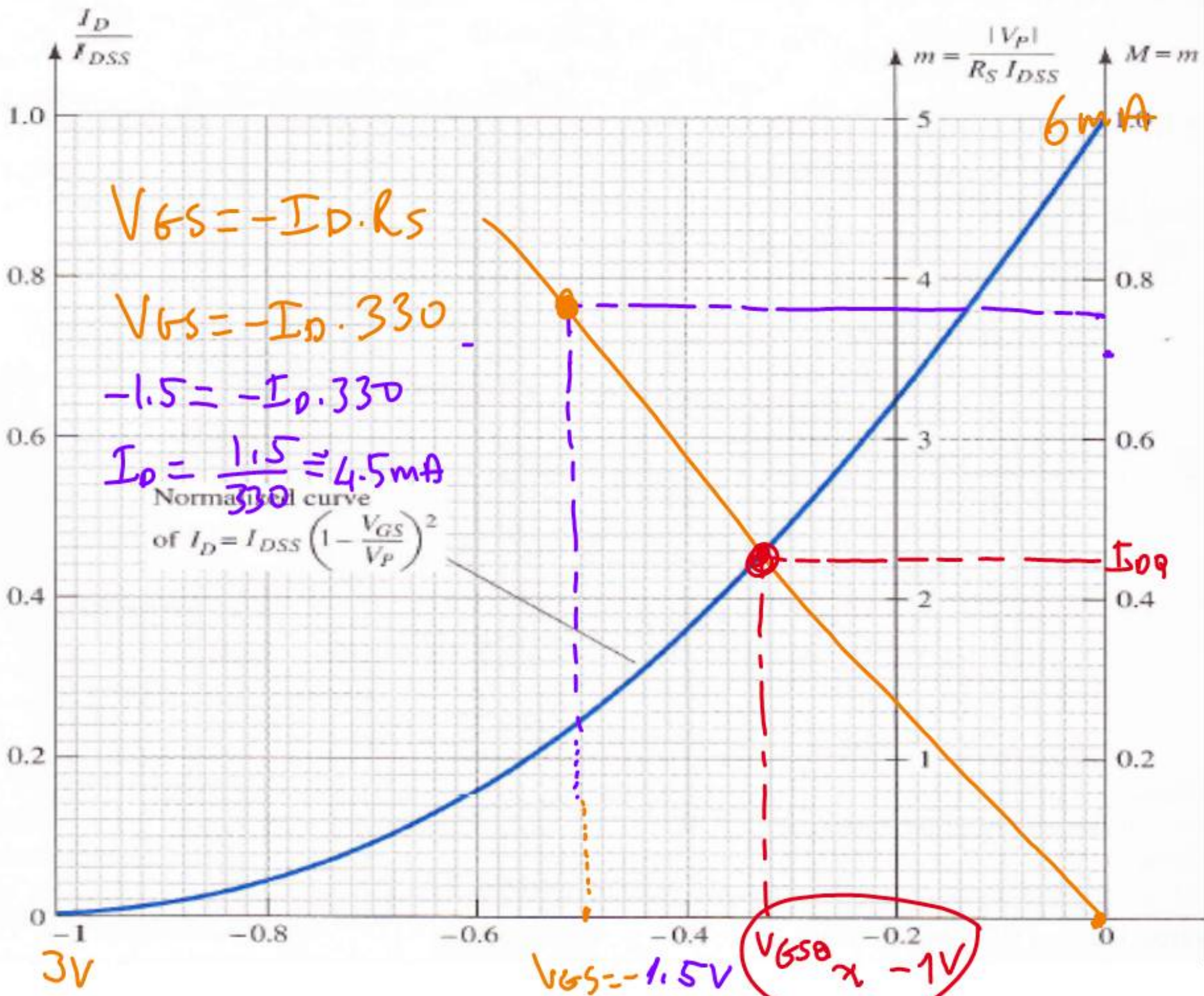


$$g_m = \frac{2I_{DSS}}{|V_p|} \cdot \left(1 - \frac{-1}{-3}\right)$$

$$= \frac{2 \times 4 \times 10^{-3}}{3} \left(1 - \frac{1}{3}\right)$$

$$= 4 \times 10^{-3} \left(\frac{2}{3}\right)$$

$$g_m = \frac{8}{3} \times 10^{-3} \text{ S}$$

$$g_m \approx 2.67 \text{ mS}$$

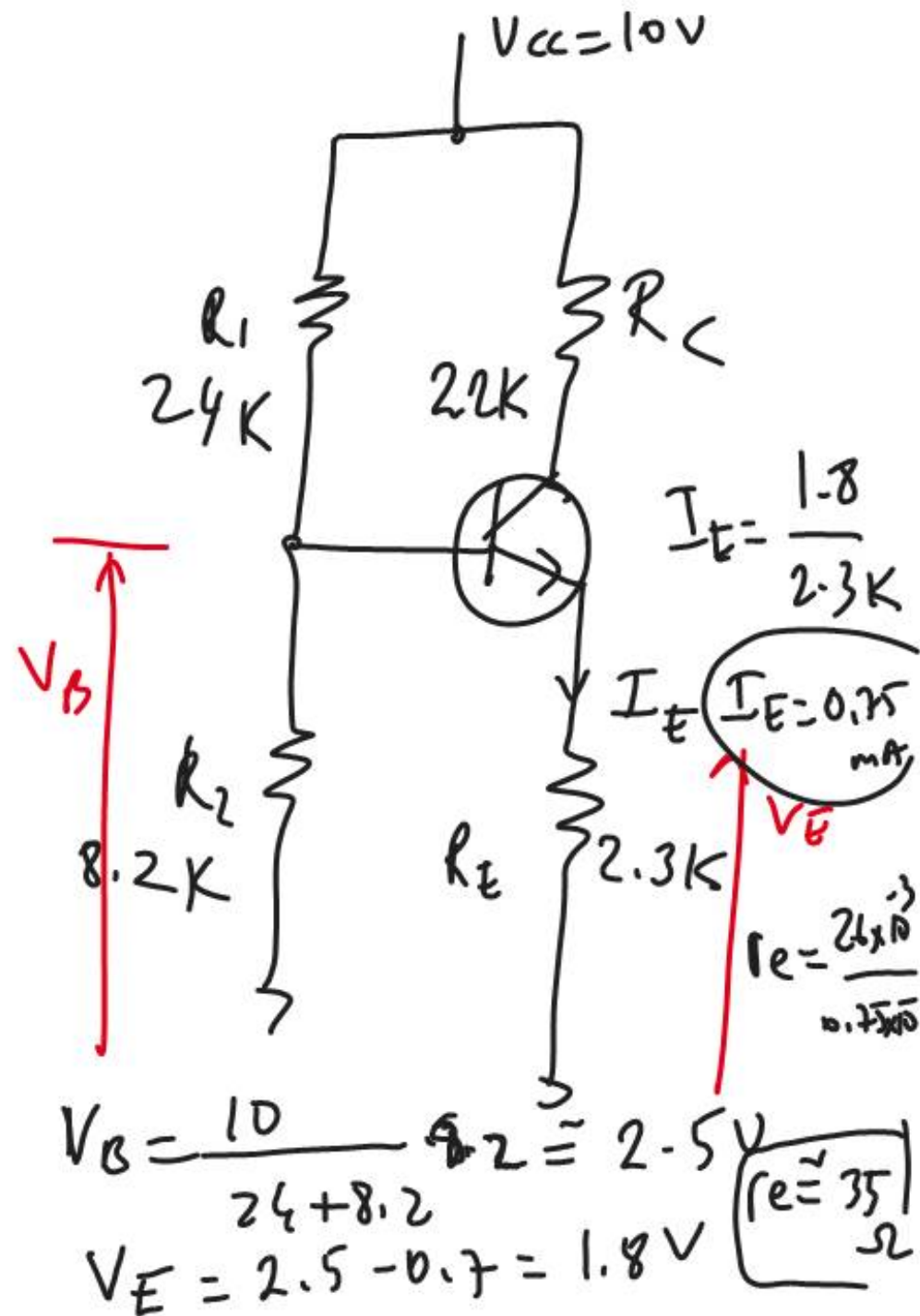


AC Analysis

$$R_D' = R_D // (\cancel{r_d} // R_1 // R_2 // \beta r_e)$$

$$A_{v1} = \frac{v_1}{v_i} = -g_m R_D'$$

$$A_{v2} = -\frac{R_C}{r_e}$$
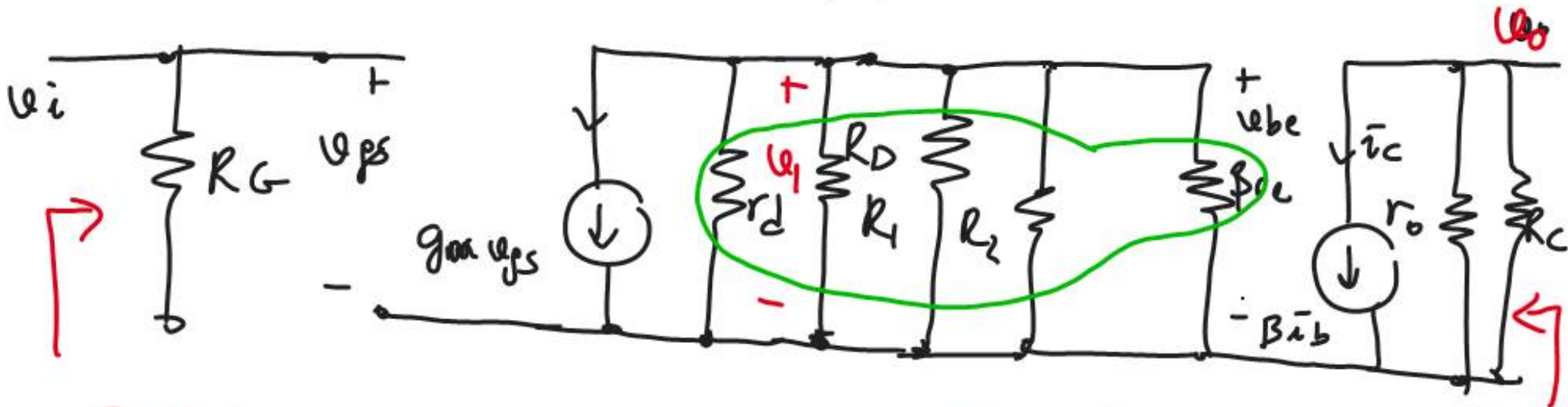
$$A_{vT} = A_{v1} \cdot A_{v2} = +g_m R_D' \cdot \frac{R_C}{r_e}$$



$$Z_i \approx R_G = 10 \text{ m}\Omega$$

$$Z_o \approx R_C // r_o \approx R_C \quad Z_o$$

$$Z_o = 2.7 \text{ k}\Omega$$

$$A_{vT} = \frac{g_m}{r_e} R_D' \cdot R_C$$

$$= \frac{2.67 \times 10^{-3}}{35} \cdot R_D' \cdot R_C \approx \frac{2.67 \times 10^{-3}}{35} \cdot (5k) \cdot (2.7k)$$

Hope to see you next year in ECE 347