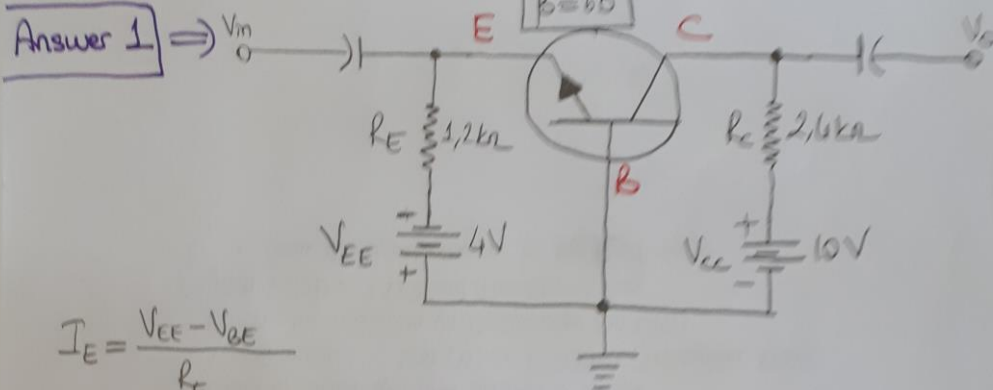


- ECE 246 HOMEWORK 2 -

- ANSWERS -



$$I_E = \frac{V_{CC} - V_{EE}}{R_E}$$

$$= \frac{(4V) - (0.7V)}{(1.2k\Omega)} = \boxed{2.75 \text{ mA}}$$

$$I_E = (\beta + 1) I_B \rightarrow \frac{2.75 \text{ mA}}{60 + 1} = \boxed{I_B = 45.08 \mu\text{A}}$$


$$V_{CE} = V_{EE} + V_{CC} - I_E (R_C + R_E) = 4V + 10V - (2.75 \text{ mA}) (2.4 + 1.2) \Rightarrow \boxed{V_{CE} = 4.1 \text{ volt}}$$

$$V_{CB} = V_{CC} - I_C R_C = V_{CC} - \beta I_B R_C = (10 \text{ volt}) - (60) (45.08 \mu\text{A}) (2.4 \text{ k}\Omega)$$

$$\boxed{V_{CB} = 3.51 \text{ volt}}$$

Answer 2 ⇒

$\beta = 60$

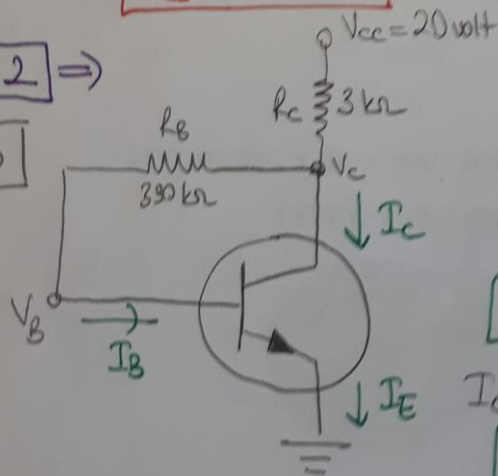

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C}$$

$$I_B = \frac{20 - 0.7}{(390 \text{ k}\Omega) + 60 \cdot (3 \text{ k}\Omega)}$$

$$\boxed{I_B = 33.85 \mu\text{A}}$$

$$I_C = \beta I_B = 60 (33.85 \mu\text{A})$$

$$\boxed{I_C = 2.031 \text{ mA}}$$

$$V_{CE} = V_{CC} - I_C R_C = (20 \text{ volt}) - (2.031) \cdot (3 \text{ k}\Omega) = \boxed{13.907 \text{ volt}}$$

$$V_B = V_{BE} = 0,7 \text{ volt}$$


$$V_E = 0 \text{ volt}$$

$$V_C = V_{CE} = 13,807 \text{ volt}$$

$$I_E = (\beta + 1) I_B = (60 + 1) (33,85 \mu\text{A}) = \underline{2,0654 \text{ mA}}$$

Answer 3 \Rightarrow

$$\beta = 60$$

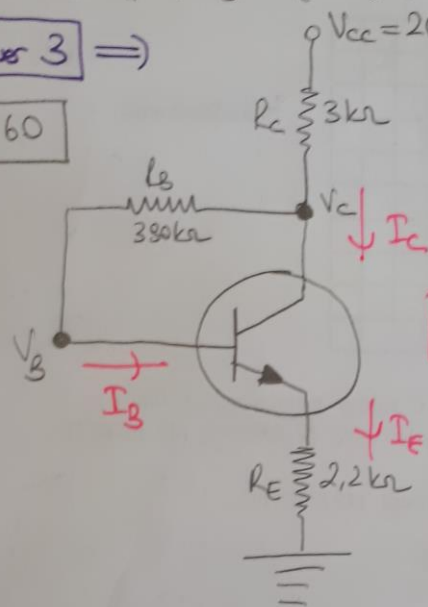

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

$$I_B = \frac{20 - 0,7}{(330\text{k}) + 60(3\text{k} + 2,2\text{k})}$$

$$I_B = 0,0274 \text{ mA} = 27,4 \mu\text{A}$$

$$I_C = \beta I_B = 60(27,4 \mu\text{A})$$

$$I_C = 1,64 \text{ mA}$$

$$I_E = (\beta + 1) I_B = (60 + 1) (27,4 \mu\text{A})$$

$$I_E = 1,67 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= (20\text{V}) - (1,64\text{mA}) (3\text{k} + 2,2\text{k})$$

$$V_{CE} = 11,472 \text{ volt}$$


$$V_E = I_E R_E = (1,67\text{mA}) (2,2\text{k})$$

$$V_E = 3,674 \text{ volt}$$


$$V_{CE} = V_C - V_E = (11,472) + (3,674) = 15,146 \text{ volt}$$

$$V_{BE} = V_B - V_E \Rightarrow (0,7 \text{ volt}) = V_B - (3,674 \text{ volt}) \rightarrow V_B = 4,374 \text{ volt}$$


Answer 4 \Rightarrow

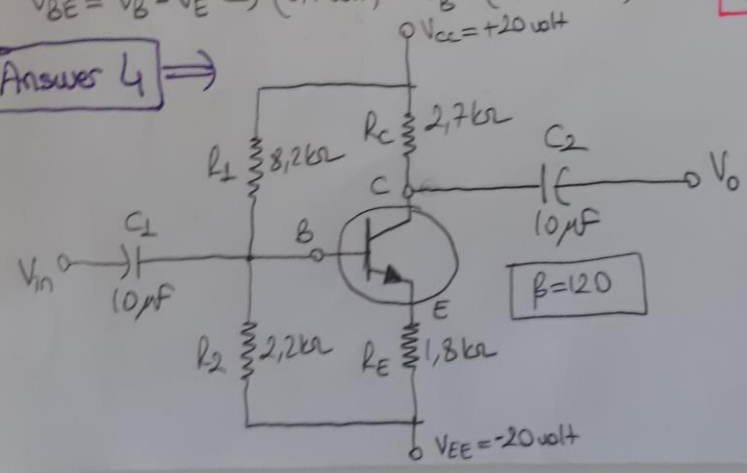
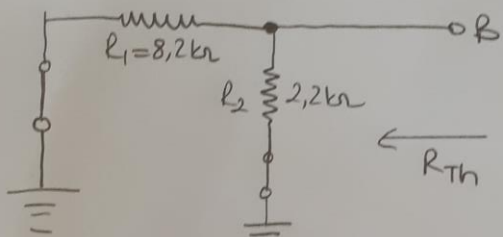
$$R_{Th} = (8,2\text{ k}\Omega) \parallel (2,2\text{ k}\Omega) = 1,73\text{ k}\Omega$$



(Determining R_{Th})

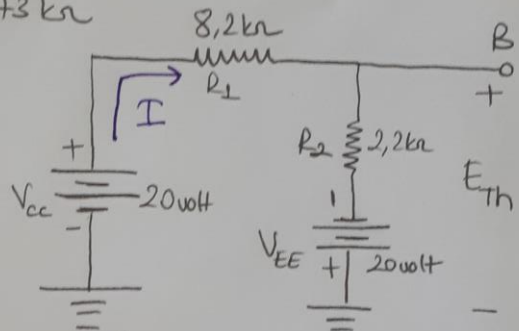


(Determining E_{Th})

$$I = \frac{V_{cc} + V_{EE}}{R_1 + R_2} = \frac{20\text{V} + 20\text{V}}{(8,2\text{ k}\Omega) + (2,2\text{ k}\Omega)} = 3,85\text{ mA}$$

$$E_{Th} = (I R_2) - V_{EE} = (3,85\text{ mA})(2,2\text{ k}\Omega) - 20 = -11,53\text{ volt}$$

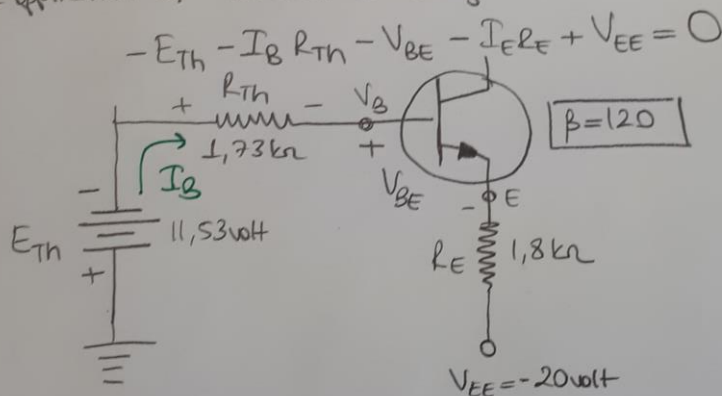The network can then be redrawn as shown in figure, where the application of Kirchoff's Voltage Law results in



$$-E_{Th} - I_B R_{Th} - V_{BE} - I_E R_E + V_{EE} = 0$$

Substituting $I_E = (\beta + 1) I_B$ gives

$$V_{EE} - E_{Th} - V_{BE} - (\beta + 1) I_B R_E - I_B R_{Th} = 0$$

$$I_B = \frac{V_{EE} - E_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E} = \frac{(20\text{V}) - (11,53\text{V}) - (0,7\text{V})}{(1,73\text{ k}\Omega) + (121)(1,8\text{ k}\Omega)}$$

$$I_B = 35,39\text{ }\mu\text{A}$$

$$I_C = \beta I_B = 120(35,39\text{ }\mu\text{A})$$

$$I_C = 4,25\text{ mA}$$

$$V_C = V_{cc} - I_C R_C = (20\text{ volt}) - (4,25\text{ mA})(2,7\text{ k}\Omega)$$

$$V_C = 8,53\text{ volt}$$

$$V_B = -E_{Th} - I_B R_{Th} = -(11,53) - (35,39\text{ }\mu\text{A})(1,73\text{ k}\Omega)$$

$$V_B = -11,53\text{ volt}$$